

QC

535

.S37











### **Net Book.**

¶ This book is supplied to the trade on terms which do not allow them to give a discount to the public.



# ELECTRICAL INSTRUMENTS AND TESTING

HOW TO USE THE VOLTMETER, OHMMETER, AMMETER,  
POTENTIOMETER, GALVANOMETER, THE WHEATSTONE  
BRIDGE, AND STANDARD PORTABLE TESTING SETS

*By*

NORMAN H. SCHNEIDER

*Author of "The Care and Management of Electric Power Plants," "Induction Coils  
and Coil Making," "Electrical Circuits and Diagrams," etc., etc.*

WITH NEW CHAPTERS

## ON TESTING WIRES AND CABLES AND LOCATING FAULTS

*By*

JESSE HARGRAVE

*Assistant Electrical Engineer Postal Telegraph Cable Company*

---

THIRD EDITION, REVISED AND CONSIDERABLY  
ENLARGED, WITH 28 NEW DIAGRAMS

---


NEW YORK :

SPON & CHAMBERLAIN, 123-125 Liberty Street

LONDON :

E. & F. N. SPON, LIMITED, 57 Haymarket, S. W.

1907

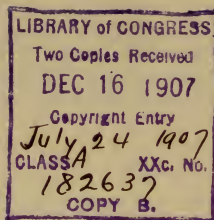


Copyright, 1904  
By SPON & CHAMBERLAIN

Copyright, 1907  
By SPON & CHAMBERLAIN

---

Entered at Stationers' Hall, London

BURR PRINTING HOUSE  
NEW YORK

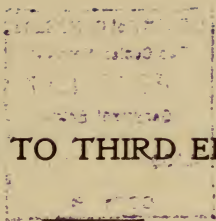

## PREFACE TO THIRD EDITION.

Since this work was first published it has found a ready sale among telegraph and telephone workers, and it was pointed out that the testing of telegraph and telephone wires was not as fully covered as it might have been. With a view to making the book still more attractive and useful to workers in those important branches of the electrical field, Mr. Jesse Hargrave, Assistant Electrical Engineer of the Postal Telegraph Cable Company, was asked to contribute two chapters devoted to the testing of telegraph and telephone wires and cables, and he agreed to undertake the work.

In compiling the matter contained in Chapters XII and XIII Mr. Hargrave has endeavored to carry out Mr. Schneider's ideas of clearness and simplicity. The testing of the wires is taken up in its first stage—the first test of the day, the early-morning test—and the student is taken step by step through the different methods of testing for faults, insulation and conductivity, cable faults, etc.

The different tests and measurements, aside from being described in the simplest possible language, are treated from a strictly practical standpoint, Mr. Hargrave having made use of them in actual practice.

Thanks are due Messrs. Leeds & Northrup for sketches, etc.

## PREFACE.

---

This book is intended for practical use and also as an introduction to the larger works on Electrical Testing.

The apparatus described is modern and universally adopted.

The tests are such as occur daily in the work of the engine room, power house or the technical school.

The illustrations except those of instruments by specified makers are drawn for this book. Detail unnecessary to the subject is omitted, such can be well studied in the apparatus itself.

The formulas given are explained in the text preceding them, and examples are worked out in simple arithmetic. Formulas are often looked upon as intricate mysteries by those who do not understand them. In reality they are often very simple and very necessary. The use of formulas is but a method of arithmetical shorthand. A few minutes devoted to a formula will render it clear and its use easy to those of even limited mathematical education.

The thanks of the author are due to Mr. O. T. Louis for cuts and suggestions, to Mr. F. W. Roller for information on his improved type of hot wire instruments; to Messrs. Willyoung & Gibson, The Weston Electrical Instrument Co., The Keystone Electrical Instrument Co., The General Electric Co., and others.

# CONTENTS.

---

## CHAPTER I.

The simple galvanometer. Deflections not proportional to current. Ampere turns. Selection of size of wire for coil. Tangents. The tangent galvanometer. Influence of the earth on a galvanometer. The astatic galvanometer. Compensating magnet.....	1
--	---

## CHAPTER II.

Sensibility of galvanometer. Figure of merit or constant. The Thompson reflecting galvanometer. Forms of the D'Arsonval reflecting galvanometer. Ballistic galvanometers.....	12
---	----

## CHAPTER III.

Rheostats. Resistance wires and their composition. Laboratory resistance slab. Shunts. Condensers. Keys. The reversing key. The Rymer-Jones key. Commutator. The Kempe discharge key. The standard cell. Clark cell. Weston cell .....	23
--	----

## CHAPTER IV.

The voltmeter. The series ammeter. The shunt ammeter. Types of instruments. Sensibility.	
--	--

Duplex instruments. Potential indicators. Milli-volt and milliamperes. Multipliers. Hot wire instruments. Shunts. The wattmeter. Thomson inclined coil instrument. Queen instruments. Keystone instruments. G. E. potential indicator. Electrostatic voltmeters. Electrodynamometer type. Electromagnetic type. Reading instruments. Parallax. Care of instruments.....	39
---	----

## CHAPTER V.

The Wheatstone bridge. Post Office bridge. How to use the bridge.....	75
---	----

## CHAPTER VI.

Forms of portable sets and how to use them. Queen bridge. Willyoung bridge. Whitney bridge. Sage ohmmeter. Evershed testing set.....	85
--	----

## CHAPTER VII.

Current flow and e.m.f. Galvanometer constant. Direct deflection method. With Queen set. With voltmeter. Testing resistance of galvanometer. Five methods of battery testing.....	102
---	-----

## CHAPTER VIII.

The Potentiometer. Checking voltmeter. Checking e.m.f. Use of various portable testing sets....	123
---	-----

## CHAPTER IX.

Charge and discharge of condenser. Testing capacity and insulation of condenser. Loss of charge method.....	142
---	-----

## CHAPTER X.

Cable testing. Capacity. Insulation and conductivity. Locating cable faults. Varley test. Murray test. ....	135
---	-----

## CHAPTER XI.

Testing with voltmeter. Testing wiring. Insulation of generator. E.m.f. around commutator. Measuring drop. Testing high e.m.f. with low reading voltmeter. Temperature and resistance. Testing temperature by rise of resistance. Test- ing field coils. Testing armature coils. Plot- ting curves of tests. ....	163
---	-----

## CHAPTER XII.

Early morning tests. Wrecks: Locating grounds by Wheatstone bridge measurements. Measure- ment for crosses using Varley test. Measure- ment for crosses using the two cross wires only. Locating a cross by voltmeter test. Insulation tests—milli-ammeter method. Insulation tests by voltmeter method. Conductivity tests. ....	193
---	-----

## CHAPTER XIII.

Location of grounds and crosses by Varley method using multiplied arm ratios. How to find trouble after located. Varley test by Leeds & Northrup's dial testing set. Murray test with Leeds & Northrup dial bridge. Locating openings in cable conductors by bridge method. The Leeds & Northrup fault finder. Resistance measurement with the Leeds & Northrup fault finder. Fault location with the Leeds & Northrup fault finder. To locate openings using buzzer and telephone...	211
--	-----

## LIST OF ILLUSTRATIONS.

---

1	Simple galvanometer.....	1
2	Tangent 15°.....	7
3	Tangent 30°.....	7
4	Tangent 60°.....	7
5	Tangent 75°.....	7
6	Astatic galvanometer.....	9
7	Compensating magnet.....	10
8	Tripod galvanometer.....	13
9	Four coil galvanometer.....	15
10	D'Arsonval galvanometer.....	16
11	D'Arsonval galvanometer.....	18
12	Wall pattern galvanometer.....	19
13	Willyoung suspension.....	20
14	Willyoung portable galvanometer.....	21
15	Galvanometer scale.....	22
16	Rheostat plug switch.....	24
17	Shunt and galvanometer.....	28
18	Condenser.....	30
19	Condenser built up.....	30
20	Condenser adjustable.....	31
21	Reversing key.....	33
22	Rymer Jones key.....	34
23	Commutator.....	35
24	Kempe discharge key.....	36
25	Weston standard cell.....	38
26	Voltmeter connection.....	40
27	Series ammeter.....	41

28	Shunt ammeter.....	41
29	Weston voltmeter detail.....	42
30	Weston portable instrument.....	43
31	Weston laboratory instrument.....	44
32	Laboratory instrument scale.....	44
33	Switchboard instrument.....	45
34	Switchboard instrument flush type.....	46
35	Switchboard instrument illuminated dial.....	47
36	Switchboard instrument illuminated dial.....	47
37	Duplex instrument.....	48
38	Potential indicator scale.....	50
39	Multipliers.....	52
40	Styles of instruments.....	53
41	Whitney hot wire system.....	55
42	Whitney portable instrument.....	56
43	Whitney switchboard instrument.....	57
44	Weston shunts.....	58
45	Whitney shunts.....	59
46	Solenoid type.....	61
47	Solenoid type.....	61
48	Magnetic vane type.....	61
49	Magnetic needle instrument.....	62
50	Electromagnetic instrument.....	62
51	Thermometric instrument.....	62
52	G. E. potential indicator.....	63
53	Thomson inclined coil ammeter.....	64
54	Thomson switchboard ammeter.....	65
55	Thomson edgewise voltmeter.....	66
56	Thomson astatic voltmeter.....	67
57	Edgewise voltmeter.....	72
58	Kite or lozenge bridge.....	76
59	P. O. bridge.....	78
60	Willyoung bridge.....	86
61	Willyoung bridge diagram.....	87
62	Queen Acme set.....	89
63	Whitney testing set... ..	92
64	Whitney testing set diagram.....	92

65	Slide wire bridge.....	95
66	Sage ohmmeter.....	97
67	Sage ohmmeter diagram.....	98
68	Sage ohmmeter diagram.....	98
69	Evershed testing set.....	99
70	Evershed testing set.....	100
71	Fall of potential diagram.....	103
72	Direct deflection method.....	105
73	Setting of Queen bridge.....	111
74	Direct deflection with voltmeter.....	114
75	Resistance of galvanometer.....	115
76	Resistance of galvanometer.....	116
77	Resistance of battery.....	117
78	Resistance of battery by bridge.....	120
79	Potentiometer.....	124
80	Willyoung potentiometer.....	131
81	Charging condenser.....	135
82	Discharge of condenser.....	136
83	Telephone test of cable.....	145
84	Testing cable.....	146
85	Circuit for cable test.....	148
86	Cable test with Aone set.....	150
87	Cable test with Aone set.....	151
88	Testing for fault.....	155
89	Testing for fault.....	156
90	Varley test.....	157
91	Murray test.....	158
92	Murray test with Aone set.....	161
93	Testing resistance with voltmeter.....	164
94	Insulation of generator.....	165
95	E.m.f. around armature.....	173
96	E.m.f. around armature.....	173
97	Drop across lamp.....	174
98	High e.m.f. with low reading voltmeter.....	176
99	Testing field coil.....	180
100	Testing field coil.....	180
101	Testing field coil.....	181

102	Testing armature.....	183
103	Testing armature.....	184
104	Testing drop on line.....	185
105	Plotting curves.....	188
106	Relay test for a "ground".....	194
107	Relay test for an opening.....	194
108	Relay test for a cross.....	195
109	Relay test-out of a wreck.....	196
110	Automatic signaling device to indicate when wires come O.K.....	196
111, 112 and 113	Measurements for crosses using Varley test.....	199, 200
114	Measurement for crosses using the two crossed wires only. First method.....	202
115	Measurement for crosses using the two crossed wires only. Second measurement.....	203
116	Another method of locating a cross.....	204
117 and 118	Locating a cross by voltmeter test....	205, 206
119	Insulation tests. Milli-ammeter method.....	207
120 and 121	Location of cable fault by Varley method, using multiplied arm ratios.....	212, 213
122	Check measurement.....	214
123	Method of finding trouble after locating it.....	216
124	Theoretical arrangement of Leeds & Northrup dial bridge.....	218
125	Actual arrangement of Leeds & Northrup dial bridge .....	219
126	Locating opening in cable conductor by bridge measurement .....	220
127	Locating opening in cable conductor by bridge measurement. Second method.....	221
128	Resistance measurement with the Leeds & North- rup fault finder.....	224
129	Fault location with the Leeds & Northrup fault finder. First method.....	225
130	Fault location with the Leeds & Northrup fault finder. Second method.....	226

131	Fault location with the Leeds & Northrup fault finder. Third method.....	227
132	To locate opens using buzzer and telephone by employing Leeds & Northrup fault finder.....	227
133	Actual arrangement of Leeds & Northrup fault finder .....	228

## CONTENTS OF TABLES.

---

I.	Resistance of Copper Wire.....	5
II.	Natural Tangents of Angles.....	8
III.	Setting of Bridge Arms.....	91
IV.	Specific Inductive Capacity.....	141
V.	Voltmeter readings and Resistance Tests.....	171
VI.	Increase of Resistance with Temperature.....	177

## INTRODUCTION.

---

**Classification.** Electrical instruments used in the detection or measurement of electrical currents are divisible into two classes.

The first class includes such as show the presence of a current without directly indicating its value in units of measurement.

To this class belong the various kinds of galvanometers.

Instruments of the second class indicate by the movement of pointers over dials or some such means the value of the electrical current passing.

The dial under the pointer or index is graduated into divisions representing units of measurement. Examples of this class are the voltmeter, ammeter and wattmeter.

Instruments which leave a record of the fluctuations or the current strength for a given period of time are Recording Voltmeters, Recording Watt-

meters, etc., according to the unit by which their records are read.

As the underlying principles of instruments belonging to the latter class are mostly to be found in those of the first class, the latter will be first considered.

## CHAPTER I.

### GALVANOMETERS.

**The Simple Galvanometer.** Perhaps the simplest form of galvanometer is shown in Fig. 1, and although home made, is capable of many uses.

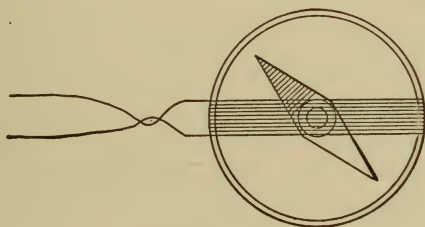


FIG. 1.

An ordinary mariner's compass has a few turns of fine insulated copper wire wound around its case, a suitable gauge being No. 26 B. & S. or No. 28 S.W.G.

If current from a battery or other source be sent through the coil of wire, the magnetic needle will tend to turn at an angle to the wire turns, providing the galvanometer has first been set so that both needle and wire turns are parallel.

The stronger the current through the coil, the farther the needle swings out from it.

And reversing the connections will cause the needle to swing in a reversed direction as the current is reversed in its flow around the coil.

But it will be noticed that the amount of the needle swing is not in proportion to the strength of the current.

Let the circle or card forming the bottom of the compass case be divided into 360 degrees having the zero where one end of the needle normally rests.

On connecting the coil ends to a dry cell suppose the needle swings out to 30 degrees.

If a second cell is put in series with the first and the two cells connected to the coil as before the swing may now only be 35 degrees, a gain of but five degrees by doubling the current strength instead of a gain of 30 degrees.

It is to be remarked before proceeding that these readings as they are termed are only for sake of example, not being necessarily exactly the number of degrees obtained in any experiment.

If a galvanometer gives a large reading with one cell as compared with a reading taken under precisely similar conditions on another galvanometer the one giving the largest reading will be said to have the greater sensibility.

The movement of a galvanometer needle from one position to another is termed its deflection and is measured in degrees.

Now the primary laws of electricity teach that the current strength or rate of flow depend upon the electromotive force (e.m.f.) or voltage impelling that current and upon the resistance of the circuit through which it travels.

Increasing the e.m.f. or decreasing the resistance increases the current flow, and vice versa, decreasing the e.m.f. or increasing the resistance decreases the current flow.\*

In order to decrease the deflection of the needle resistance must be added to the circuit, this may be done by means of a rheostat.

One form of rheostat would consist of coils of wire so connected that one or any desired number of coils could be inserted in series with the galvanometer. The electrical energy expended in these coils being therefore not available in the galvanometer coils would have no effect upon its needle deflection which would be thereby reduced.

The sensibility of this galvanometer will depend upon the ampere turns of its coil (neglecting friction, etc.), and the coil winding should be suitable for the current in the circuit in which it is used.

If the galvanometer is to measure currents in a circuit of low resistance, its coil should be also of low resistance and vice versa.

The meaning of ampere turns must be thoroughly understood. It will suffice here to remark that one ampere traveling round the needle for

---

\*See "Electricity and Its Laws, for Beginners," for the elementary laws governing electric current.

one turn would equal one hundredth of an ampere for one hundred turns and the needle deflection would be the same in each case.

In a circuit of low resistance, a large current would flow (presumably) and this current would not need to travel around the needle as many times as the lesser current in a circuit of higher resistance to produce the same deflection. In this case using a coil of many fine wire turns in the low resistance circuit would only reduce the current around the needle. And using a coil of large wire and few turns would not give ampere turns enough in a circuit of high resistance.

An apparent contradiction may be met by the experimenter who in adding more turns of wire to a simple galvanometer gets a greater deflection of the needle. This, however, only shows that the ampere turns were not sufficient in the first case, and therefore the contradiction does not exist.

To sum up, the reason for using a large number of fine wire turns as is done in some galvanometers is that the current strength is often so small as to require its circulation many times around the needle to produce the requisite ampere turns.

It is very common practice to speak of a coil as being wound to a given resistance when ampere turns are really desired. If resistance were the object, a resistance metal could be used to advantage.

The relation of resistance and diameter of copper wire is given in Table I., from which may be

TABLE I.

TABLE SHOWING GAUGE DIAMETER, AREA AND RESISTANCE OF COPPER WIRE.

Gauge No.	Brown and Sharpe Gauge.			Standard Wire Gauge.		
	Dia- meter inches.	Circular Mils.	Ohms per 1000 ft. at 15° Cent.	Dia- meter inches.	Circular Mils.	Ohms per 1000 ft. at 15° Cent.
0000	.4600	211600	.048	.400	160000	.063
000	.4096	167810	.060	.372	138384	.073
00	.3648	133080	.076	.348	121104	.084
0	.3249	105590	.096	.324	104976	.096
1	.2893	83694	.121	.300	90000	.113
2	.2576	66373	.153	.276	76176	.133
3	.2294	52633	.193	.252	63504	.160
4	.2043	41743	.243	.232	53824	.189
5	.1819	33102	.307	.212	44944	.226
6	.1620	26250	.387	.192	36864	.276
7	.1442	20817	.489	.176	30976	.329
8	.1284	16510	.616	.160	25600	.397
9	.1144	13094	.777	.144	20736	.490
10	.1018	10382	.980	.128	16384	.624
11	.0907	8233.7	1.236	.116	13456	.758
12	.0808	6530.3	1.559	.104	10816	.940
13	.0719	5178.2	1.966	.092	8464	1.202
14	.0640	4106.2	2.479	.080	6400	1.590
15	.0570	3255.8	3.127	.072	5184	1.963
16	.0508	2582.7	3.942	.064	4096	2.485
17	.0452	2047.6	4.972	.056	3136	3.246
18	.0403	1624.9	6.269	.048	2304	4.420
20	.0319	1022	10.140	.036	1296	8.038
22	.0253	642	16.120	.028	784	13.212
24	.0201	404	25.630	.022	484	21.394
26	.0159	251	40.750	.018	324	31.963
28	.0126	160	67.790	.015	219	47.707
30	.0100	100	103.300	.012	154	66.866
32	.0080	63	183.	.011	106	103.410
34	.0063	40	291.	.009	84	127.860
36	.0050	25.	462.	.008	57	189.660

computed the size of wire to use for a galvanometer coil.

**Deflections not Uniform.** The needle does not move twice as far for twice the current because as soon as it starts to move it commences to get out of the strongest influence of the coil, or out of the intense part of the field.

If the coil is very large and the needle very small, then the latter can deflect more uniformly as the field is more uniform.

**Tangent Galvanometer.** The tangent galvanometer has a coil wound around a ring perhaps twelve inches in diameter, and the needle is a fraction of an inch in length.

In this case the deflections of the needle are compared by referring to a table of tangents, Table II.


A tangent is a straight line perpendicular to the diameter of a circle, limited in length by the sides of the angle one of which is the diameter of the circle.

In Fig. 2 the dotted line is the diameter of the circle and passes clear through the zero mark. *N* is a straight line drawn through the centre of the pointer or needle, in other words shows the number of degrees of deflection. The degrees between this line and the zero will be the number of degrees forming the angle of deflection, angles being measured in degrees. If the pointer were at

$45^\circ$  the angle would be one of  $45^\circ$  or half a right angle ( $90^\circ$ ).

$T$  is a straight line perpendicular to the diameter but cut by  $N$ . The portion between the diameter line and where it is cut by  $N$  is the tangent. Fig. 2 represents an angle of about  $15^\circ$ , that is, the needle is deflected  $15^\circ$ . Fig. 3 shows the tangent of an angle of about  $30^\circ$ , Fig. 4 the tangent of  $60^\circ$ , and Fig. 5 the tangent of about  $75^\circ$ .

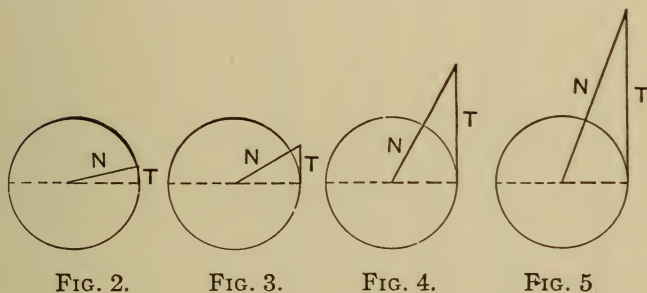It will be seen that the tangent increases in



length very rapidly, far more so than the deflection angle.

To make a comparison, let the needle be deflected  $5^\circ$ , its tangent will be .0875, double the deflection, the tangent of  $10^\circ$  is .1763, more than double the one of  $5^\circ$ .

Deflect the needle to  $30^\circ$  or six times its first deflection and the tangent is .5774, about seven times.

A still farther deflection to  $60^\circ$ , or twelve times

the first one, the tangent is now 1.7321, or about twenty times that of  $5^\circ$ .

In a tangent galvanometer when it is desired to compare the strength of two currents, readings

TABLE II.  
Natural Tangents of Angles.

Angle Degrees	Tangent	Angle Degrees	Tangent	Angle Degrees	Tangent
1	.0174	31	.6008	61	1.8040
2	.0349	32	.6248	62	1.8807
3	.0524	33	.6494	63	1.9626
4	.0699	34	.6745	64	2.0503
5	.0874	35	.7002	65	2.1445
6	.1051	36	.7265	66	2.2460
7	.1227	37	.7535	67	2.3559
8	.1405	38	.7812	68	2.4751
9	.1583	39	.8097	69	2.6051
10	.1768	40	.8391	70	2.7475
11	.1943	41	.8692	71	2.9042
12	.2125	42	.9004	72	3.0777
13	.2308	43	.9325	73	3.2709
14	.2493	44	.9656	74	3.4879
15	.2679	45	1.0000	75	3.7321
16	.2867	46	1.0355	76	4.0108
17	.3057	47	1.0724	77	4.3315
18	.3249	48	1.1106	78	4.7046
19	.3443	49	1.1504	79	5.1446
20	.3639	50	1.1918	80	5.6713
21	.3838	51	1.2349	81	6.3138
22	.4040	52	1.2799	82	7.1154
23	.4244	53	1.3270	83	8.1443
24	.4452	54	1.3764	84	9.5144
25	.4663	55	1.4281	85	11.4301
26	.4887	56	1.4826	86	14.3007
27	.5095	57	1.5399	87	19.0811
28	.5317	58	1.6003	88	28.6863
29	.5543	59	1.6643	89	57.2900
30	.5773	60	1.7321	90	infinite

are made of the two deflections obtained. The tangents of these angles or deflections are then compared.

If one deflection were  $11^\circ$  and the second one

63°, the second current would be nearly ten times the greater, or as .1944 is to 1.9626.

**Influence of the Earth's Magnetic Field.** It was necessary to move the galvanometer around so as to bring the needle point to zero.

As the galvanometer was made out of a compass this was done because the needle tended to point to the magnetic *N* and *S* of the earth.

In order to avoid having to turn the instrument about before using it, the influence of the earth's

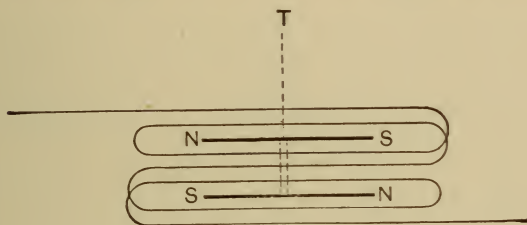


FIG. 6.

magnetic field is compensated for in the astatic galvanometer.

**The Astatic Galvanometer.** In Fig. 6 two magnetic needles are rigidly attached to a stem in such manner that the *N* pole of one is over the *S* pole of the other. If both needles are equally strong, such a combination on being suspended by a fine thread *T* or balanced on a point, would stay in whatever direction it was placed. It would be entirely unaffected by the earth's mag-

netic field, one needle neutralizing the other. But this is not obtained in practice, the pair of needles take a set position in which, however, their movement is little restrained by the earth's magnetism.

The coil is wound as shown in order that the

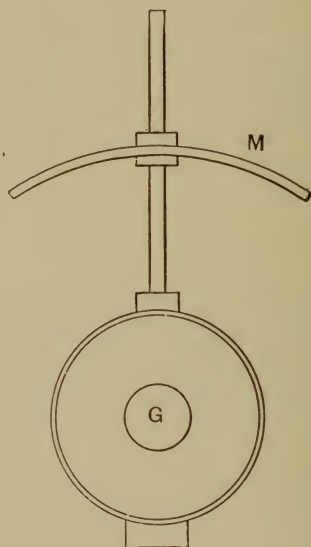


FIG. 7.

current may tend to turn each needle in the same direction.

**Compensating Magnet.** A compensating magnet is used with certain forms of galvanometers to neutralize the effect of the earth's magnetism on the needle.

It is generally of a curved form as in Fig. 7 at *M*, being mounted on a rod upon which it can be slid up or down over the galvanometer *G*. It can also be rotated on its axis.

An ordinary bar magnet is used for the same purpose by placing it in different positions with relation to the galvanometer until the desired result is obtained.

Where the latter method is pursued it is a good plan to attach the magnet to a block of lead so that a slight jar will not displace it.

## CHAPTER II.

### GALVANOMETERS.

In describing galvanometers, the terms constant, figure of merit and sensibility are used.

A full description of these terms rightly belongs to the pages on practical testing.

But it may be stated here, that these terms are those by which galvanometers are compared when considering their sensitiveness.

The constant or sensibility is the number of ohms resistance through which an e.m.f. of one volt will cause the galvanometer to give a deflection of one degree on a standard scale.

A more complete explanation of the terms will be found in a later chapter.

**The Thompson Reflecting Galvanometer.** In the Thompson reflecting galvanometer, a flat mirror of less than one-half inch in diameter has a number of fine steel magnets fastened on its back. This mirror-magnet combination is suspended by a fibre of cocoon silk inside a coil of many turns of fine insulated wire.

When the magnets are deflected by current flowing in the coil, the mirror also turns, and a beam of light directed on it is reflected on a curved scale.

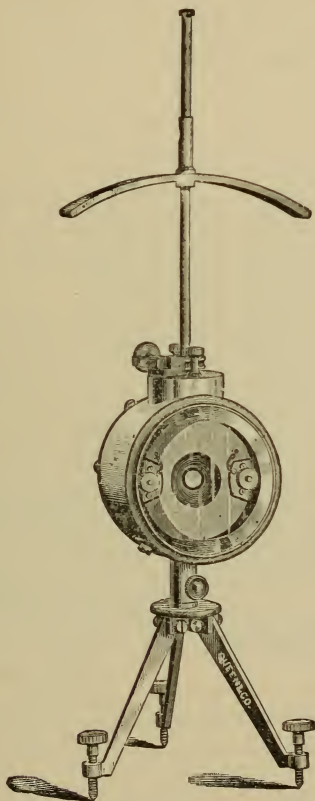


FIG. 8.

This scale has the zero mark in the centre, readings being thus possible in either direction.

A compensating magnet is attached on a rod fixed to the top of the case and leveling screws are provided to level the instrument.

As the mirror is small and light it has little momentum, its moving in a small chamber gives it an air cushion, and it quickly comes to rest or is "dead beat."

In Fig. 8 is the tripod form of Thompson reflecting galvanometer.

This instrument is made with interchangeable coils from 150 ohms to 5000 ohms in resistance. The sensibility for minute currents with the 5000 ohm coil is very great.

A four coil reflecting galvanometer of the Thompson pattern in Fig. 9 has a hinged door which opens, breaking the circuit through the coils.

This gives easy access to the suspension system. Spring contacts *C* seen at the lower part of the base make connection at *P* when the door is shut.

The magnetic system is suspended from a tube *B* equipped with an adjusting screw *K*.

A compensating or control magnet *M* is fitted in a tube and adjusted by the milled head *S*.

**Moving Coil Galvanometers.** One of the greatest drawbacks to the use of galvanometers built on the Thompson pattern is their sensitiveness to external influences. In large cities where trolley cars and buildings of iron frame construction abound, this type of instrument needs constant adjustment. Allowances and checks have to

enter into tests made with them so largely as to almost prohibit their use.

A class of galvanometers based upon the rotation of a coil carrying current in a magnetic field

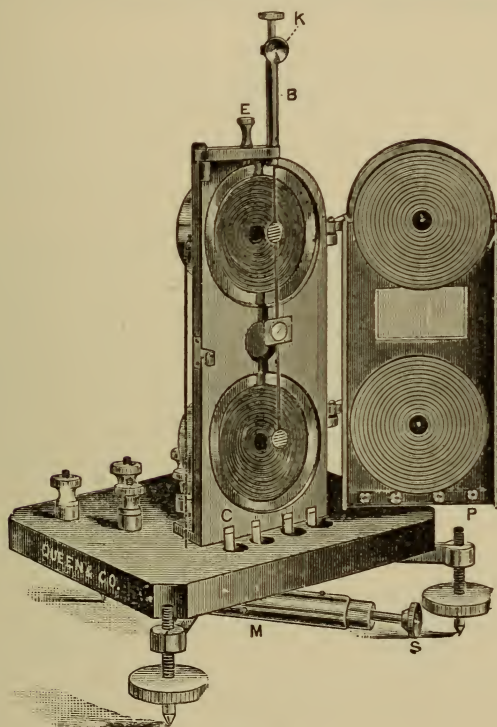


FIG. 9.

has been so perfected that they are being almost universally adopted.

The pioneer moving coil galvanometer is that invented by D'Arsonval.

**The D'Arsonval Galvanometer.** In Fig. 10 *H* is a horseshoe shaped magnet or series of magnets bolted together and to the base *B* which is supplied with leveling screws *LL*.

A core of soft iron *I* is held stationary, around

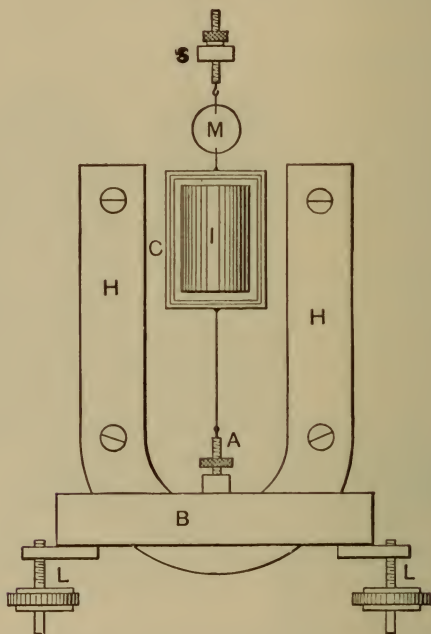


FIG. 10.

which turns a coil of fine insulated wire *C*. This coil is suspended between adjustable screws *SA* by fine wires in such manner that current entering at the screw *S* passes through the coil and out at *A*, or vice versa.

A tiny mirror  $M$  of circular form is also carried by the suspension wires and turns with the coil.

When current is applied to  $S$  and  $A$ , the coil tends to turn in the magnetic field formed by the magnet poles and strengthened by the soft iron core  $I$ .

The instrument is so constructed that the magnetic field is as nearly uniform as possible, and the deflections of  $M$  are proportional to the current flowing through  $C$ .

**Horizontal Magnet.** This type of D'Arsonval galvanometer is shown in elevation in Fig. 11.

In this galvanometer the coil and mirror are suspended in a tube by a phosphor bronze strip.

This form of construction permits the mirror and coil to swing but to return to zero without any distortion from twisting of the suspension or "set."

Interchangeable tubes are furnished with coils of varying resistances and sensibilities. The 20 ohm tube has a sensibility of 75 megohms (75 million ohms). The 4000 ohm tube has the extreme sensibility of 1750 megohms.

The deflections in these instruments are proportional to the current.

The moving system is either dead beat or ballistic.

The ballistic type is adapted for the measurement of currents of short duration. The current has ceased before the deflection is complete. But

the impetus received by the coil carries it to a distance and gives the possibility of measuring the current strength from the distance of swing.

A form of D'Arsonval galvanometer, Fig. 12, is adapted for attachment to a wall. The galvano-



FIG. 11.

meter is entirely enclosed in a cylindrical case; the mirror deflections being observed through a window in front.

A removable bracket carries a reading telescope and scale so proportioned that it gives the same

effect as a standard millimeter scale at a distance of one meter.

Gimbal suspension of the galvanometer itself causes it to be self-leveling.

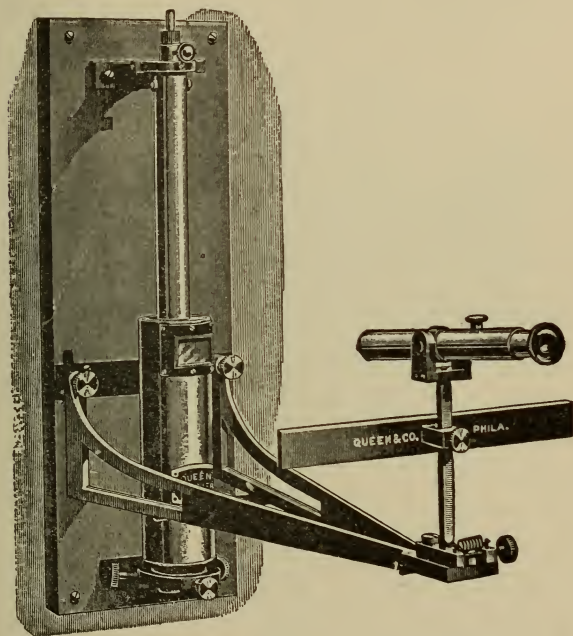


FIG. 12.

The scale deflections are directly proportional to the current causing them.

The sensibility is about 500 megohms per volt of battery used, a sensibility sufficient for all ordinary measurements.



of new suspension wires. It is clamped by a set screw at  $e$ .

The upper suspension is grounded on the tube case, the lower one  $L$  is connected to a platinum faced disc  $F$ .

The electrical connections are therefore from one binding post through the case, down  $u$ , coil  $L$

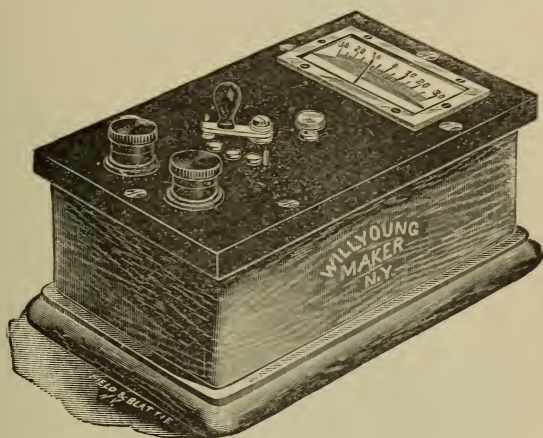


FIG. 14.

and out through  $F$  to a spring connected to a binding post.

A portable D'Arsonval galvanometer, Fig. 14, is constructed with a sensibility of upwards of one megohm. It is dead beat and has a scale divided from a central zero into 50 divisions right or left.

As has been remarked before, instruments constructed on the D'Arsonval principle read in direct proportion to the current passing.

And they are not affected by external magnetic fields. An instrument similar to the above with 100 cells of battery would be capable of measuring insulations up to 100 megohms, and higher if fractions of a deflection be read.

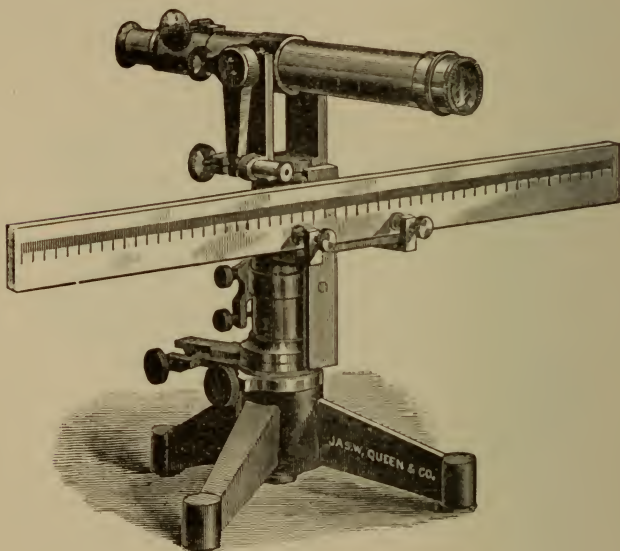


FIG. 15.

**Scale and Lamp.** The oscillations of the galvanometer mirror are read in two ways. By watching a spot of light on a scale or observing the image of the scale reflected in the mirror by means of a telescope.

The scale is made in various forms but in principle resembles that in Fig. 15.

## CHAPTER III.

### RHEOSTATS, KEYS AND SHUNTS.

**Rheostats.** The resistances used in testing-rheostats are mostly made of insulated wire having a high specific resistance, and but little liable to change under varying temperature conditions.

They are also wound non-inductively so that no currents due to inductance shall affect the galvanometer. This end is obtained by winding the wire so that the current shall flow half around the spool in one direction and half around it in the reverse direction.

The piece of wire may be either doubled upon itself and then wound on, or may be wound on in two equal lengths, the inside ends being soldered together. The outside ends are for attachment to the circuit.

It is always desirable that the binding posts or terminals of a resistance coil be made large enough that they do not offer any perceptible resistance to the circuit.

In the practical construction of rheostats for testing, they are adjustable in several ways. The

cutting in or out of coils is effected by plugs or sliding switches.

In the plug form of switch, Fig. 16, a brass taper plug  $P$  is inserted in a hole between brass strips  $S$ , connecting these strips together.

The resistance coils  $R$  are connected as shown. If one plug be now removed from the hole, a coil becomes part of the circuit between  $A B$ . A second plug cuts in another coil and so on. Each coil thus cut in adds its resistance to the circuit.

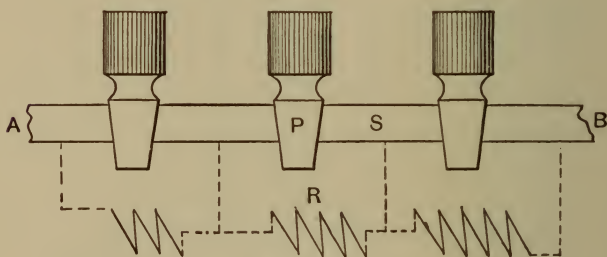


FIG. 16.

The chief disadvantages of this system are that it requires a plug for each coil, and that if a plug be not tight a coil is not entirely cut out.

Plug switches are also arranged to connect *in* coils when inserted in holes.

Modern rheostats are being constructed, however, with sliding switches which cannot get lost and which make good firm contact.

**Resistance Wires.** The choice of a metal for resistances to be used for testing purposes must be

determined by several points. The metal must change in resistance as little as possible under varying temperatures.

It is also desirable that the metal used shall have a high specific resistance, that is, its resistance per unit of length shall be as great as possible in comparison with other metals. This is in order to keep the coil as small as possible, resistance coils with figures as high as 100,000 ohms being in common use.

German silver, although formerly much used, has been replaced by several compound metals.

The composition of some commonly used resistance wires is as follows: German silver, copper 60 parts, zinc 26 parts, nickel 14 parts. This alloy is also made with 30 per cent. nickel.

Platinum silver contains platinum 67 parts, silver 33 parts.

Platinoid is German silver 98 parts, tungsten 2 parts.

Manganin contains copper 84 parts, manganese 4 parts, nickel 12 parts.

The relative resistances of the above are in comparison with copper as 1, as follows: German silver 12, platinum silver 15, platinoid 20 and manganin 30.

As the proportions of these alloys is varied by different manufacturers, the figures given are but approximate. For example, if the platinum silver alloy were platinum 50 and silver 50 parts, its relative resistance would be about 20

as compared with copper, or more nearly that of platinoid.

Of the above alloys, manganin seems to be the most favored by manufacturers of high-class instruments, although platinoid is preferred by some.

**Glass Slab Resistances.** It often becomes necessary to use a high resistance for testing purposes when none is at hand. A ground glass slab covered with lead pencil lines will serve for temporary work.

To make one proceed as follows:

Take a slab of ground glass about 1 inch by 4 inches and drill a hole at each end large enough to receive the machine screws at the bases of two binding posts.

Rub a soft lead pencil over the slab around these holes covering the area of a circle of one inch or thereabouts. Blow off the dust and lay a few strips of tin-foil over the holes nearly covering the lead pencil circles. Slip a washer over one machine screw and also a few washers of tin-foil and insert the screw in the hole from the plain side of the glass. The screws should penetrate the tin-foil on top of the glass also. Then screw down the binding post.

The tin-foil below the slab acts as a cushion between the washer and the glass. That on top of the slab also acts as a cushion, but it ensures a better contact between the binding post and pencil circle.

A similar binding post is to be fitted at each end of the slab.

Now draw a few lines joining the pencil circles. Measure the resistance of this penciled path. To lower its resistance rub on more pencil lead between the circles. To raise its resistance, rub out some of the lead. Of course all dust should be blown off.

The object of the circles was to give a point of junction between the lines and binding posts.

Resistance slabs as above may be varnished or covered with insulating compound if desired. But pencil lead or plumbago being carbon is extremely erratic in the matter of maintaining a given resistance.

**Galvanometer Shunts.** As in most cases it is not desirable to permit the entire current used in a test to flow through the galvanometer, part of it is shunted or caused to pass around the latter.

A shunt bears a definite ratio to the resistance of the galvanometer, being generally adjustable to

$\frac{1}{9}$ ,  $\frac{1}{99}$ , or  $\frac{1}{999}$ , of its resistance so that  $\frac{1}{10}$ ,  $\frac{1}{100}$ ,

or  $\frac{1}{1000}$  part of the current only passes into the galvanometer.

Fig. 17 shows the connections of the shunts *S* and galvanometer *G*.

The degree in which the shunt increases the

range of deflection of a galvanometer is termed its multiplying power.

If one-tenth of the current flowing went through the galvanometer and nine-tenths through the shunt, the current in the circuit would be actually ten times that through the galvanometer.

The current therefore in the galvanometer must be multiplied by the multiplying power of the shunt to show its true value in the circuit.

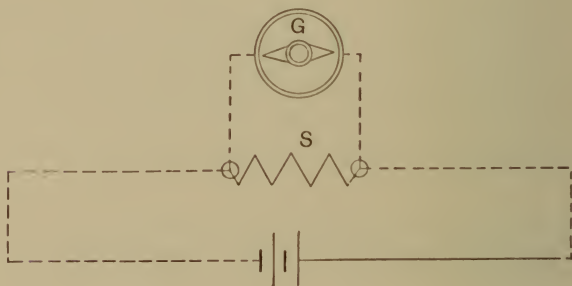


FIG. 17.

In order to find the resistance necessary in a shunt to be used with a certain galvanometer, the resistance of the latter is to be divided by the multiplying power desired less one.

As an example, let a shunt be needed for a galvanometer of 2000 ohms resistance where only one-fifth the total current is to pass through the galvanometer. This would equal a multiplying power of 5; then  $\frac{2000}{5-1} = 500$  ohms.

**Formula.** Let  $G$  be resistance of galvanometer;  $n$  be multiplying power of shunt;  $S$  resistance of shunt; then  $S = \frac{G}{n-1}$ .

To find the multiplying power of a shunt of given resistance add its resistance to that of the galvanometer and divide the answer by the resistance of the shunt.

For example, galvanometer is 10,000 ohms, shunt 1000 ohms,  $10,000 + 1000 = 11,000$ , divided by 1000 = 11, the multiplying power of the shunt.

**Formula.** Let resistance of galvanometer be  $G$  and shunt  $S$ ; then  $\frac{G+S}{S} =$  multiplying power.

Shunts should be connected to the galvanometer by wires of ample size, no undue resistance should be introduced by the connecting wires.

It is a good plan always to use the shunt of greatest multiplying power at first and reduce as occasion requires. Otherwise a heavy current in the galvanometer might injure suspension.

**Condensers.** The modern condenser is but a handy form of the Leyden jar; it consists of leaves of tin-foil alternating with insulated paper, mica, glass, etc., insulation between the tin-foil layers being of prime importance.

The layers are built up as follows, Fig. 18: First a sheet of insulation  $A$  (or dielectric), then a sheet of tin-foil  $B$  projecting at one end; another sheet

of insulation *C* and the next sheet of tin-foil *D* projecting at the other end.

Sheet after sheet is built up, Fig. 19, until the desired number is obtained, the whole mass then being subjected to immersion in paraffin or other insulator and kept under heavy pressure until set.

The portions of tin-foil projecting from one end being pressed together form one connection, the ends at the other being the second connection.

This results in every other sheet of tin-foil being connected, in fact the condenser can be considered

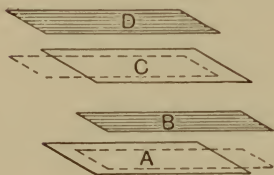


FIG. 18.

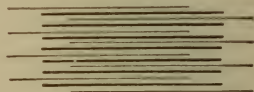


FIG. 19.

as being made up of two large sheets of tin-foil highly insulated from each other.

Condensers are made up with many different dielectrics, mica being one of the best for testing purposes. Tin-foil is most always used for the metal plates.

Adjustable condensers permit of their capacities being varied by means of plugs which cut in or out of multiple, portions of the foil sheets. In Fig. 20 is the diagram of an adjustable condenser.

*CC* are the tin-foil sheets, *BB* brass strips which carry the terminals or binding posts.

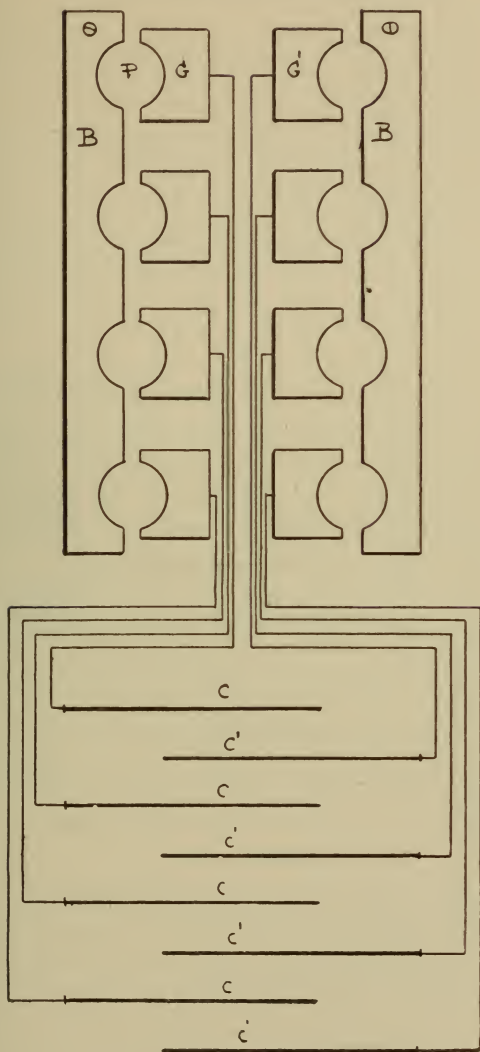


FIG. 20.

The tin-foil sheets are connected to brass blocks  $G G$  in such proportion of the total number in the condenser as desired.

By inserting taper brass plugs in holes between the brass strips and blocks as at  $P$  various combinations may be made.

A standard adjustable condenser is arranged so that the pairs of foil sheets may be connected in multiple as above, or in series.

**Keys.** In electrical testing various kinds of switches or keys are used; for opening or closing a circuit, for short circuiting, for ground connection and for reversing the direction of current flow.

The insulated parts are made of hard rubber, contacts being equipped with platinum.

In order to ensure the greatest possible insulation, the hard rubber pillars are often encircled by grooves.

This decreases the leakage from dampness as it increases the distance between the conductor supported and the table, measuring up the surface of the pillar.

**Reversing Key.** A reversing key, Fig. 21, is used to reverse the direction of current flowing into the galvanometer. Two spring brass levers  $A B$  provided with hard rubber knobs are connected by means of binding posts to the galvanometer  $G$ . A brass strip  $O$  carrying platinum con-

tacts bridges the levers and a similar brass strip  $U$  passes under them.

The battery is connected as shown, one terminal to the lower strip and the other terminal to the upper strip.

When both  $A B$  are up they make contact with  $O$ , and form a short circuit to the galvanometer  $G$ , and likewise when both levers are held down on strip  $U$ .

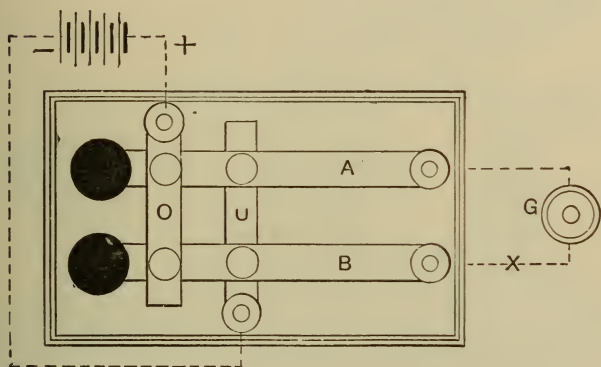


FIG. 21.

But if one lever  $A$ , for example, be pressed down the negative terminal of the battery is connected to  $A$  and the positive terminal to  $B$  and thence to the galvanometer.

On the other hand, if  $B$  only is pressed down the current to  $G$  is reversed because  $B$  is now connected to the negative terminal of the battery and  $A$  to the positive.

This key should not be so connected that the

platinum contacts form part of a circuit, the resistance of which is being measured. The contact resistance will vary as it is not possible to hold a spring key down with an unvarying pressure.

It will be seen that under no circumstances should the battery be connected to the terminals

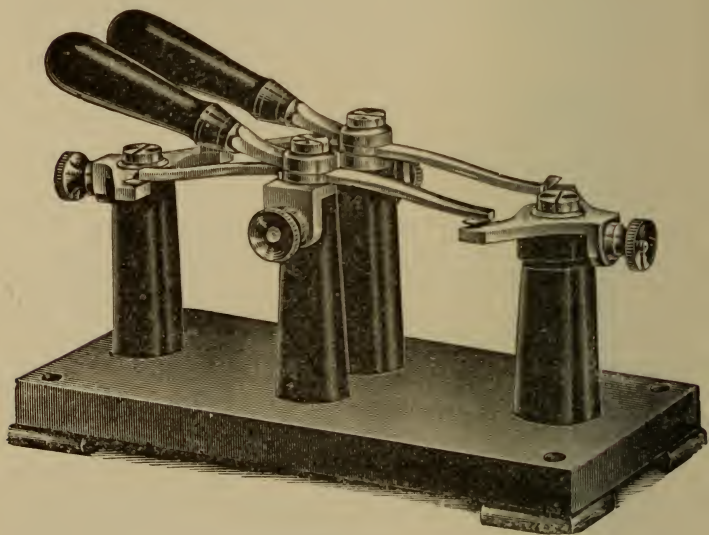


FIG. 22.

at the end of *A* and *B*, a short circuit of the battery would result.

The Rymer Jones reversing key shown in Fig. 22 makes a rubbing or wiping contact. The levers moved by the hard rubber handles are equipped with large contacts of platinum.

The contacts on which these levers work are also faced with platinum.

A rubbing contact of this nature ensures but a nominal resistance. In fact, it can be neglected in ordinary operations.

Keys of this style of construction are always preferable to those with striking contacts.

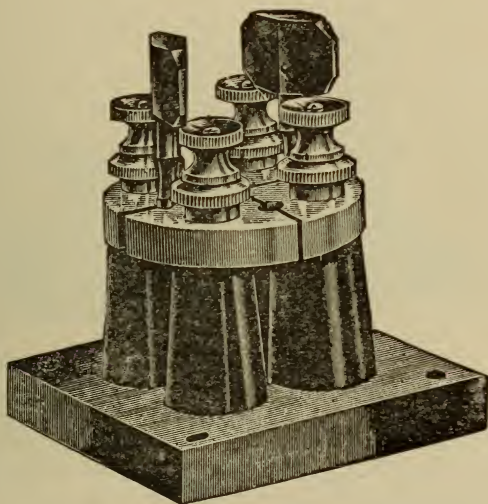


FIG. 23.

**Commutator.** A form of reversing switch or commutator is shown in Fig. 23. By changing the plugs into different holes, circuits connected to the commutator may be reversed, put to earth, or short circuited.

The brass pieces are mounted on hard rubber pillars to increase the insulating distance from each other and from the base.

**Discharge Key.** A discharge key of the Kempe pattern, Fig. 24, has two triggers controlled by buttons. One button is marked "insulate," the other "discharge."

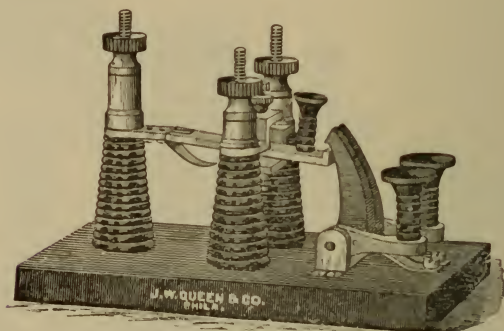


FIG. 24.

There are three binding posts, one connected to a movable lever operated by a button, one to a contact underneath this lever, and one to a contact over this lever.

When the lever is up, it presses against the upper contact completing a circuit connected to the lever binding post and top contact binding post.

When the lever is down, it presses against the lower contact; the circuit is now through the lever and lower contacts and their respective binding posts.

But in certain tests it becomes necessary to leave open the circuit connected to the lever.

The key provides for this in its second operation as follows:

Depress lever all the way down and it locks under a trigger controlled by the "insulate" button. Lower contact and lever are together. Press "insulate" button and lever flies up. But not all the way, it is caught and held in mid-air by the trigger attached to the "discharge" button. The circuit attached to the lever is thus broken.

Third, press "discharge" button and lever being released rises and rests against top contact.

**The Standard Cell.** A standard cell is a battery cell used in testing which maintains a steady e.m.f. of known value. It is used principally for comparison of other cells and to check voltmeters.

A standard cell is not required to give a large current, in actual work the current flow is kept as low as possible.

A standard cell has a thermometer included in the case as a small correction must be made for changes of temperature.

For tests not requiring extreme accuracy, the Daniel or copper sulphate cell may be used. Its e.m.f. is so near one volt as to be usable as such. A number of Daniel cells carefully set up and connected in series may be measured as to e.m.f. and the reading used for tests.

But for accurate work the Clark or the Weston cell is necessary.

The Clark cell has a positive element of mercury and a negative element of zinc sulphate and mercurous sulphate. Platinum electrodes form the connections in these elements. The e.m.f. at 15° C. is 1.434 volts.



FIG. 25,

The Weston cell, Fig. 25, has a positive element of mercury also, but the negative element is cadmium amalgam in a saturated solution of cadmium sulphate. Its e.m.f. is 1.019 volts.

The actual construction of standard cells may be found in any of the large works on testing.

## CHAPTER IV.

### VOLTMETERS AND AMMETERS.

**The Voltmeter.** A voltmeter is merely a galvanometer of high resistance connected across two conductors of opposite polarity.

The resistance of the voltmeter is extremely high in comparison with that of the conductors, and but a minute current flows through it.

As this resistance is fixed the only way to vary the amount of current flow is to vary the e.m.f.

An increased e.m.f. will increase the current flow and likewise a decrease of one will produce a decrease of the other.

And these current variations producing corresponding deflections of the needle, the deflections show actually the changes of e.m.f.

The scale divisions are calibrated or given a value in volts either by using e.m.fs. of known value, or by means of a standard voltmeter.

Voltmeters are connected across the circuit as in Fig. 26.

**The Series Ammeter.** There are two classes of ammeters, the series and the shunt.

In the former the *entire current* to be measured passes through the coils of the instrument, Fig. 27, and its changes of value directly affect the needle as in the simple galvanometer. Changes of e.m.f. will therefore not affect the ammeter directly but only in that they vary the current flowing in the circuit in which the ammeter is connected.

Series ammeters are unwieldy for large currents as will readily be seen, for the coils must be large enough to carry all the current of the circuit. They are therefore almost entirely displaced by the shunt ammeters.

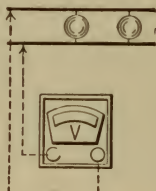


FIG. 26.

**The Shunt Ammeter.** The shunt ammeter is really a voltmeter calibrated to read in amperes and dependent upon the changes of e.m.f. in a portion of the circuit.

The current in a circuit of given resistance is controlled by the e.m.f. at its terminals.

Ohms law teaches that the current or  $I$  equals the e.m.f. or  $E$  divided by the resistance or  $R$ , as

a formula  $I = \frac{E}{R}$ .

If then there is an increased current flow in a circuit it must be due to an increased e.m.f. unless the resistance is changed.

By taking a portion of the circuit and connecting a voltmeter across it, the variations of e.m.f. causing the current flow will be indicated.

In the shunt ammeter, Fig. 28, a German silver shunt  $S$  or one made of a special alloy is connected in series with the main circuit  $A B$ .

A low reading voltmeter  $A$  is connected to the opposite ends of the shunt.

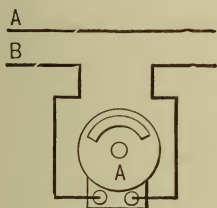


FIG. 27.

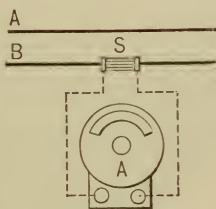


FIG. 28.

Variations of e.m.f. across the terminals of  $S$  will affect  $A$ , which is calibrated in amperes by comparison with a standard or by calculation.

**The Weston Voltmeter.** The principle of the Weston voltmeter or ammeter for direct current is that of the D'Arsonval galvanometer. The moving coil is mounted on pivots between jeweled centres instead of being suspended from wires or threads. This mounting permits of portability and compactness.

The construction of the moving system and magnet pole pieces is shown in Fig. 29.

The portable type of Weston voltmeter and ammeter is shown in Fig. 30.

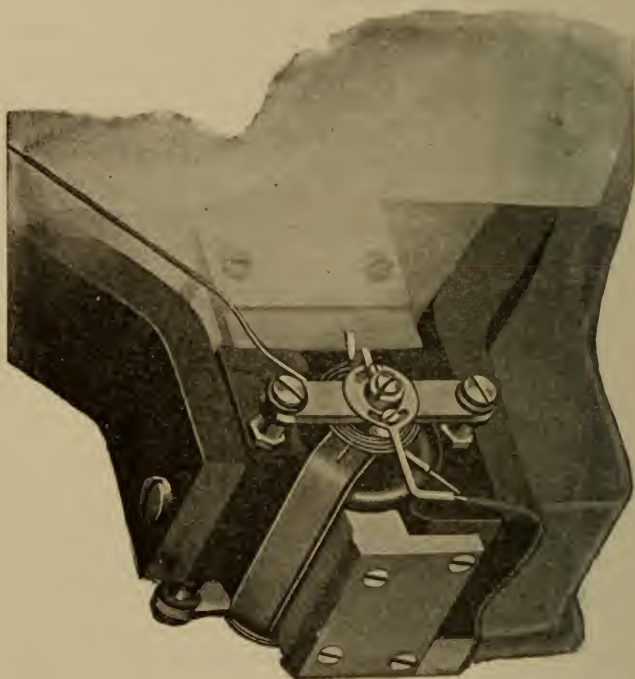


FIG. 29.

In the portable instruments the data of resistance, etc., will be found printed on the inside of the lid. Care should be taken not to interchange

the case lids, each instrument bears a serial number.

The laboratory type, Fig. 31, has a very large scale of peculiar design, Fig. 32, which admits of readings being made to a fraction of one degree of deflection.

Types of Weston switchboard instruments are shown in Figs. 33 and 34, the latter being made to fit flush with the face of a switchboard.



FIG. 30.

Figs. 35 and 36 show forms which have transparent dials illuminated from behind.

Instruments of this pattern are often mounted on a swinging arm that they may be read from various parts of the room.

A black disc controlled by a button in the middle of the case front, is set to a determined point.

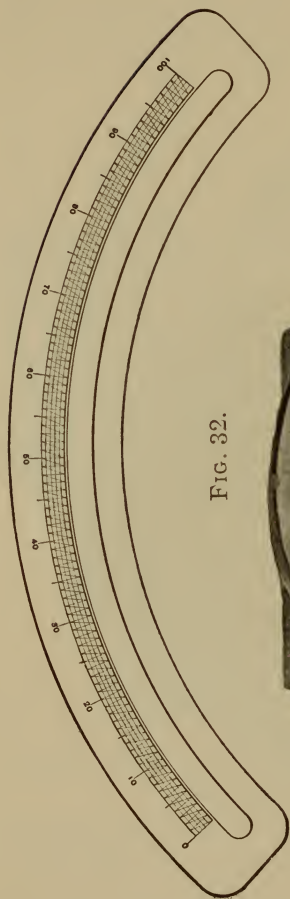


FIG. 32.



FIG. 31.

The pointer is then more readily located as to its proximity to this disc when viewed from a distance.

**Sensibility.** In the Weston direct current instruments of the portable or the Type *B* form, a resistance of about 100 ohms per volt is added.

In the other types of switchboard voltmeters the resistance is usually about 65 ohms per volt.



FIG. 33.

In case the exact resistance is not marked, it can be obtained from the makers by quoting the serial number of the particular voltmeter.

As the figures are needed in testing work, they should always be recorded.

The sensibility of a Weston instrument type B or of the portable form is about 10,000 ohms. One

scale division of deflection represents one volt through 10,000 ohms if 100 divisions equal one volt through 100 ohms.

The current used will equal the voltage indicated divided by the resistance of the instrument. For example, in a 150 volt voltmeter of 15,000 ohms,  $\frac{150}{15000} = \frac{1}{100}$  ampere for full scale deflec-



FIG. 34.

tion. One scale division here representing one volt would equal  $\frac{1}{15000}$  of an ampere.

**Switchboard Type.** The energy necessary to operate the Weston switchboard type does not exceed .05 of one per cent. of the total energy being measured.



FIG. 35.

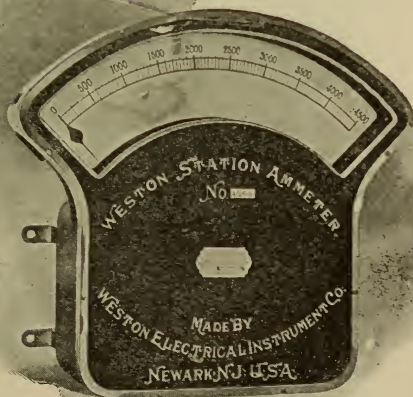


FIG. 36.

As an example of close reading, a change of 1 ampere may be detected on an instrument reading to 1200 amperes at any point in the scale.

Most switchboard instruments are calibrated for a temperature of 90° F., the error amounts to one per cent. for a change of 10° F. above or below 90°.

The resistance of the coils will be increased by a

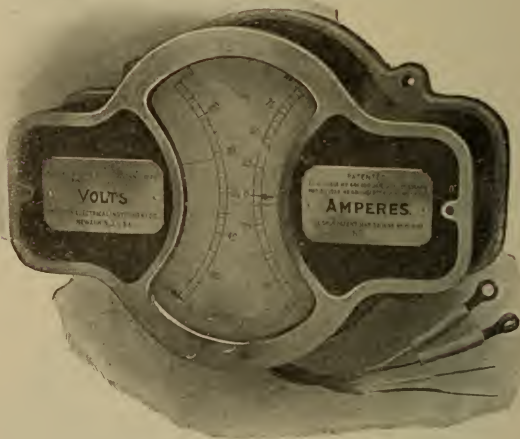


FIG. 37.

rise and decreased by a fall of temperature. The instrument therefore reads lower for an increase of temperature than the actual e.m.f. and vice versa.

**Duplex Instruments.** Most of these instruments, Fig. 37, consist of a voltmeter and an ammeter combined in one case.

But if desired two voltmeters or two ammeters may be so combined.

They are most suitable for automobile and motor switchboard work, being constructed to stand a maximum of vibration.

In connecting up automobile instruments where the wires run under the mat, some precaution must be taken against injury to the wire. The customary slipshod manner of pulling a flexible wire beneath the mat where it is forever being abraded, is to be condemned.

No instrument will indicate correctly with poor connections and this is particularly true of shunt ammeters.

Any change in resistance of the wires between shunt and instrument will affect the readings.

**Potential Indicators.** These instruments are so constructed as to give large indications for slight changes of current or e.m.f.

In order to keep the scale within limits, the pointer does not move until the e.m.f. (for example) is near the average. In Fig. 38 is an illustrative scale for an e.m.f. of 500 volts.

The index or pointer commences to move as soon as the e.m.f. increases above 400, reading e.m.f. on lower scale.

The upper scale with central zero shows the number of volts above or below 500 as it will be seen that adding the upper left scale reading and that on the lower left scale directly underneath it, the

total will be 500. And subtracting the upper reading from the lower reading on the right scale also gives 500.

**Differential Voltmeters.** Differential voltmeters have a central zero and are used in connection with two independent sources of e.m.f.

In the case of two generators which are to be run in parallel, the generators are adjusted until the needle stands at zero, when the e.m.fs. of both

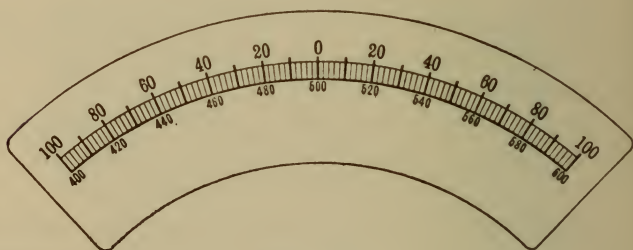


FIG. 38.

are equal. The needle points towards the side of higher e.m.f.

When the two generators are being operated, the readings on either side must not be taken to represent the e.m.f. of that particular generator. The readings indicate the difference between the generators.

**Double Scale Instruments.** Indicating instruments are provided with double scales so that a greater range of measurement is possible.

For example, the upper scale might read from 0 to 150 volts and the lower scale from 0 to 15 volts. In this case as the instruments are all direct reading with deflections proportional to the current, the resistance put in circuit for the higher reading would be ten times that for the lower.

There are generally two marked binding posts on one side and one on the other. Care must be taken to connect to the correct posts. In an instrument at hand, the same scale reading to 6 volts has three readings. The 6 volt total scale has 521.6 ohms in circuit with the coil, the 60 volt = 5215 ohms and the 240 volt = 20869 ohms.

A simple calculation will show that all these resistances are almost exactly proportional to the total scale readings.

**Multipliers.** Multipliers for increasing the readings of voltmeters are largely used. They are resistance coils in portable cases, Fig. 39, and are put in series with the voltmeter.

Multipliers must be adjusted for each particular instrument as the resistance coil must be a multiple of the voltmeter resistance. A multiplier with a value of 10, for instance, used with a 6 volt voltmeter of 521 ohms would measure about 5215 ohms; one with a value of 40 would equal about 20,860 ohms. The multiplier by 10 would give a total scale value of 60 and the multiplier by 40, a total scale value of 240 volts to the 6 volt instrument.

The value of such an apparatus in practical work is very great. It does away with the necessity of having a number of voltmeters of different ranges.



FIG. 39.

**Millivolt and Milliampere Instruments.** The prefix milli means one thousandth, a millivolt is an e.m.f. of one thousandth of a volt, a milampere or milliampere, one thousandth of an ampere.

Instruments of which the total scale reading is about one volt or one ampere, and those in which each scale division represents one thousandth of a unit, are millivoltmeters or milammeters respectively.

Such instruments are of the utmost service in measuring low resistances, temperature changes,

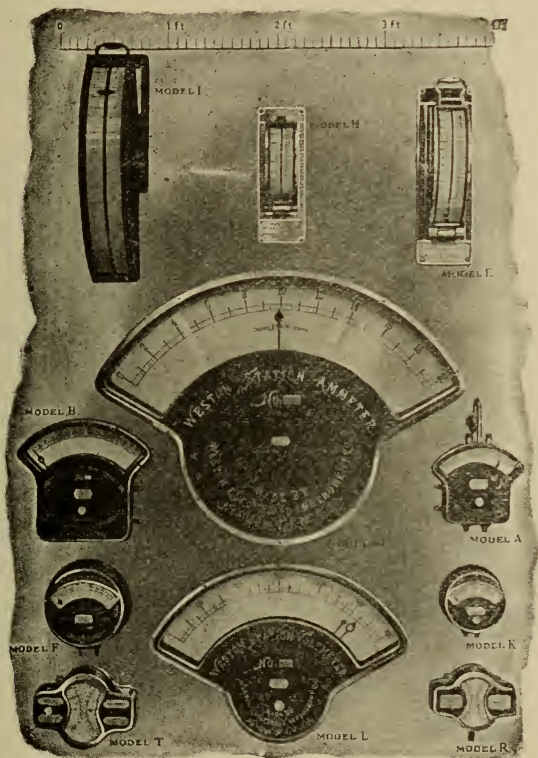


FIG. 40.

etc., and their use will be described in the chapter on testing.

**Relative Sizes.** Fig. 40 embodies the relative sizes and styles of Weston instruments with their style letters.

**Hot Wire Instruments.** Voltmeters and ammeters indicating from the expansion and contraction of wires carrying current were first represented by the Cardew types.

A fine wire was run over a pulley carrying an index, one end of the wire being rigidly attached and the other end held taut by a spring. When current passed along this wire, the latter expanded, the slack was taken up by the spring and the pulley rotated. Upon cessation of the current, the wire cooled and contracted, the pulley reversed and its pointer returned to zero.

Instruments made on this principle could be used on either direct or alternating currents.

But they possessed the disadvantages of burning out on accidental overloads, of the wire becoming stretched or otherwise distorted, of consuming a larger current than the other types which would render them less accurate, of requiring a long case and an undesirable position of that case and many minor defects.

**The Whitney Hot Wire Instruments.** The Whitney type of hot wire instruments represents the practical solution of the before mentioned defects.

The mechanism is shown in diagram in Fig. 41.

A wire *A B* of high resistance, low temperature

coefficient and non-oxidizable metal is secured at one end to a plate *C*. It runs over a pulley *D* mounted on a shaft *E*, and its free end is attached to the other end of *C*, but is insulated therefrom. A spring *F* keeps the wire taut and takes up any slack imparted to the wire by the passage of current.

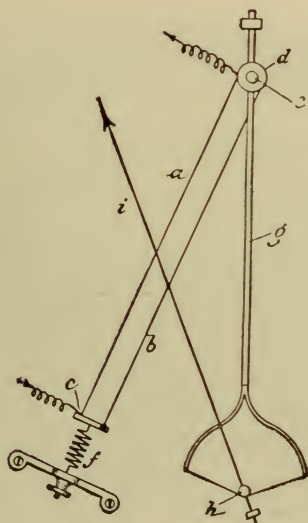


FIG. 41.

Current only flows in the portion of wire *A* between *C* and the pulley *D* where the coiled wire connection is shown.

When *A* is heated by current flow it expands, *F* taking up the slack, pulls *A* round *D*, and rotates *D* and *E*.

If a pointer were directly attached to shaft *E* it would indicate on a scale the movement of *D* and *E*.

But a magnifying device is employed. *G* is a forked rod rigidly attached to *E*, at its lower end a silk fibre fastened between the forks passes around a pulley *H* which carries the pointer.

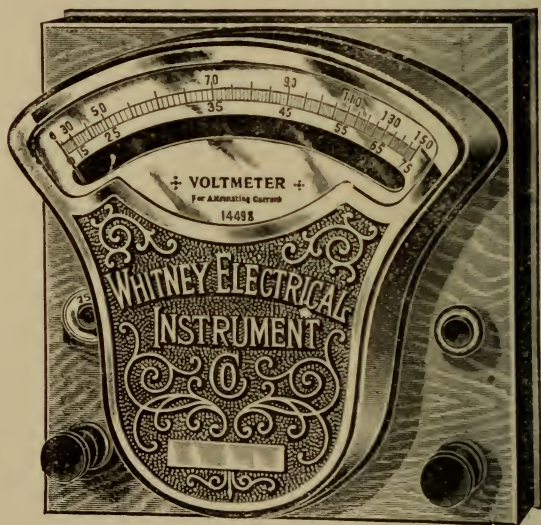


FIG. 42.

The rotating of *E* therefore moves *G* and the silk fibre rotates *H* and the pointer, thus magnifying the movement of *G*.

Any temperature variations will affect *A B* equally, it is therefore self-compensating.

The tension of  $F$  being slight, wire  $AB$  is not under a heavy strain, it more nearly returns to its original length after current ceases.

The instrument, however, can be adjusted to zero very readily if it should become necessary.

A portable instrument is shown in Fig. 42 and

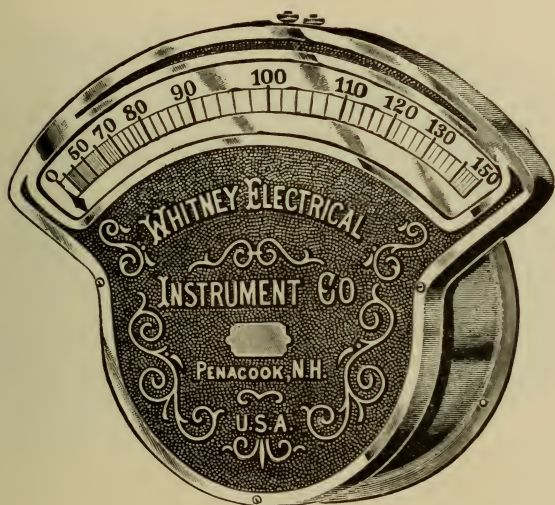


FIG. 43.

a switchboard instrument in Fig. 43, many other types being manufactured.

For direct current work only an electro-magnetic system is used. The ammeters of this type have a uniform drop of .05 volt. Shunts are thus interchangeable.

**Ammeter Shunts.** The ammeter shunts used with Weston switchboard instruments are shown in Fig. 44.

The shunt itself is made of one or more sheets of alloy resembling German silver in appearance. The ends of these sheets are fastened into brass or copper blocks.

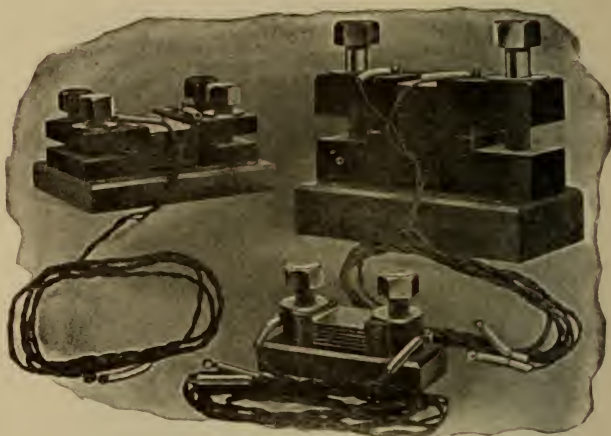


FIG. 44.

Large clamping screws are provided for attachment of the shunt to the bus-bar, which latter are inserted in the large slots at each end of the shunt. The small screws are for the instrument cords.

The Whitney shunt, Fig. 45, is made of a solid block of metal slotted as shown so as to give the resistance of a long bar.

In all cases the connections to shunts must be

as perfect as possible. Poor contact causes heating if at the bus-bar connections and thereby incorrect indicating at the instrument terminals.

The shunt cords must also be properly clamped or incorrect readings will result.

The importance of these precautions will be thoroughly appreciated when the principle of the shunt ammeter is considered.

For the same reason the cords must on no account be tampered with. If too long loop them up and



FIG. 45.

bind the looped part if desired with tape. A shortened cord would increase reading of instruments as it lowers the resistance in series with the ammeter. And a poor connection would decrease readings on account of its resistance.

Too little attention is often given to these points by those in charge of a plant, an instrument cannot give correct readings if improperly connected.

Shunts for portable instruments are included in the base of the instrument.

For extreme adaptability, a millivoltmeter can

be equipped with a set of shunts so that the same instrument will measure from a fraction of an ampere to many thousand amperes.

**Other Types of Instruments.** Voltmeters and ammeters are constructed on principles other than that of the D'Arsonval galvanometer, or the stretching of a hot wire.

It is unquestioned that the D'Arsonval system is the only correct one for instruments to be used *on direct current circuits only*. But owing to patent rights it has been necessary for manufacturers to seek other methods of construction.

The result is that while no new principles are used, those less suitable than the D'Arsonval have been perfected with such ingenuity as to make most excellent substitutes.

It is also unquestioned that when the D'Arsonval patent expires it will be the only principle that will survive. That is, unless the electrostatic instruments are much improved and made practicable for measurements of low potentials. The above refers more to laboratory and portable instruments than to those designed for switch-board work.

The solenoid type of Fig. 46 has a pivoted soft iron armature curved to enter a solenoid. Current being passed through the wire of the solenoid causes the armature to be attracted more or less against a restraining force. The latter may be gravity or springs.

A pointer attached to the armature indicates on a dial.

A simpler solenoidal instrument is shown in Fig. 47 but acts in the same manner.

A type of magnetic vane instrument, Fig. 48, depends upon the repulsion between two pieces of iron in the same field. One is stationary inside a coil of wire, the other is movable on an axis.

As both lie in the coil the same way they both



FIG. 46.

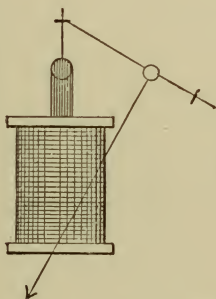


FIG. 47.

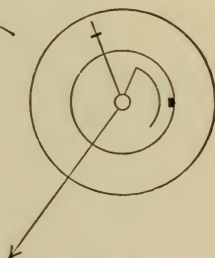


FIG. 48.

have *N* poles or *S* poles at the same end. As similar magnetic poles repel each other the stronger these iron pieces become magnetized the farther apart they move.

The galvanometer principle, Fig. 49, is used where a short magnet is pivoted inside a coil large enough to give a fairly uniform field.

In Fig. 50 the attraction is between two curved armatures and the two poles of an electro magnet.

This is purely magnetic attraction and is counter-balanced by the force of gravity, a spring, or an adjustable weight.

The heating effects of current are used in Fig. 51 where a coil of wire surrounds a thermometer bulb. By the rise of the mercury the heat and thereby the current flow is measured.

**Westinghouse Type K.** The Westinghouse type K voltmeters and ammeters are made on the prin-

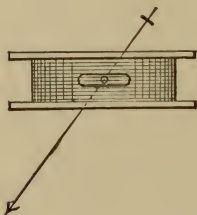


FIG. 49.

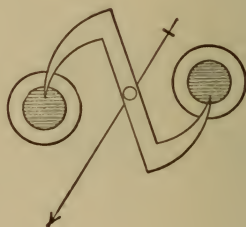


FIG. 50.



FIG. 51.

ciple illustrated in Fig. 47, the lower end of the armature working in a glass tube filled with oil. This steadies the moving system and renders it dead beat. The armature is not rigidly attached to the pointer shaft, but has a flexible connection of silk. The shaft itself takes the form of a scale beam working on knife edges. The bearings for the knife edges are so constructed that the leverage

becomes uniform and the divisions remarkably even throughout the scale.

Being purely electromagnetic attracting instruments they can be used on circuits of either direct or alternating current.

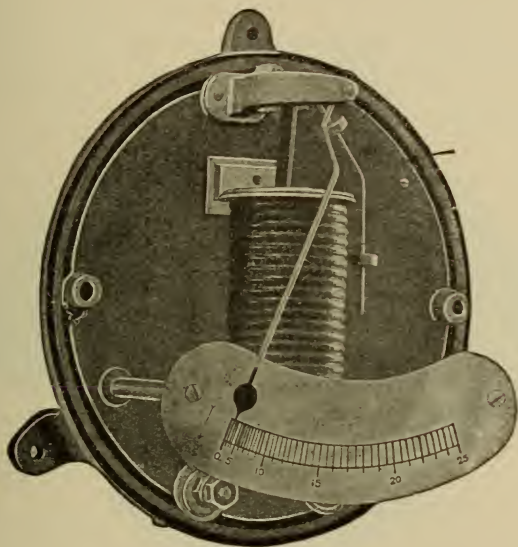


FIG. 52.

**G. E. Potential Indicators.** A simple form of voltmeter and also of ammeter made by the General Electric Company is illustrated in Fig. 52. The movement of the armature in the solenoid is controlled by gravity, means of adjustment being by means of the balance weights shown in the illus-

tration. The ammeters of this type are series connected not shunted.

**Thomson Inclined Coil Meter.** The Thomson inclined coil ammeter is adapted for use on circuits of alternating current.

The instrument is constructed on the magnetic vane principle in which an iron vane or wing strives to turn itself parallel with the axis of a coil carrying the current to be measured.



FIG. 53.

The name comes from the peculiar position of the coil. Instead of lying flat on the base its axis is inclined.

A soft iron vane is mounted obliquely on a shaft which latter is held in a vertical position and controlled by springs.

The shaft also carries a pointer moving over a graduated dial.

When current is sent through the coil the vane turns against the springs so as to set itself parallel with the axis of the coil. The inclined position of the latter and the peculiar shape of the vane give a more evenly divided scale than is obtained in most other instruments of this class.



FIG. 54.

The voltmeter has a similarly placed stationary coil, but in place of the iron vane is equipped with a moving coil in series with the other coil.

The pointer is carried by the moving coil system which is controlled by springs.

This type of instrument can also be used on direct current circuits.

On alternating current circuits they work equally well for all frequencies of alternations.

The mechanism of the pocket ammeter is shown

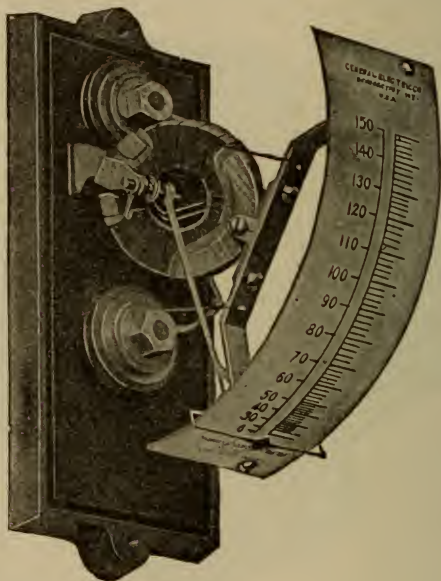


FIG. 55.

in Fig. 53, the switchboard ammeter in Fig. 54, and the switchboard "edgewise" voltmeter with iron vane moving system in Fig. 55. The ammeters below 500 amperes total scale are series, the entire current passing through the instrument.

Although the above type may be used on direct

current circuits, the manufacturers recommend the Thomson astatic form for such circuits.

**The Thomson Astatic Voltmeter.** The mechanism is illustrated in Fig. 56, the same principle being used in the astatic ammeter which, however, is a shunt instrument.

The pointer shaft carries a coil through which

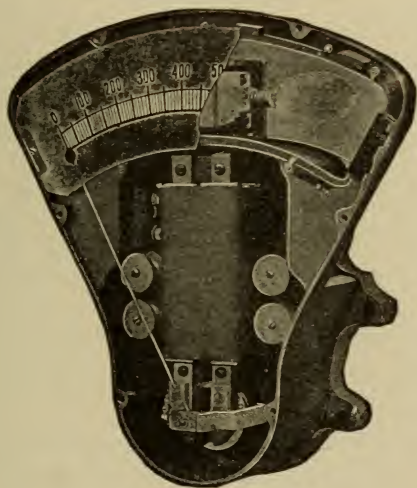


FIG. 56.

passes the current to be measured and also two pieces of magnetic metal.

The field magnets are electromagnetic, not permanent, as in the D'Arsonval instruments.

An astatically arranged magnetic field is mount-

ed perpendicularly to the shaft and restrains the pieces mounted on the shaft.

Deflections of the coil due to current flowing through it are opposed by the magnetic field acting on the pieces of metal which are carried by the same shaft. There are thus no restraining springs, current to the moving coil being conveyed by torsionless spirals of silver wire. The illustration shows the illuminated dial voltmeter one of the miniature lamps for lighting the dial being visible. The resistance spools are also shown, two on each side of the electromagnet coils.

The dead beat or damping effect is produced by an aluminum disc which moves in the field of an electromagnet.

Thomson astatic instruments can be provided with polarity indicators, a red disc showing in the scale card when polarity is reversed.

**The Wattmeter.** The most efficient forms of wattmeters are constructed on the electro-dynamo-meter principle.

If two coils of wire are constructed, one stationary and the other free to turn inside it, the movable one will tend to turn until its coils are parallel with the stationary one when current is applied to both.

In the wattmeter, the stationary coil is of heavy wire and the main current flows through it. The movable coil is of fine wire in shunt across the circuit.

Changes of current strength in the main circuit thus affect one coil, and changes of e.m.f. the other.

As the watt is the product of the e.m.f. multiplied by the current, the index attached to the movable coil is influenced by the watts in the circuit.

This type of instrument can be used on direct or alternating current lines.

**Keystone Instruments.** The Keystone voltmeters at present are made either on the electro-dynamometer principle just described, or are electromagnetic.

In both types they can be calibrated to read on alternating or direct current circuits.

The makers recommend the electro-dynamometer type for direct current voltmeters, but not for ammeters. The connections between the moving coil and the circuit would have to be so large as to interpose friction.

The ammeters are electromagnetic and are for series connection. The scales, however, are remarkably even.

In the electro-dynamometer type, there are two springs to control the moving coil.

Over the first part of the scale a spiral spring opposes the movement, while a "pendulum" spring assists it. Further on, the latter spring assists the spiral spring, thus opposing the coil movement when the deflecting force is greatest.

This ensures greater evenness in the scale divisions throughout the range.

**Queen Instruments.** The Queen Wirt voltmeters and ammeters can be used on circuits of either direct or alternating current.

They are electromagnetic, the principle being that in which an iron armature tends to move into the strongest part of a magnetic field.

A tube of soft iron lies parallel with the axis of a coil of wire through which current passes. Being mounted away from the true centre of the coil it moves towards that centre where the field is strongest.

The electromagnetic principle does not allow of absolutely even scale divisions, but those in the middle of the scale are fairly uniform.

Although for use on both circuits, the scales must be graduated for either one or the other.

For alternating current the divisions are most uniform.

In the Queen portable form, an upper scale can be graduated for direct current and a lower scale for alternating current.

**Electro-Static Instruments.** A type of instrument much used on circuits of extremely high e.m.f. is made on the principle that two oppositely charged plates will attract each other.

A movable plate of aluminum is suspended between fixed plates of similar metal. The movable plate carries an index and is controlled either by gravity or springs, generally the former.

The fixed plates are connected to **one side** of

the circuit and the movable plate to the other side.

The instrument in fact is a form of condenser.

When a source of high e.m.f. is connected as above to the instrument the mutual attraction between the two series of plates causes the movable plate to swing and its index to indicate on a scale.

As the attractive force depends upon the *square* of the e.m.f., the scale divisions are not uniform.

Such instruments consume no current.

The chief advantage of the electrostatic voltmeter is that it can be directly connected to a circuit of extremely high potential.

In the case of alternating current circuits with voltages up in the tens of thousands it becomes necessary with other types of voltmeters to reduce the voltage before applying it to the instrument.

This is done by means of a "potential transformer," which is a small transformer especially constructed to reduce the high voltage to a lower one suitable to the instrument in use.

The voltmeter is thus not directly connected to the circuit but is inductively connected.

**Reading Instruments—Parallax.** One source of error in reading voltmeters and ammeters lies in the fact that the pointer or index does not touch the scale.

If the eye is not directly in front of the index a reading to one side or the other is liable to be made.

Where an index stands as much as a quarter of an inch away from the scale, a large error in reading might result.

This error is called parallax and is prevented in portable instruments for accurate testing by the following device:

The index is made thin and flat, lying edgewise towards the eye. A strip of mirror is placed be-

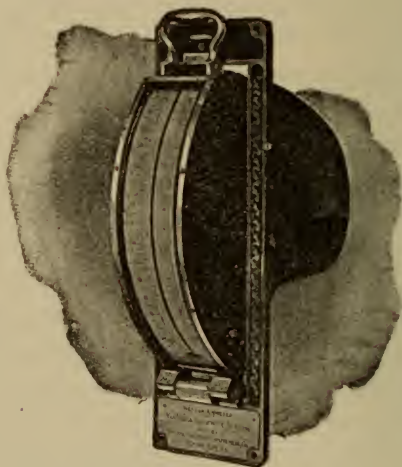


FIG. 57.

neath the index. The reading is made when by looking down on index and mirror, the index hides its own reflection.

Some switchboard instruments are made for edgewise reading, that is, the scale is at right angles to the base, Fig. 57. The scale is curved and the index is bent so as to follow it.

In this type, the error of parallax is likely to be greater than with the ordinary type.

**Care of Instruments.** Electrical measuring instruments must be handled with at least ordinary care.

Although made as air tight as possible, dampness and excessive heat should not be permitted to attack them.

Violent swinging of a pointer through excessive current is liable to do more than bend the pointer.

Even if it does not permanently injure the instrument it does it no good. This is more likely to happen in using a double scale instrument, or by reversing the connections.

When taking measurements the instrument should not be set down on a generator or its bed plate.

And a direct current voltmeter should not be tried on an alternating current circuit.

The glass front should never be rubbed before taking a reading, or the pointer will be influenced by so-called static currents.

They may be dissipated by touching the finger to the middle of the cover, but are best omitted.

In the case of two or more compound wound generators being connected together to run in multiple, a so-called equalizer is used. This is a bus-bar or cable connecting together a point on each dynamo between the series field winding and its brush connection.

The ammeter or its shunt is not to be connected in series with the lead from the series field or equalizer side, but in that lead which runs directly from the brush to the main switch or bus-bar. Otherwise current flowing in the equalizer bus would not be indicated.

Ammeters for storage battery circuits are made with a central zero as the deflections of charge or discharge are in different directions.

This is of course only true of that class of instrument in which the direction of deflection depends upon the direction of current flow, that is, polarized instruments.

If a polarized instrument without a central zero be used for storage battery work, a reversing switch becomes necessary between the shunt and the ammeter.

This is but a makeshift and is by no means to be recommended.

Any instrument built to be used only in a vertical position must not be used when laid horizontally and vice versa. Readings may be made, but they are liable to be inaccurate, owing to friction or gravity.

## CHAPTER V.

### THE WHEATSTONE BRIDGE.

**The Wheatstone Bridge.** In Fig. 58 is shown the lozenge or kite diagram of the Wheatstone bridge.

$A$   $B$  are two adjustable resistances. These form the proportional arms of the bridge.

$R$  is an adjustable resistance or rheostat,  $G$  a galvanometer,  $B$  the battery and  $K$   $K$  keys closing the battery or galvanometer circuits respectively.  $x$  is a resistance which it is desired to measure.

If the battery key be closed, current will divide between  $A$  and  $B$  and flow through  $R$  and  $x$  back to battery  $B$ .

If  $A$   $B$ ,  $R$  and  $x$  are equal, the current will divide equally down each side of the lozenge. Even if the galvanometer key be closed, no current will flow into  $G$ .

If  $x$  be greater in resistance than  $R$ , part of the current through  $B$  will travel through  $G$  and thence through  $R$  in accordance with the law of shunts. The galvanometer needle is thus deflected. But by adjusting  $R$  to agree with  $x$  the two paths  $R$  and  $x$  being equal no current flows through  $G$ .

Should  $R$  be greater than  $x$ , current flows through

$A$  and through  $x$  by way of the galvanometer, and the needle is deflected, but in the opposite direction to the former case.

The Wheatstone bridge is based on the fact that no current flows between points of equal potential.

Consider the two sides of the bridge  $AR$  and  $Bx$  as two wires of equal resistance per unit length in multiple between the battery terminals.

The drop of e.m.f. will be the same in each wire for the same length.

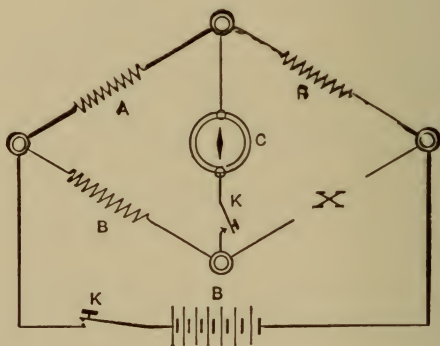


FIG. 58.

If the galvanometer be connected to a point in each wire equally distant from either end, say the middle of each, no current will flow in the galvanometer.

The effect is the same as if both terminals of the galvanometer were placed on the same spot in a single wire carrying current.

Shift one galvanometer connection, this has the

same effect as separating the two contacts on a single wire.

The galvanometer in the latter case will be in shunt with the piece of wire included between its contacts. As the points are at a different potential, the galvanometer will show the potential in that piece of the circuit.

The same applies to the double wires. When the bridge galvanometer is connected as in the figure but assuming  $ARB$  and  $x$  as equal, the galvanometer is connected between two points of the same potential.

If  $x$  be increased in resistance over that of  $R$  it would be the same as increasing the length of the wire  $x$ .

In the latter case the galvanometer contact could be shifted along the  $x$  wire until it again stood at the middle, when the galvanometer would remain undeflected.

In the bridge the resistance  $R$  would be adjusted until it was equal to  $x$ ,  $A$  being in the same proportion to  $R$  as  $B$  was to  $x$ , the galvanometer would be at the points of equal potential. Of course  $B$  could be changed but  $R$  is the adjustable resistance.

If  $A$  is to  $B$  as  $R$  is to  $x$ , then  $x$  will be the same as  $B$  multiplied by  $R$  and divided by  $A$ .

This is just simple proportion in arithmetic as the following example shows. In simple proportion, to get the fourth term or answer, the second and third are multiplied together and divided by the first.

For example, if  $1 = 2$  what will 4 equal?

$$1 : 2 :: 4 : x \text{ or } \frac{2 \times 4}{1} = 8.$$

And in the foregoing formula, if  $A = B$  what will  $R$  equal?

$$A : B :: R : x, \text{ or } \frac{B \times R}{A} = x.$$

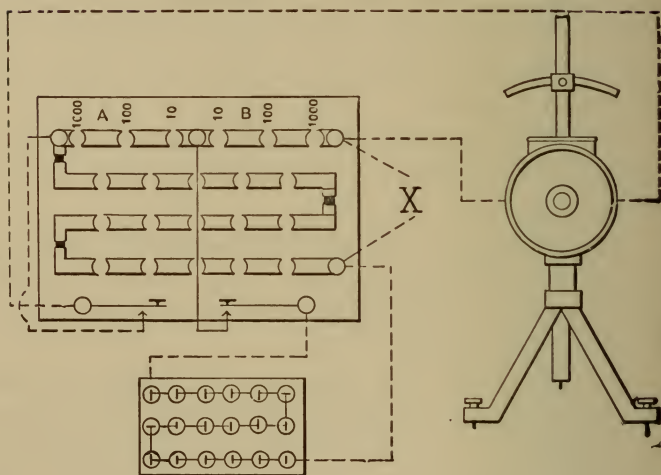


FIG. 59.

**The Post-Office Bridge.** The connection for resistance tests of the form of bridge known as the (English) Post-Office Bridge is in Fig. 59.

A tripod form of Thompson galvanometer is illustrated and an 18 cell battery but it is evident that a larger or smaller battery could be used.

And any form of galvanometer would be connected up in the same way.

The shunt is not shown, it would be connected across the galvanometer terminals. The resistance to be measured is connected at  $x$ .

The key on the left of the bridge is the battery key and should always be depressed first. The right hand key is the galvanometer key and is to be only tapped until a close balance is obtained. Otherwise were the bridge rheostat not adjusted to the measurement being made, the deflection would be violent.

Much damage to a galvanometer is done by neglecting this rule.

In a reflecting galvanometer where the mirror is suspended by a silk fibre, the latter may be broken. Replacing it is a work requiring expert knowledge and vast patience.

**Testing with the Bridge.** For illustration of the use of the bridge the one shown in the last figure will be selected.

Suppose it is desired to measure the resistance of a coil of wire. The two ends are bared of insulation, scraped clean and inserted in the binding posts as shown at  $x$ .

The other connections of the figure are already made as described. For the first test, however, it will be well to use only one cell of battery.

All plugs are in the holes in the rows of resistance coil connections.

Remove from both *A* and *B* the plugs from the 10 ohm coils.

Remove a 10 ohm coil plug from the rheostat part.

Depress the battery key and tap the galvanometer key.

The deflection is noted both as to amount and direction. Suppose it is  $60^\circ$  to the left.

Remove another plug say from 100 ohm coil and tap key again.

Deflection in same direction only  $10^\circ$ .

Remove 20 ohm plug, deflection  $5^\circ$  to right. This indicates that too much resistance has been unplugged.

Replace 20 ohm plug and remove 10 ohm plug, deflection is now  $1^\circ$  but to left.

Indicates that still too little resistance is out.

Remove 1 ohm plug; no deflection perceptible.

Then read resistance unplugged.  $10 + 100 + 10 + 1$  or 121 ohms is resistance of wire coil.

When a resistance equal to that being measured is unplugged, no deflection takes place.

It may be stated here that in these examples no actual statement of deflection due to resistance is meant. The values given are only illustrative.

It will be seen that the deflection is to one side when too much resistance is unplugged and to the other side when too little resistance is unplugged.

Most galvanometers fitted in the cases of portable testing sets are marked + and - on opposite ends of the scale.

As the battery is connected so as to send current always in the proper direction, a deflection to the + side means too much resistance and one to the - side too little resistance unplugged. Of course reversing the battery connections will reverse the value of these signs.

In the bridge of the instruments being described in this section, there are three coils in each arm, reading from left to right 1000-100-10 in *A* and 10-100-1000 in *B*.

At present only equal ones are used in each arm. For measuring low resistances the 10 ohm coils in each arm are unplugged. For high resistances, 100 ohm coils in each arm are used.

For very high resistances 1000 ohms in each arm.

The rule is to use the nearest bridge coils to the resistance being measured.

As the total resistance of the rheostat is in this case only 11,110 ohms, it is evident that by the method before pursued, no higher resistance can be measured and none lower than 1 ohm as that is the lowest coil in the rheostat.

**Proportional Arms of Bridge.** This is where the proportional arms of the bridge come in to use.

By unplugging a higher coil in the *B* side, the value of each coil in the rheostat is multiplied by the number of times the unplugged coil in *A* divides into that of *B*.

And by reversing this and unplugging higher in *A*, the rheostat coils are divided by the number of

times  $A$  is greater than  $B$ . As a memory aid— $A$  divides,  $B$  multiplies.

This gives new values to the rheostat coils and vastly extends the range of measurement.

For example, let  $A$  be 10 and  $B$  100, then  $B$  is ten times  $A$ ; *multiply* the rheostat figures by 10.

The 1 ohm coil then becomes equivalent to a 10 ohm coil and the 1000 ohm a 10,000 ohm coil, and so on.

And let  $A$  be 10 and  $B$  1000 and the rheostat is multiplied by 100, the 1 ohm coil is thus equal to 100 ohms, the 1000 ohm to 100,000 ohms.

This last setting of the arms will give a value to the rheostat of  $11,110 \times 100$  or 1,111,000 ohms.

If then the bridge arms were so set and a balance obtained at 162 ohms, the actual resistance would be  $162 \times 100$  or 16,200.

In some bridges there are 1 ohm coils, then the range will be 1000 times and  $\frac{1}{1000\text{th}}$ .

The dividing method or higher coil in  $A$  is on the same plan.

Unplug 10 ohms in  $B$  and 100 in  $A$ , then the readings will be *divided* by 10, which is the number of times 10 goes into 100. And the 1 ohm coil becomes  $\frac{1}{10}$  ohm, the 10 ohm coil now being equal to a one ohm coil.

This proportional property of the arms not only enables larger or smaller measurements to be made

than are in the rheostat, but it gives closer readings.

Take the first example, the coil of wire. Set the bridge arms  $A$  1000,  $B$  10, making a division by 100 necessary of the rheostat readings. As the first test showed 121 ohms, unplug one hundred times 121 ohms or 12,100 in the rheostat.

As the bridge now stands this only equals 121 ohms. It may be necessary to increase the battery.

Having depressed the battery key, depress the galvanometer key and there will probably be a deflection one way or the other. Suppose it is to the - side.

Unplug 10 ohms now  $\left(\frac{1}{10}\right)$  and try deflection.

Let it take 18 ohms more to get a balance or zero on the scale.

Then the rheostat will read 12,118 which divided by 100 gives 121.18 ohms, a far closer reading than with equal arms.

It is a good plan to make a number of tests of coils of known resistance, or to check up tests by trying various combinations of the arms.

It must be remembered that as the resistance of copper increases from heat, readings will vary from time to time owing to the current flowing in the wire being tested. The relation between heat and resistance will be found elsewhere in these pages.

In testing coils, electro magnets, etc., they must

not lie near the galvanometer. Where leads are necessary from the bridge to the apparatus being tested, the leads also should be tested as their added resistance would give a false value to the test.

**Formula.** A stating of the foregoing rules as formulas will be as follows:

Let  $R$  be the resistance unplugged in rheostat,  $A$  that in arm  $A$  of bridge,  $B$  that in arm  $B$  of bridge,  $x$  the unknown resistance.

Then  $A : B :: R : x$ , and  $A x = B R$ ; therefore

$$x = \frac{B R}{A}.$$

## CHAPTER VI.

### PORTABLE TESTING SETS.

#### **The Willyoung Portable Testing Set—Model K.**

A form of portable Wheatstone Bridge is shown in Fig. 60. It is furnished with a small battery in the case, and a set of working shunts.

The galvanometer is of the D'Arsonval type with a sensibility of one scale division for one volt through over two megohms.

It is not disturbed by the proximity of other electrical machinery or magnetic fields.

Full directions are furnished with each instrument. The general rules of its use are those for all forms of Wheatstone Bridges.

In testing a resistance with this instrument it is connected to binding posts *C D*, Fig. 61. The flexible battery cords are connected by their cup connectors to two adjacent studs on the battery. This cuts in one cell; if more are desired the cups are connected to include them in circuit.

The commutator plugs connect *A x* and *B R* as shown. Plugs *G a* and *B a* are inserted. Plug *V* is omitted, galvanometer switch is turned to "in"

and shunt switch put on  $I$ , that is, if the particular set is equipped with a contained shunt.

Plug all holes in the bridge arms but those corresponding to 100 ohms in each arm.

Then unplug rheostat until enough resistance is

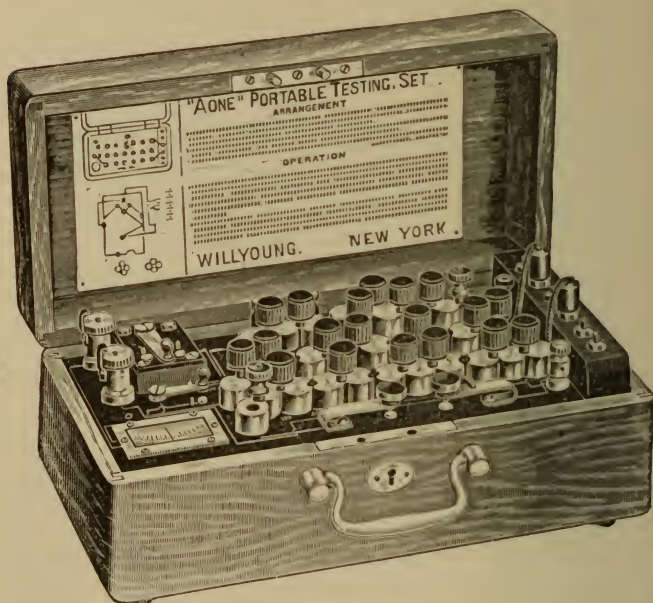


FIG. 60.

cut in circuit to equal what the resistance being measured amounts to. (When no idea is had of the latter, the galvanometer key must be tapped carefully that no undue deflection injures galvanometer).

Depress battery key and tap galvanometer key.



the rheostat can be measured. The latter runs from 1 ohm to a total of 21,110 ohms.

The working range of this set is from .001 ohm to about 500,000 ohms with the battery supplied in the case.

By using a larger battery connected at + and - at the right hand of the case, much larger readings may be made. And if a more sensitive galvanometer be connected where the shunt is, readings to a maximum of 21 megohms is claimed for this set.

But for such high resistance work as the latter, the direct deflection method will be found preferable.

**The Queen Portable Testing Set.** The Queen Acme portable testing set, Fig. 62, is adapted for all resistance measurements. There are three rows of brass blocks and plugs controlling resistance coils.

The middle row is the Bridge, the top and bottom rows, the rheostat.

In the centre of the Bridge is a split block commutator  $Rx$  which can be connected to the Bridge arms by plugs.

If the plugs are inserted in this commutator in the direction of arrow  $L$  as shown, the resistance in the rheostat is divided by the quotient obtained in dividing the higher Bridge arm by the lower.

If plugs are in direction of arrow  $H$ , multiply rheostat by quotient. For example, let rheostat

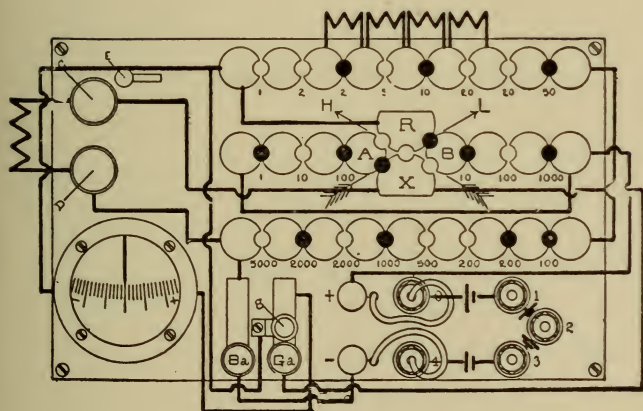
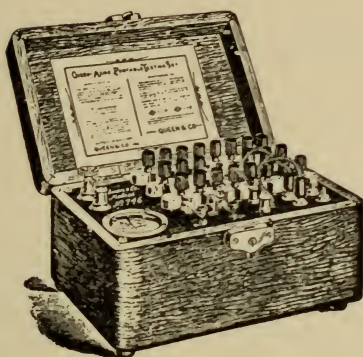


FIG. 62.

equal 100 ohms and commutator be set as in figure. 100 ohms in arm  $B$  divided by 10 ohms in arm  $B = 10$ . Divide rheostat by 10,  $\frac{100}{10} = 10$  ohms.

But let commutator be set in direction of arrow  $H$ . Then same example,  $\frac{100}{10} = 10$ , 100 ohms in rheostat  $\times 10 = 1000$  ohms.

The galvanometer scale is marked  $+$  and  $-$ . If the needle swings towards  $+$ , reduce the rheostat if to  $-$ , increase it.

The range of the Bridge arms is 1 to 1000 ohms, and the rheostat 11,100 ohms. This gives a range of testing from .001 to 11,100,000 ohms. For resistances above one megohm, however, more battery is required than will be found in the case.

**Formula.** For this Bridge, the formula for the commutator setting in direction of arrow  $L$  is  $\frac{A}{B} = \frac{x}{R}$ , and for direction  $H$ ,  $\frac{A}{B} = \frac{R}{x}$ .

The general directions for this set are similar to the regular Wheatstone Bridge tests. It is very simple and easily handled. Other adoptions of the set will be found in later pages of this book.

Table III. gives the Bridge setting for various resistance measurements. It is used in conjunction with the directions regarding the commutator before given.

TABLE III.

Showing setting of Bridge arms to measure resistances as in first column.

<i>"x" Ohms.</i>		Ohms	
		A	B
Below	1.5.....	1	1000
From	1.5 to 11.....	1	100
"	11 to 78.....	10	100
"	78 to 1,100.....	100	1000
"	1,100 to 6,100.....	100	100
"	6,100 to 110,000.....	1000	100
"	110,000 to 1,110,000.....	1000	10
"	1,110,000 to 11,110,000.....	1000	1

**Whitney Testing Set.** This portable set, Fig. 63, has 11,110 ohms in the rheostat and 1, 10, 100 and 1000 ohm coils in each arm of the Bridge.

One plug only is used in each row of the rheostat inserting the plug cuts in a resistance equal to the number marked on the block.

The battery and galvanometer keys can be controlled by one button, the battery contacts being made first. Or they can be depressed separately, as desired.

The inside connections are shown in Fig. 64.

**To Use Bridge.** Connect the terminals of the unknown resistance to the lower right hand binding posts. The terminal of the flexible cord projecting from the hard rubber top between the bridge arms should then be adjusted to one of the



FIG. 63.

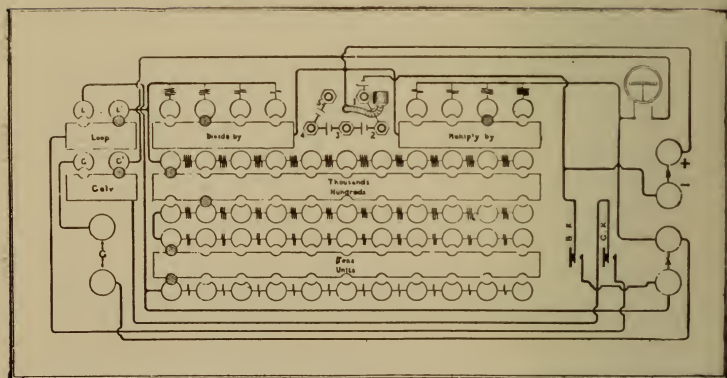


FIG. 64.

five posts, likewise so located; thus throwing in circuit from one to five cells of battery, as will be seen by the diagrammatic illustration herewith.

If more battery power is needed remove the flexible cord terminal from the post and attach the terminals of an external source of direct current to the binding posts *B B*, the positive terminal being attached to the post marked “+.”

This external e.m.f. should not exceed 15 volts.

Assuming that nothing is known of the magnitude of the resistance to be measured, insert the plug in the bridge arm lettered “multiplied by” in the gap numbered “100” and the plug in the bridge arm “divide by” in the gap numbered “100.” Place the plug in the “hundreds” row in the gap numbered “1.” The three remaining plugs numbered “0” in their respective rows. This act has inserted 100 ohms in the rheostat arm of the bridge.

Depress the combination key momentarily.

If the galvanometer needle deflects towards “-” the rheostat resistance is too small and more should be added by moving the plugs along.

If the deflection is towards “+” the rheostat resistance is too much and less is to be substituted by putting the “hundreds” plug into its “0” gap and moving the “tens” plug along.

Proceed in this manner until some combination of coil values is found where the galvanometer needle will no longer deflect when the key is depressed.

The value of the unknown resistance is then indicated by the position of the rheostat plugs.

The above applies only where the unknown resistance has a value between 1 ohm and 11,110 ohms.

If the resistance is lower than 1 ohm insert the plug in the left hand ratio arm into "10" and the right hand ratio arm plug into "100" or "1000." Balance may now be obtained as before, then

$$R \frac{\text{Multiply by}}{\text{Divide by}} = X \text{ or } \frac{B}{A} R = x.$$

For resistances higher than 11,110 ohms the plug in the left hand bridge arm must be inserted in a higher number than the plug in the right hand bridge arm.

When using the set for the Varley loop as a Wheatstone bridge see that the plug in the "loop" bar is in block marked "V. & B." When using set for Murray loop test shift the plug into block marked "M."

The lower right hand binding posts are used for all measurements with this set.

The upper right hand binding posts are for extra battery.

If an external galvanometer is to be used, it is to be connected to the left hand binding posts. The plug is shifted from the right hand hole in block marked galv. to the left hand hole in the same

block. This cuts out the galvanometer in the set and cuts in the external galvanometer.

**The Slide Wire Bridge.** A simple form of Wheatstone bridge is in Fig. 65.

A piece of resistance wire about No. 24 B. & S. is stretched between two binding posts *D E*. Their distance apart is a little over one metre.

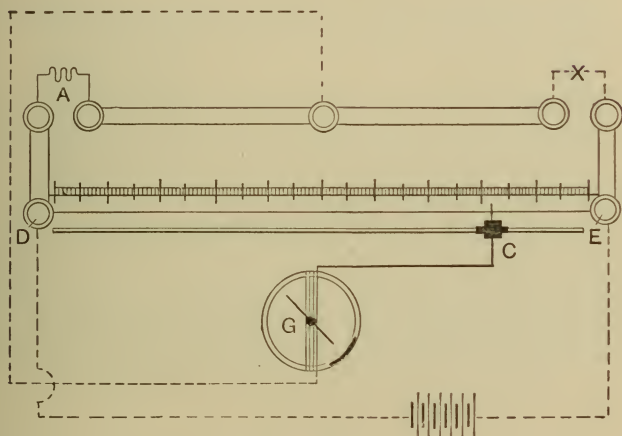


FIG. 65.

Under this wire lies a scale graduated into 1000 equal divisions with a zero at each end.

Brass or copper strips of too small a resistance to be considered lie on the base connecting the binding posts as shown.

The resistance to be measured is connected at *x*.

An adjustable resistance is connected at *A*,

partly taking the place of the rheostat in the P.O. and other Bridges.

A battery and galvanometer being connected as shown, the slider  $C$  is moved along the wire  $DE$  until the galvanometer needle stands at zero.

When the balance is obtained, the resistance of  $x$  will equal the result obtained by multiplying  $A$  by the length of wire between  $CE$  and dividing it by the length between  $DE$ .

The length of the wire can be read either in millimetres or divisions of one thousand.

**Formula.** Let  $x$  be the unknown resistance,  $R$  the resistance at  $A$ ,  $A$  the length between  $DC$  and  $B$  the length between  $CE$ . Then  $R = \frac{R \times B}{A}$ .

**The Stearns Bridge.** An ingenious application of the Wheatstone bridge to the measurement of the resistance of bare wire in continuous lengths is found in the Stearns bridge.

One each of the  $x$  terminals of a bridge is connected to a contact device consisting of a metal roller and a form of knife edge.

The bare wire is wound from one drum on to a second drum passing in its passage through both of the contact devices.

The bridge is adjusted to zero by making the rheostat equal the resistance of a length of wire between the contacts.

The drums being then started, each successive

length passes the contacts and a continuous measurement takes place.

The distance between these contacts being unchangeable, the resistance of the wire included between them should also remain unchanged.

**The Sage Ohmmeter.** The Sage ohmmeter, Fig. 66, is a portable slide wire Wheatstone Bridge of

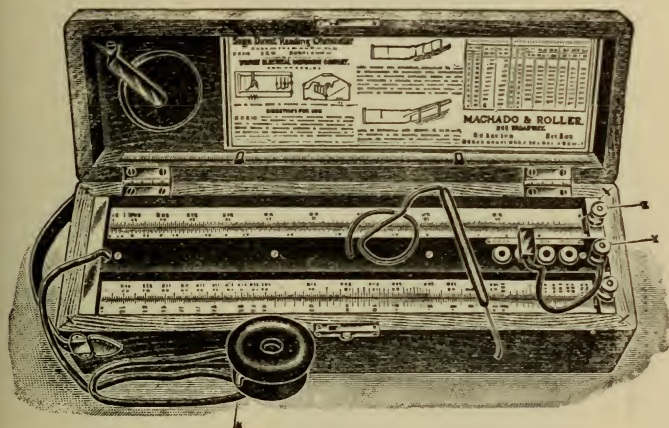


FIG. 66.

peculiar pattern with a telephone receiver as well as a galvanometer.

The adjustable rheostat takes the form of a fine wire, under which are marked resistances in various colors.

A stylus *S* is connected to the telephone *T* as shown in Figs. 67 and 68 and can be touched at

any point on the wire rheostat. Plug *P* cuts in various resistance coils in the Bridge arm, the plug holes being colored to correspond with the markings on the scale.

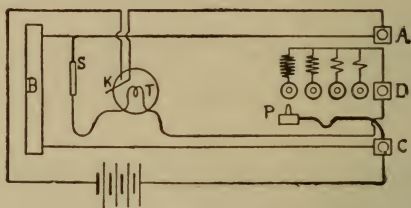


FIG. 67.

In operation the resistance to be measured is connected to posts *A* and *D*. The telephone is held to the ear and the battery key on the telephone is closed. The stylus is tapped at various points on the rheostat wire until no sound is heard

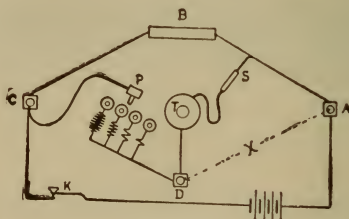


FIG. 68.

in the telephone, the resistance being measured will be found in the figures at the point of stylus contact, where no sound was obtained.

The numbers are to be read in that color corre-

sponding to the plug socket in use. If the plug is in a red hole, read the red figures, and so on. The plug must always be in one of the sockets when testing.

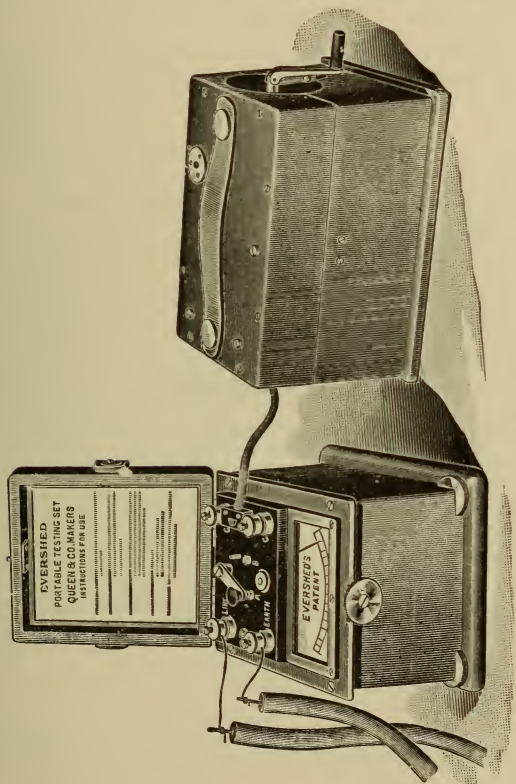


FIG. 69.

**The Evershed Testing Set.** This simple testing outfit, Fig. 69, consists of an ohmmeter and a hand

generator. To test an insulation or other resistance, all that is required is to connect the resistance to the binding posts, turn the generator handle and read the resistance off the dial. No calculations whatever are necessary.

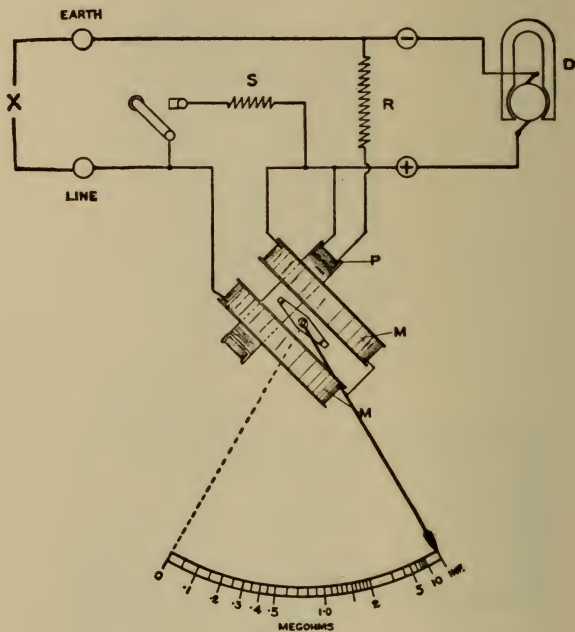


FIG. 70.

The connections of the Evershed set are given in Fig. 70.

Current from the generator *D* flows to the ohm-meter — + where it divides. Part travels through the pressure coil *P* and resistance *R* and tends to

turn the magnetic needle towards the infinity mark on the scale. The other path of the current is through the current coil  $C$  and the fault  $x$ .

If  $x$  has no appreciable resistance the current in  $C$  will be dependent only on the resistance of  $C$  and the e.m.f. of the generator.

In this case the current coil will deflect the needle to zero, which is where the influence of each coil is equal.

The resistance of  $x$  is in series with the current coil. It is obvious therefore that the more resistance in  $x$  the less current in  $C$ . And coil  $P$  turns the needle in proportion as its influence becomes strengthened by reason of the weakening of  $C$ .

Increase of voltage from the generator does not affect the result as it affects both coils.

The scale is graduated in ohms, the instrument being constructed with various sensibilities.

The different instruments range from 2500 ohms to 5 megohms in one instrument and 25,000 ohms to 50 megohms in another. Sets for intermediate readings can also be had.

The generators furnished range from 100 volts to 1000 volts in output.

## CHAPTER VII.

### TESTING WITH GALVANOMETER.

**Current flow and e.m.f. in a Circuit.** The current flow in all parts of a circuit is equal, but the e.m.f. varies according to where it is measured.

In Fig. 71 a fine German silver wire is stretched between terminals *A E* and connected in series with a battery and an ammeter *G*; *F* is a second ammeter connected in the circuit or *G* may be shifted.

When the battery current flows through *A E*, the ammeter placed at *G* or *F* shows the same reading, the current at *G*, *F*, or in fact in any part of the circuit is the same.

Connect a voltmeter *V* at *A* and *E* and note reading, then connect *V* between *A B*, *B.C*, *C D* and *D E* and the latter four readings added together will equal the one between *A* and *E*.

If the wire *A E* is of uniform resistance, the e.m.f. between points at equal distances along it will also be equal.

If *V* be connected as at first to *A* and the connection at *E* be drawn along the wire towards *A*, the e.m.f. will be observed to decrease. This il-

illustrates what is termed "the fall of potential," or if electrical work is being performed, the fall of e.m.f.

If the voltmeter be connected across any two points and a greater current flow be permitted by means of an adjustable resistance  $R$ , the e.m.f. will rise with the current.

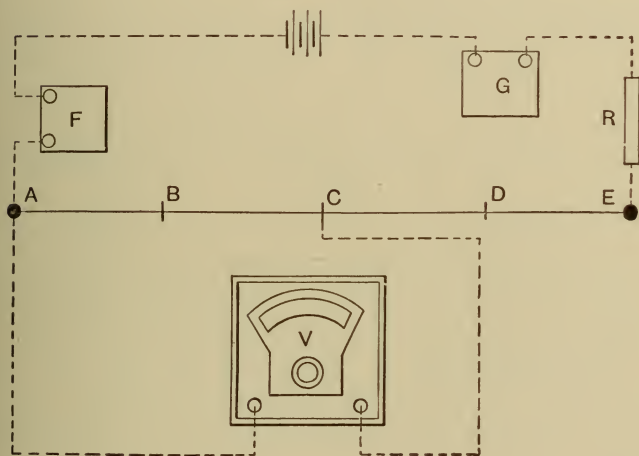


FIG. 71.

As long as the resistance of  $AE$  remains unchanged, a greater current flow requires a greater e.m.f.

**Applications of Ohms Law.** If the resistance between the connections of  $V$  be known, the cur-

rent flowing may be computed from the deflection of  $V$  by Ohms law.  $I = \frac{E}{R}$  or the current equals the e.m.f. divided by the resistance.

For example, let  $A E$  measure 2 ohms and  $V$  indicate 4 volts, then the current will be  $\frac{4}{2}$  or 2 amperes.

If any two readings be known, the third can be computed by Ohms law.

From the e.m.f. and current flow find the resistance.  $R = \frac{E}{I}$  or the resistance equals the e.m.f. divided by the current. In this example  $\frac{4}{2} = 2$  ohms.

And from the current and the resistance find the e.m.f.  $E = R \times I$  or the e.m.f. equals the resistance times the current in this example  $2 \times 2 = 4$  volts.

The applications of Ohms law and the fall of potential will be found in the potentiometer, the shunt ammeter and in various tests to be described later.

**Testing Resistance.** Let an unknown resistance be placed in series with a battery of constant e.m.f. and a galvanometer. Note the deflection and replace the unknown resistance by an adjustable resistance. Adjust the latter until the second deflection is equal to the first and the two resistances are equal.

If the adjustable resistance be of known value this method can be pursued, but a more practical method is to first ascertain the constant of the galvanometer.

**The "Direct Deflection" Method.** This is the simplest method of testing resistances or insulations and is capable of extended application.

It is based upon the fact that the greater the current flow through the galvanometer the wider the angle of deflection.

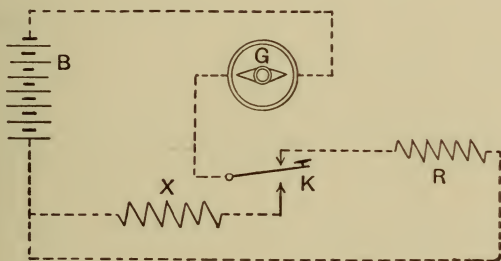


FIG. 72.

A known resistance  $R$ , Fig. 72, is put in circuit with the galvanometer  $G$ , battery  $B$  and double contact key  $K$ .

After noting the deflection, the key is depressed and the unknown resistance  $x$  thrown in circuit. The second deflection is then noted and compared with the first.

If the galvanometer deflections are proportional to the current,  $x$  will be as many times the resist-

ance of  $R$  as the deflection through  $R$  is greater than that through  $x$ .

For example, let  $R$  equal one hundred ohms and the deflection through it be ten degrees. The second deflection through  $x$  is twenty degrees. This shows that the current flowing through  $x$  is twice that which flowed through  $R$  and therefore the resistance of  $x$  is only one-half that of  $R$ , or fifty ohms.

**Formula.** As a formula, let  $x$  equal the unknown resistance,  $R$  the known resistance,  $D$  the deflection through  $R$  and  $d$  the deflection through  $x$ .

$$\text{Then } x = \frac{D \times R}{d}.$$

In case the galvanometer resistance is to be allowed for it is to be added to  $R$  but deducted from  $x$ . Calling it  $r$ , the formula stands

$$x = \frac{D \times (R + r)}{d} - r$$

**Galvanometer Figure of Merit or Constant.** It is customary in many uses of the galvanometer to determine the figure of merit or constant of the galvanometer.

This is the resistance through which the galvanometer will give a deflection of one scale degree for one volt of e.m.f.

If 100,000 ohms could be inserted in series with the galvanometer and one volt e.m.f. and still one degree of deflection be obtained, the figure of

merit or constant of the galvanometer would be 100,000 ohms.

And if 50,000 ohms with one and one-half volts gave a deflection of three degrees, the constant would be as follows:

The e.m.f. is one-half as much again as required, therefore the deflection will be one-half as much again or one-third more than it should be. Reducing it by one-third gives two degrees of deflection.

And it is evident that if two degrees are obtained through a certain resistance, one degree would be obtained through twice the resistance.

One degree of deflection only requires one-half the current to produce it that two degrees does, therefore the constant for the galvanometer is  $50,000 \times 2$  or 100,000 ohms.

**Formula.** To make a formula out of this let  $D$  be the deflection through the resistance,  $R$  be the resistance,  $V$  the e.m.f., and  $x$  the constant required. Then  $\frac{D \times R}{V} = x$  or  $\frac{3 \times 50,000}{1\frac{1}{2}} = 100,000$ .

The terms constant, figure of merit and sensibility are used to mean the same. Sensibility or constant are the most generally adopted, however.

**With Shunts.** If a shunt is used in obtaining the constant the deflection and resistance must be multiplied by the value of the shunt which will be known as  $n$ , as before.

In the above example let the shunt be  $\frac{1}{10}$  with a multiplying power of 10.

The formula will be then

$$\frac{D \times R \times n}{V} = x \text{ and the last example } \frac{3 \times 50000 \times 10}{1\frac{1}{2}}$$

or 1,000,000 ohms.

Using the  $\frac{1}{10}$  shunt only one-tenth of the current went through the galvanometer but as it is for example assumed to give the same deflection as at first, its constant is ten times higher.

In some cases the full battery perhaps 100 cells is used to get a constant by shunting the galvanometer.

The constant is then not for one cell but for the whole battery.

Its value will be the product of the deflection, the known resistance and the shunt.

**Formula.** Using the above letters, (battery of one hundred cells),

$$D \times R \times n = \text{constant.}$$

**EXAMPLE.** Let the deflection be  $16^\circ$ , resistance 100,000 and shunt  $\frac{1}{100}$ . Then constant for the battery in use will be  $16 \times 100,000 \times 100$  or 160 megohms.

And it is evident that the constant for one cell will be one-hundredth of the above, or 1,600 000 ohms.

Where the figures of resistance become high it is preferable in calculating to substitute the value in megohms or fractions of a megohm.

Second Example. Let the figures used in determining the constant be,  $R = .1$  (one-tenth) of a megohm,  $D$  be  $100^\circ$  and the shunt  $\frac{1}{1000}$ .

In testing an unknown resistance with the same shunt and battery the deflection is  $10^\circ$ .

Then the constant is  $100 \times .1 \times 1000$  or 10,000 megohms.

And the unknown resistance  $\frac{10,000}{10}$  or 1000 megohms.

**Summary of Rule.** When using the same shunt battery and galvanometer the value of an unknown resistance will be determined by dividing the constant by the deflection obtained through this unknown resistance. If a different shunt  $s$  is used the formula will be

$$\frac{D \times R \times n}{d \times s}$$

**Deflection Constant.** It is often convenient to use the deflection obtained through a known resistance as the constant. The degrees of deflection obtained in a test will then be calculated in terms of the resistance used when getting the constant.

For example, let the deflection through one megohm be  $85^\circ$ . Then the resistance-con-

stant would be one degree through 85 megohms, and the deflection-constant would be 85 degrees through one megohm.

In testing an unknown resistance under the same conditions of battery, shunt, etc., the deflection is 170 degrees. Then  $\frac{85}{170} = \frac{1}{2}$  and the unknown resistance is one-half megohm.

Rule: Divide the deflection-constant by the deflection through the unknown resistance; answer is in terms of standard used to determine constant.

**Formula.** Let  $R$  be the standard resistance,  $D$  the deflection through it,  $x$  be the unknown resistance,  $d$  the deflection through  $x$ . Then

$$x = \frac{D \times R}{d}$$

If  $R$  be one megohm the calculation is simplified for quick working, and becomes  $\frac{D}{d}$  in megohms.

**Direct Deflection with Queen Set.** The Queen Acme set,  $T$  460, may be used for tests of this nature; a special set is, however, constructed having a resistance in series with the galvanometer. The latter can also be shunted by manipulating the Bridge.

The  $T$  460 set is used as follows:

To obtain the constant, connect a resistance of about 100,000 ohms such as one of the glass slabs,

between the top left hand post and the + battery post.

Remove all plugs from the commutator between the Bridge arms and plug in all coils. Connect in one cell of battery by means of the flexible cords.

The setting should be as in Fig. 73. It will be seen from this diagram that the circuit starting downwards from the slab runs through the + battery post, battery key *B a*, rheostat

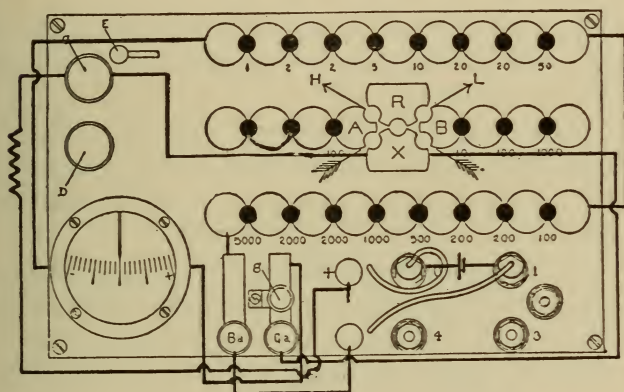


FIG. 73.

blocks, galvanometer, galvanometer key *G a*, to the main post and to the upper part of resistance slab.

The slab, galvanometer and battery will thus be in series when *B a* and *G a* are depressed.

If any plugs have been left out in the rheostat, the resistance of the coils they control will also be included in the circuit.

When *B a* and *G a* are depressed a deflection of the galvanometer will ensue. If this deflection is one degree, the constant is 100,000 ohms.

If more than 1 degree, remove plugs from rheostat and add resistance thereby interpolated to resistance of slab. The constant will be the figure so obtained.

And if less than one degree, a lower resistance than 100,000 ohms must be used, but it is not likely that this will be the case.

The constant having been obtained, detach slab and connect resistance or insulation to be measured in its place.

If the deflection is too small add more cells. A larger battery can be added by connecting it to the battery posts, detaching the flexible cords and cups from the battery in the case.

To determine the resistance now being measured, divide the constant by the deflections obtained and multiply the result by the number of cells used.

For example, let the deflection be  $10^{\circ}$  with 5 cells.

$$\frac{100,000 \times 5}{10} = 50,000 \text{ ohms.}$$

The deflection has been increased 10 times, which would show that the resistance was only one-tenth of the constant or 10,000 ohms.

But as five times the e.m.f. has been used, the result must be multiplied by five.

Another method is to use the deflection obtained through 100,000 ohms as the constant. Divide this constant by the deflection obtained in the test and

multiply by the number of cells used. The answer will be in terms of 100,000 ohms.

For example, let  $8^\circ$  be the deflection constant through 100,000 ohms with one cell, and  $4^\circ$  be that through the unknown resistance with five cells.

Then  $\frac{8}{4} \times 5 \times 100,000 =$  the unknown resistance, or 1,000,000 ohms.

In such tests the resistance of the galvanometer may be neglected.

If it is desired to use only the galvanometer of the Acme set, remove the plugs from the commutator, insert all other plugs and connect to the main posts at left end of case. The galvanometer and key are now directly connected to these binding posts.

**Measuring Resistance with Voltmeter.** The voltmeter being considered merely as a galvanometer, it may be substituted for the latter.

The deflection obtained from a battery or other source of current is noted.

This deflection is actually through the resistance of the voltmeter.

A second deflection is then taken with the unknown resistance in series with the voltmeter and battery.

This deflection is dependent upon the current allowed to flow through both the voltmeter resistance and the unknown resistance.

The first deflection multiplied by the voltmeter

resistance will give the resistance through which one degree of deflection could be obtained, or the constant.

The value of the second deflection can then be calculated from this constant, the latter divided by the second deflection will give the total resistance. Subtract the voltmeter resistance and the result will be the value of the unknown resistance.

The connections are as in Fig. 74, more extended

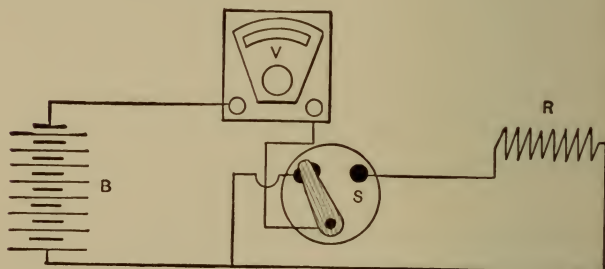


FIG. 74.

description of this test being given in the chapter treating on measurements with the voltmeter.

**Testing Resistance of Galvanometer.** In many tests it is necessary to know the resistance of the galvanometer being used. If it is not marked on the instrument it may be found by the following method:

Arrange the galvanometer *G*, Fig. 75, in series with an adjustable resistance *R* and battery *C*.

The resistance and battery should be so selected that the deflection of  $G$  is about one-half the scale. This is to enable readings to be made with accuracy.

Having noted first deflection, increase resistance  $R$  until deflection of  $G$  is just one-half of its first deflection.

The battery used must be constant or its variations will affect result. They may, however, be compensated for. Battery resistance is omitted.

The resistance of the galvanometer will equal the resistance of  $R$  as measured at the time of one-half deflection less twice the original resistance of  $R$ .



FIG. 75.

For example, let  $R$  equal 10,000 ohms and the first deflection be  $40^\circ$ , increase  $R$  until at one-half deflection it equals say 25,000 ohms. Then  $10,000 \times 2$  or 20,000 from 25,000 leaves 5000 ohms, the resistance of the galvanometer coils.

**Formula.** As a formula, let  $R$  be first resistance,  $r$  be second resistance; then  $G = r - 2R$ .

**Resistance of Galvanometer by Bridge.** Connect the galvanometer  $G$  between the posts used in ordinary resistance tests, as in Fig. 76.

Adjust the rheostat  $R$  until the needle of  $G$  is at the same deflection when key is open or closed. Then the resistance of  $G$  will equal resistance in  $R$  multiplied by result obtained from dividing resistance in arm  $B$  by that in arm  $A$ .

**Battery Tests.** Tests of battery cells may be to determine e.m.f., internal resistance or life. For the latter no directions will be given.

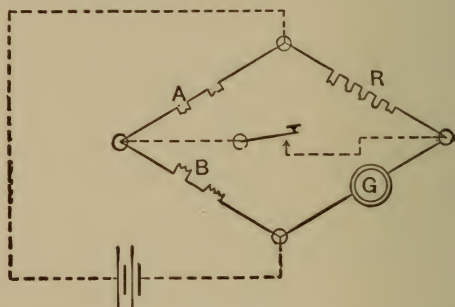


FIG. 76.

The simplest test for e.m.f. is to connect a voltmeter across the terminals of the cell. A high resistance voltmeter must be used, one with not less than 80 ohms per volt is desirable.

The cell being disconnected from any other circuit will give its e.m.f. on open circuit.

Tests of similar nature may be made by discharging cell through resistances of different values.

Tests for internal resistance are needful in many electrical operations and a number of methods will be described.

**First Method of Measuring Resistance of a Cell.**

Take open circuit e.m.f. of cell with voltmeter of known resistance  $R$ .

Add resistance  $r$  in series with cell and voltmeter and adjust until e.m.f. deflection is one-half.

Calculation: Add additional resistance to that of voltmeter so as to obtain total resistance in series with cell. Subtract twice the resistance of voltmeter and answer will be that of cell. This test is only suitable where internal resistance of cell is high.

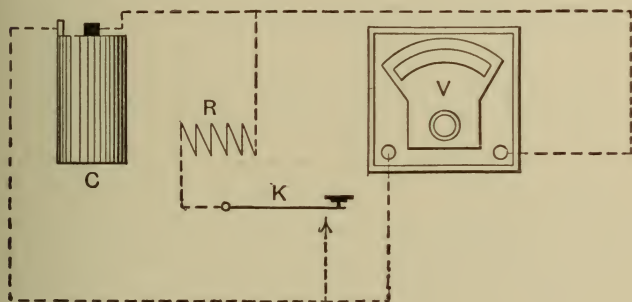


FIG. 77.

**EXAMPLE.** Voltmeter = 521 ohms, e.m.f. 1.5 volts; adding 530 ohms reduces e.m.f. to .75 volt. Total resistance  $521 + 530 = 1051$ . This less  $521 \times 2$  or  $1042 = 9$  ohms.

**Formula.**  $(R + r) - 2R = \text{cell resistance.}$

**Second Method.** In Fig. 77  $C$  is the cell whose internal resistance it is desired to measure,  $V$  a

voltmeter,  $R$  a known resistance and  $K$  a key to connect  $R$  across the circuit when desired.

First read the e.m.f. of  $C$  with the key open; then depress key and read the e.m.f. across  $R$ .

Then the resistance of the cell will equal the first e.m.f. minus the second e.m.f. divided by the second e.m.f., or as a formula,  $r = R \times \frac{v - v_1}{v_1}$ .

The second e.m.f. is really the drop across the resistance.

EXAMPLE.—Let first e.m.f. be 2 volts, resistance be 2 ohms, second e.m.f. across resistance be 1.5 volts, then internal resistance is

$$2 \times \frac{2 - 1.5}{1.5} \text{ or } 2 \times \frac{.5}{1.5} \text{ or } 2 \times \frac{1}{3} = \frac{2}{3} \text{ ohm.}$$

**Third Method.** Another shunt method is by using a resistance which equals the total resistances in the circuit such as galvanometer, wires, etc. Connect this in shunt across the cell, also connect galvanometer and wires to which shunt was adjusted across cell.

The connection would be similar to the last figure, only the shunt should be directly connected across  $C$ .

Having made these connections, note deflection, and then remove shunt by opening key.

Note second deflection. Add resistance in galvanometer (or voltmeter) circuit until second deflection equals first.

The value of the added resistance will be the internal resistance of the cell.

At the first deflection, there was a two branch divided circuit of equal resistances, the current then through galvanometer was one-half the total flowing.

At the second reading the added resistance cut down the current by one-half, but by a series resistance instead of a shunt.

**Fourth Method.** The simplest test of internal resistance is with the voltmeter and ammeter. Connect ammeter so as to obtain reading of current using a resistance to control current.

Take e.m.f. reading directly across cell terminals.

Then by ohms law  $R = \frac{E}{I}$ .

In making this last test the current from the cell may be reduced which is an advantage by adding a resistance in series with it. The ammeter is to be included in the circuit.

The e.m.f.  $V$  of the cell on open circuit is first read. With the resistance in, the e.m.f. is again read  $v_1$ . The current ( $I$ ) is also read on the ammeter.

Then  $r$  or the resistance of the battery is equal to  $\frac{V-v_1}{I}$ .

Most of the above methods are only suitable for non-polarizing cells or cells of low internal resist-

ance. The Wheatstone Bridge methods are preferable.

**Resistance of Battery by Bridge.** In Fig. 78  $C$  is the cell to be measured connected to line posts of bridge.

A key  $K$  and the galvanometer  $G$  is connected as shown.

Make the reading of  $G$  equal whether  $K$  is open or closed by adjusting rheostat  $R$ .

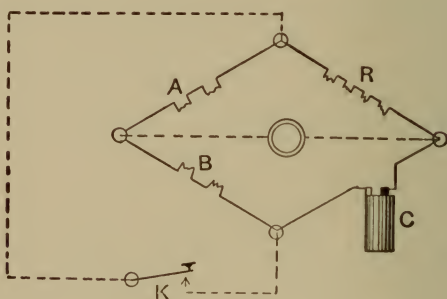


FIG. 78.

**Formula.** Then the resistance of  $C$  will equal the result obtained by multiplying  $R$  by  $\frac{B}{A}$ .

In the formula  $R$  is resistance of rheostat,  $B$  that of arm  $B$  of bridge, and  $A$  that of arm  $A$  of bridge.

**Measuring Current Flow of Cell.** The rate of current flow of a cell may be deduced from Ohms

law after reading the e.m.f. and the internal resistance.

But it may also be measured with an ammeter on short circuit.

The latter method is not always desirable. The test can also be made with a tangent galvanometer.

The tangent galvanometer can be used as an ammeter providing the directive force of the earth's magnetism be known for the place where the measurement is made.

This directive force is used in the form of a constant. It varies however, from time to time.

The constant of the place of measurement is multiplied by the radius of the galvanometer coil in inches and the result divided by the number of turns in the galvanometer coil. This gives a constant for the galvanometer.

When a current produces a deflection of the needle, the tangent of the angle of deflection multiplied by this galvanometer constant equals the current flow in amperes.

EXAMPLE.—A cell of battery applied to the terminals of a 10 turn coil which had a radius of 6 inches produced a deflection of  $18^\circ$ . The test was made in New York.

Constant of the galvanometer equals  $\frac{.744 \times 6}{10}$

or .4464.

$\tan (\text{tangent}) 18^\circ = .3249.$

Then  $.4464 \times .3249 = 1.4518$  amperes.

**Formula.** Let  $I$  = current flow;  $H$  constant of location;  $r$  radius of coil;  $N$  number of turns of coil;  $G$  constant of galvanometer;  $T$  tangent of deflection. Then  $G = \frac{H \times r}{N}$  and  $I = G \times T$ , or

$$I = \frac{H \times r}{N} T.$$

## CHAPTER VIII.

### THE POTENTIOMETER.

**The Potentiometer.** Referring back to Fig. 71 let the negative terminals of two independent battery cells be attached to  $A$  and their positive terminals to  $E$ . No current will flow along  $A E$  if the e.m.fs. of the cells are equal. This can be proven by inserting a voltmeter in series with either cell or between  $A E$ . One e.m.f. is opposing the other e.m.f. If now two cells in series be applied to  $A E$  and a third cell be connected in multiple between  $A E$  as before, a voltmeter or galvanometer will show current due to the excess of e.m.f. from two cells against one. Or if all the cells are equal, the deflecting force will be equal to that of one cell.

Connect a voltmeter or galvanometer in series with the one cell and leaving the negative terminal connected to  $A$  move a wire from the voltmeter along  $W$ . A point will be reached where the voltmeter or galvanometer will settle to zero showing the e.m.f. of the one cell is equal to that opposing it from the two cells. As the wire  $W$  is of uniform resistance, the e.m.f. across one-half of

it will be one-half that across its entire length. The point of zero will then in the present case be in the middle at  $C$ , and the relation between the two lengths of wire will equal that between the two e.m.fs. Or the length  $AC$  will be to  $AE$  as the e.m.f. of the one cell will be to that of the two cells.

Although there is some similarity between a potentiometer and a Wheatstone bridge there exist two great differences. The bridge has one source

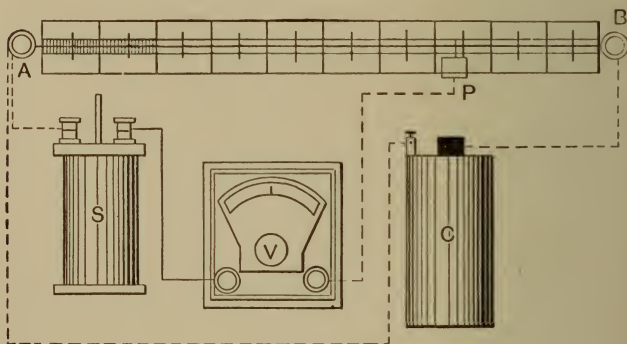


FIG. 79.

of e.m.f. and two circuits; the potentiometer two opposing e.m.fs. in one circuit.

A balance is obtained in the bridge when the points of equal e.m.f. in two circuits are connected through the galvanometer.

In the potentiometer the point of equal e.m.f. between two e.m.fs. is found in one circuit.

A simple form of potentiometer is shown in Fig. 79. Between the binding posts  $AB$  is

stretched a fine resistance wire. A sliding contact  $P$  moving on a guide rod carries an index which indicates on a scale graduated into 1000 equal divisions. This scale may conveniently be one metre long and the wire No. 24 B. & S. gauge. A standard cell  $S$  is connected, one terminal to  $A$  and the other terminal to the voltmeter  $V$ . The second terminal of the voltmeter goes to the sliding contact  $P$ . If  $V$  is not provided with a key one may be inserted between  $A$  and  $P$ . The cell the e.m.f. of which is to be compared is connected to  $A$  and  $B$ . Similar terminals of each cell must be connected to  $A$ .

Contact  $P$  being moved,  $S$  and  $C$  being both in circuit, a point on the wire will be found where  $V$  gives a zero reading.

When the balance is obtained, the scale divisions from  $A$  to  $P$  will bear the same relation to those from  $A$  to  $B$  that the e.m.f. of cell  $S$  does to the e.m.f. of  $C$ . The e.m.f. of  $S$  being known the e.m.f. of  $C$  is easily calculated.

Let  $S$  be 1.019 volts,  $AP$  be 755 and  $AB$  1000. Then  $755:1000 :: 1.019$  is to  $C$  or  $\frac{1000 \times 1.019}{755} = 1.349 \dots \text{volts.}$

If  $AP$  were 10 and  $AB$  1000,  $C$  would equal 101.9 volts. It is evident that  $S$  should be less than  $C$  or no point of zero will be found.

As this is a zero method, that is the object being to reduce  $V$  to zero,  $V$  need not be calibrated in volts but may be any form of galvanometer. If

it were desired to check a voltmeter, the latter would be inserted across  $A B$ , the reading on this voltmeter should equal the e.m.f. obtained by the calculation.

As the sliding of the contact  $P$  only cuts in or out a resistance formed by the wire, the resistance of the latter may be determined. Each scale division will then have a value in ohms or fractions of an ohm.

To make this clear, let the wire be for example 10 ohms, then each of the 1000 divisions on the scale will equal  $\frac{1}{100}$  of an ohm.

And in the foregoing example 755 divisions would equal 7.55 ohms.

The whole example would read 7.55 ohms : 10 ohms : : 1.019 is to 1.349 volts. the same result as before.

To check an ammeter it would be placed in series with a steady source of current. A shunt or known resistance is also in *series* with the ammeter.

Leads of no appreciable resistance are run from each end of the shunt to  $A$  and  $B$ , The e.m.f. across this shunt is first determined. The current flowing is then calculated by dividing the e.m.f. across the shunt by the resistance of the shunt, or

$I = \frac{E}{R}$ . This should equal the reading on the ammeter. The shunt must be of sufficiently high resistance to give a drop of e.m.f. greater than

the e.m.f. of  $S$ . For example, let the shunt be 5 ohms, and the e.m.f. across it be 10 volts. Then  $\frac{10}{5} = 2$  amperes. Some of the foregoing rules may be modified in actual work with the more complicated forms of potentiometers, but the principles remain the same.

If it is desired to measure a high e.m.f. and yet not apply it in full to the potentiometer, any desired e.m.f. may be taken off by means of resistances. A number of resistance coils being placed in series with the high e.m.f., connection may be made between two or more for the desired e.m.f. In the case of an e.m.f. of 100 volts, let 10 volts be needed for purposes of measurement. Place in series two coils one of 100 ohms and one of 900 ohms. Connecting across the 100 ohm coil will give an e.m.f. of 10 volts, across the 900 ohm coil, 90 volts, and across the two coils, 100 volts. The reason for using such high resistances is to keep down the current. The actual resistances used may vary according to circumstances, their relation to one another is only of importance.

In some tests it is desirable to connect the known source of e.m.f. across  $AB$  and the unknown across  $AP$ .

By using a charged storage battery and suitable high resistance a steady e.m.f. may be obtained for some hours. Dry cells are not suitable as their curve of e.m.f. drops too abruptly.

In using the potentiometer with a large battery

of constant e.m.f. the latter is connected to  $A B$ , its positive pole to  $A$ .

A standard cell  $S$  is connected, positive pole to  $A$  and negative pole through voltmeter or galvanometer to  $P$ .

$P$  is moved until there is no deflection. The divisions between  $A$  and  $P$  are noted, or if the scale is graduated in terms of resistance of  $W$ , the ohms are noted. Call this  $R$ .

The standard cell being replaced by the cell under test, a point of balance is again sought. Call the resistance of divisions from  $A$  to  $P$  in this case  $r$ . Then the e.m.f. of the cell being tested is to the e.m.f. of  $S$  as  $r$  is to  $R$ .

It may be necessary in order to obtain greater accuracy to use two or more standard cells in series between  $A$  and  $P$ .

For example, let e.m.f. of the standard cells  $S$  be 2.038  $A B$  equal 1000 and  $A P$  equal 100. Then the e.m.f. across  $A B$  will be  $\frac{1000}{100} \times 2.038$  or 20.38.

Substituting the cell  $C$  to be tested for  $S$  it is evident that zero balance will be again obtained when its e.m.f. balances the e.m.f. between  $A P$ . It may be then read in terms of the e.m.f. across  $A B$  or in terms of  $S$ .

Suppose balance now is obtained at 125. This will be  $\frac{125}{1000}$  of  $A B$  or 2.547 likewise  $\frac{125}{100}$  of  $S$ .

In figures  $\frac{125}{1000} \times 20.38 = \frac{125}{100} \times 2.038$ .

The modern testing sets are generally suitable for use as potentiometers as the following examples will show.

As plug switches are used instead of sliding contacts, the relations corresponding to divisions on a scale will be those of resistances in ohms. In the testing sets, the resistance equivalent to that between  $AP$ , Fig. 79, is made 100 ohms and is not changed. The resistance equal to  $PB$  is adjustable and is first made high.

As the sliding of  $P$  merely changes the *relation* between  $AP$  and  $AB$  the same result is obtained by changing only  $PB$ . This which is not feasible in the slide wire instrument becomes an advantage in the plug switch pattern.

In the following two tests consider the  $B$  arm to represent the wire  $AP$  and the rheostat the wire  $PB$ . The  $B$  arm plus the rheostat will then equal the total resistance of wire  $W$  or from  $A$  to  $B$ .

Although the examples given are measurements of e.m.f. or current, the potentiometer is equally well adapted for comparing resistances and insulations.

**Checking Voltmeters.** Voltmeters may be checked by comparison with a standard instrument or by the potentiometer method.

In the former case, the standard instrument and the one being checked are connected in multiple across the e.m.f. at the same point and their readings compared.

**Potentiometer Method with Queen Set.** Unplug 10,000 ohms from rheostat, unplug *A* arm of Bridge and unplug 100 ohms only from *B* arm. Remove plugs from commutator except one in upper right hand hole, that is, connecting *R* and *B* blocks.

Disconnect flexible battery cords from battery tips. Connect negative terminal of a standard cell or cell of known e.m.f. to line post *C* and its positive terminal to + battery post.

Connect line e.m.f. to battery posts, + to + and - to - .

Depress *B a* and *G a* keys and change resistance in rheostat until no deflection occurs. If needle goes towards + on scale, reduce rheostat and vice versa. Proceed carefully as the balance will occur at a point of slight change in the rheostat.

When balance is obtained, add 100 ohms to the reading of the rheostat and divide by 100 or point off two places.

Multiply this result by e.m.f. of standard cell and answer is e.m.f. of outside circuit.

For example, suppose balance was obtained with 8855 ohms in rheostat and e.m.f. of standard cell is 1.44.

Then  $\frac{8855 + 100}{100} = 89.55$  and this multiplied by

1.44 = 128.95 volts as e.m.f. of outside circuit.

**Formula.** Let *R* = rheostat at balance; *B* =

resistance of  $B$  arm,  $e$  = e.m.f. of standard cell, and  $E$ , e.m.f. to be found.

Then  $\frac{R+B}{B} e = E$ , or what is the same thing,  
 $\frac{R+B}{B} \times e = E$ .

**Potentiometer Method with Willyoung Set.** The connections for the measurement of an e.m.f. by the potentiometer method are shown in Fig. 80.

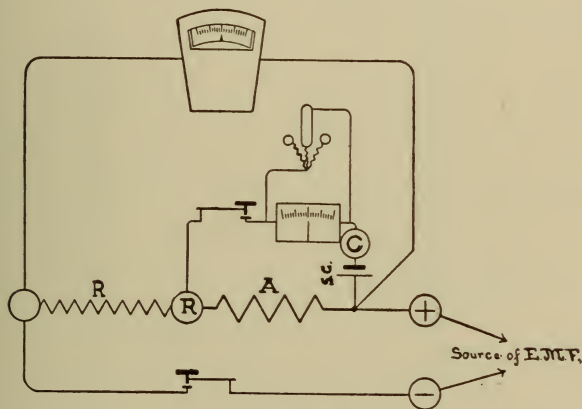


FIG. 80.

The operation to be performed here is the checking of a voltmeter.

$SC$  is a standard cell,  $A$  one arm of the bridge,  $R$  the rheostat.

A key and shunt are in the galvanometer circuit and a key or switch in the power circuit. The latter may be a tap from a direct current main or



storage battery. But a few lamps or other resistance should be put in circuit to avoid danger of excessive current.

The standard cell negative terminal is connected to *C* and the positive terminal to a movable plug which for the present is placed in the 100 ohm hole of the *A* arm.

The outside e.m.f. is connected, positive terminal to + battery post and negative terminal to - battery post. *R* is then adjusted until needle remains at zero, always closing the battery key first.

*R* should be first made very large and gradually reduced. Unplug say 20,000 ohms and then replace plugs one by one.

On a circuit of 110 volts *R* will be somewhere near 9000 ohms.

It will be found that at a certain point a very slight change in the rheostat will reverse the galvanometer deflection.

To determine the e.m.f. of the line, which should be also the reading on the voltmeter if it is accurate, figure as follows:

Add 100 (the resistance in the *B* arm) to the resistance needed in the rheostat for a balance and point off two places, that is, divide the above sum by 100. Multiply the result by the e.m.f. of the standard cell and the result is the e.m.f. of the line.

For example, suppose 7816 is the rheostat reading, 1.44 the e.m.f. of cell. Then  $\frac{7816 + 100}{100} =$

79.16 and  $\times 1.44 = 113.99$  volts. The difference between this result and indication on voltmeter is the error of the latter.

Of course if the standard cell is one volt, the e.m.f. would be 79.16 or the rheostat reading plus the  $B$  arm and divided by one hundred.

**Formula.** Let  $E$  represent e.m.f. of line (or indication voltmeter should show),  $e$  the e.m.f. of standard cell,  $R$  resistance in rheostat,  $B$  resistance in  $B$  arm.

Then 
$$E = \frac{R+B}{B} \times e.$$

## CHAPTER IX.

### CONDENSERS.

**Charge and Discharge of Condenser.** Connect a condenser  $C$ , battery  $B$ , galvanometer  $G$  and key  $K$  as in Fig. S1.

Depress  $K$  and a deflection will be noted at  $G$ . This is due to the charge of the condenser.

Release  $K$  and upon the back contacts meeting,

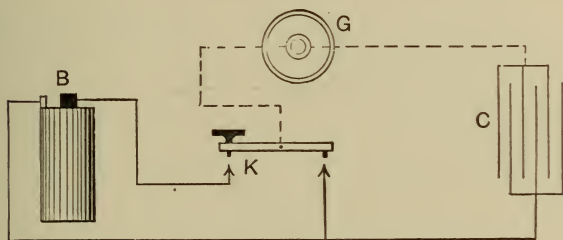


FIG. S1.

a second deflection takes place at  $G$  but in the opposite direction.

Again depress  $K$  so as to open the back contact but not close the battery circuit. Upon again releasing  $K$  a deflection will ensue but very much less than the previous ones. And this last operation being repeated, decreasing deflections will be noted.

If  $K$  be depressed for varying intervals of time and released the deflections will also vary.

It takes a certain length of time to charge a condenser. Increasing the battery will reduce the time of charge.

If a Kempe discharge key is used the connections will be practically the same. The back contact of the key in the figure will be the top contact in

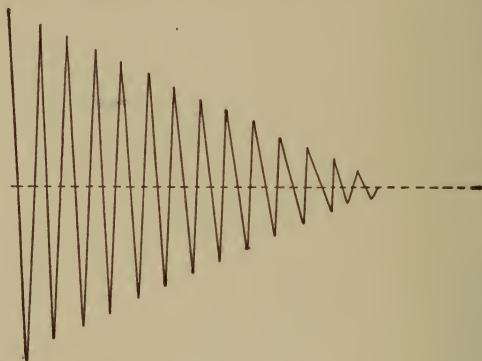


FIG. 82.

the Kempe key, and the front contact the lower contact of the Kempe key.

The capacity of the condenser is measured by the extent of the deflection upon first short circuiting it through the galvanometer. This is true when battery power and other conditions are equal.

If the discharge of  $C$  be observed with an appropriate apparatus, it will be seen to be oscillatory as in Fig. 82, not steady as that of a battery cell.

A condenser does not store up electricity, the operation called charging merely leaves it under an electric strain which is relieved when it is discharged.

It may be likened to a spiral spring which is suspended from one end and has a weight at the other end. If this spring be pulled still farther down, an ability to do work or a potential is given it. Now upon releasing the spring, it contracts, pulls up the weight, and then slightly expands again, causing the weight to jump up and down until the force is exhausted.

The spring and weight have an oscillating motion even as does the condenser discharge show an oscillatory character.

A condenser offers the resistance of its insulation to a direct current, in other words will not allow a current of this character to pass through it.

But the effect of an alternating current is not arrested by a condenser. An ordinary vibrating bell will not be rung by a battery through a condenser except one tap due to charge. The alternating current of a telephone magneto will ring the bell with which it is equipped without trouble through a condenser.

This does not show, however, that the alternating current actually passed through the dielectric. It is the inductive effect between the plates, a condenser acts therefore by the induction taking place between its parts.

To avoid complications of words the condenser

is said to retain a charge and to permit itself to be discharged.

**Measurement of Capacity.** The capacity of a condenser is measured by comparing the discharge deflections with those obtained from the discharge of a condenser of known capacity. The latter is termed a standard condenser.

The operation is as follows:

Charge standard ( $S$ ) for a certain length of time, say one minute, then discharge it and note deflection ( $D$ ).

Then replace standard by the condenser under test ( $C$ ). Charge and discharge under precisely similar conditions and note deflection ( $d$ ).

The connections may be similar to Fig. 81 or the battery may be connected directly to the condenser through the key. The galvanometer would not be then in circuit during charge. Or the galvanometer may be shunted or short circuited.

The condenser under test will bear the same relation in capacity to the standard that the deflections do to those obtained by discharging the latter.

**Formula.** Or as a formula,

$$S : C :: D : d. \quad \text{Then } C = S \frac{d}{D}.$$

Another method by the bridge is as follows: A standard condenser and the condenser to be tested are connected in a similar manner to the

two arms of the bridge. Each condenser takes the place of the coils in one arm.

An adjustable resistance is connected in the binding posts provided for the  $x$  or unknown resistance.

A discharge key and battery are connected taking the place of the regular battery in the bridge. The condensers are charged and discharged, and the resistances adjusted in the other sides of the bridge until no deflection obtains.

At balance the two condensers are to each other in respect to capacities inversely as the two resistances are to each other.

**EXAMPLE.** Capacity of standard condenser  $S$  is .3 (three-tenths) microfarad. Resistance  $R$  on same side of the bridge is 1800 ohms. Resistance  $r$  on side of bridge where condenser  $T$  to be tested is connected, is 1200 ohms. Then  $T:3::1800$ .

$$1200 \text{ or } \frac{.3 \times 1800}{1200} = .45 \text{ microfarad.}$$

**Formula.** Using above letters,  $T: S :: R: r$ .

**Insulation of Condenser.** A condenser can be tested for insulation by charging it through a shunted galvanometer. When fully charged the deflection should return to zero.

If a deflection is shown after charging is completed it indicates that current is passing through condenser. The value of this current and the resistance of the fault in the condenser are computed

from the galvanometer constant as in any direct deflection method.

But this method does not give as close a test of very high insulations as the loss of charge method.

**Insulation by Loss of Charge.** A condenser retains its charge (or electric strain) for a length of time dependent upon the perfection of its insulation. This property gives a method for determining its insulation as well as by the usual resistance tests.

A condenser is attached to a battery for a given length of time and then discharged through a galvanometer. The deflection having been noted, the condenser is again charged under precisely similar conditions and left with its terminals insulated for a given period of time and again discharged through the galvanometer.

The two deflections being compared the loss of deflection in the second reading is a measure of the loss of charge. This loss being due to the state of insulation, the latter is therefore determined.

In a good standard condenser this loss for a short period of time is inconsiderable.

As cables and wires act in a similar manner to condensers, their insulation can also often be determined by the loss of charge method.

The following figures are approximate as the actual substance or fluid varies somewhat. For purposes of comparison, however, the figures are sufficiently accurate.

TABLE IV.

Specific inductive capacity taking air as 1.

---

Flint Glass.....	10
Plate Glass.....	7.06
Gutta-percha.....	2.62
Mica.....	5
Paraffin wax.....	2.31
Pitch.....	1.80
Shellac.....	2.59
Sulphur.....	3.82
Olive oil.....	3.16
Castor oil.....	4.78
Turpentine.....	2.23

---

## CHAPTER X.

### CABLE TESTING.

**Cable Testing.** If a resistance be shunted across a condenser it will be found that no steady deflection can be obtained until the condenser is charged.

The effect of shunting the resistance around the condenser has had the practical result of adding capacity to the resistance.

A few experiments with a key, battery and galvanometer will show what the effect would be of adding capacity to a signalling circuit.

As the insulation in a cable acts as a condenser dielectric, the choice of an insulation of little capacity is necessary (see Table IV.)

One of the tests of a cable is to determine its capacity, the other two main tests are as to its insulation and the conductivity of the conductor or core. The insulation of a cable may be that between its core and the earth. Or in the case of a multiple cable having several separate cores, the insulation between these cores.

Where cables are armored with iron or steel wire, or lead covered, the armor or lead covering forms one of the two connections in insulation or capacity tests.

As in most cases, the cable armor or lead sheath is in direct contact with the earth, a connection may be had with the latter. But a good contact on the armor or sheath is preferable.

In testing multiple cables, all the cores not being tested at the time should be grounded. This is done by twisting a bare copper wire around a bared end of each conductor and then to the armor or sheath.

If no very delicate instruments are at hand, all the cores may be so connected or "bunched" omitting the armor connection. An insulation test made between the bunch and the ground will give the multiple insulation of all the cores. This must be less than that of one core as the copper surface to the insulation is so much increased. If a large deflection results, the cores may be thrown off one at a time, watching the deflection. Should it suddenly decrease upon detaching a core from the bunch, trouble is evident in that core.

In preparing core ends for attachment to the testing circuit, much care must be exercised. The insulation should be removed in a tapering form as one would point a lead pencil.

Absolutely no dampness must exist on the insulation or current will be conducted from the copper to the sheath and destroy the value of the test. A good plan is to coat the cable from the copper under the binding posts with hot paraffin.

In testing cables one point will be noticed, the deflections on an insulation test will gradually de-

crease. This is due to electrification of the cable. The insulation apparently improves.

The deflections are generally read after one minute's electrification.

In a multiple cable the actual resistance of each conductor must be worked out and then all the resistances added together. Dividing this by the number of conductors will give the average insulation of the cable.

In speaking of insulation, the cable length must be specified. For instance, if a piece measuring 1000 feet had an insulation of 1000 megohms, a piece only half as long would be 2000 megohms. Its insulation surface and therefore its leakage surface is only one-half.

It is customary to reduce the result to the average per mile. In the foregoing example, the insulation would be 189 megohms per mile.

The rule is to multiply the insulation obtained by the length of the cable reduced to miles or parts of a mile.

In the direct deflection method of testing cable to be described, the same reading should be given whichever terminal of the battery is grounded. The negative terminal of the battery to the cable conductor shows up a fault in a cable quicker than the positive pole for reasons to be given later.

The temperature at which a test of insulation is made is of prime importance. The insulating properties of gutta-percha, rubber and compounds of similar nature decrease very rapidly with in-

crease of temperature. Taking the case of gutta-percha at 50 degrees Fahrenheit as of unit resistance, at 60 degrees it would be less than one-half, at 75 degrees only one-fifth, and at 90 degrees only one-twelfth. With other insulations the decrease of resistance may be even greater than this. It is customary to test cables at 75 degrees Fahrenheit or to correct the readings to that temperature.

Tables of corrections will be found in most large works on testing, such as Kempe's "Hand Book of Electrical Testing," or Hoskaier's "Electrical Testing of Telegraph Cables."

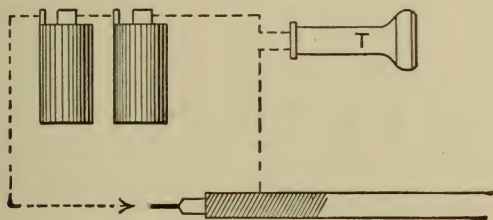


FIG. 83.

**Telephone Test of Insulation.** A simple test of cable insulation may be made with a telephone receiver and battery as in Fig. 83.

One wire makes good connection with the cable armor or lead covering the other wire being touched to the cable core.

Upon making the first contact with the core a click will be heard in the telephone owing to the charge of the cable.

But if the connection be kept closed for a minute or so the cable will be charged.

Subsequent tapping will give no click if the insulation be good. The clicks are of course due to current leaking through the insulation.

**Cable Testing for Insulation Resistance.** In Fig. 84 *B* is a battery, *R* a reversing key, *G* a galvanometer, *S* a shunt box, *C* the cable, *E* an earth con-

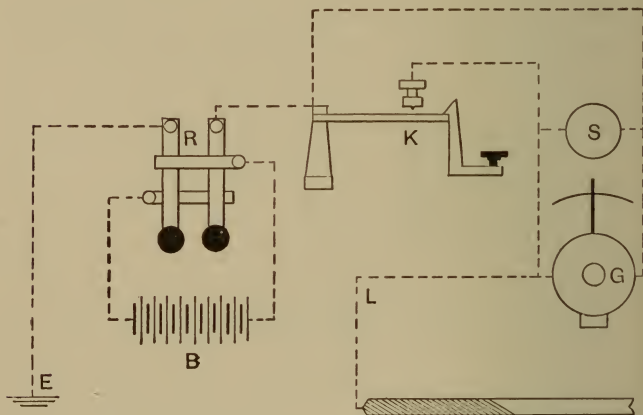


FIG. 84.

nection, *L* a lead from the cable core to the galvanometer connection. *K* is a short circuit key, that is, one which can be left closed to short circuit and cut out the galvanometer and also be opened to cut in the galvanometer.

Before connecting *L* to the cable, test the insulation of *L*. Connect one end as in the figure to

the contact of  $K$ , depress one button of  $R$  and open  $K$ , using a shunt according to the sensibility of  $G$  and strength of  $B$ .

No deflection should appear.

If any deflection deduct it later from readings in testing cable.

Close short circuit key  $K$ ; connect other end of  $L$  to cable and open  $K$ . Any deflection of  $G$  will be due to earth currents.

If the deflections so obtained are in the directions of deflection when battery is used, deduct same from cable readings, if in the reverse direction, add them.

Shunt  $G$  with say  $\frac{1}{100}$  shunt, closing  $K$  and press one button of  $R$ . As long as  $K$  is closed the current all goes into the cable in a similar manner to charging a condenser. After ten seconds, open  $K$ , keeping  $R$  still down and a deflection of  $G$  will ensue.

If off the scale use a higher shunt or reduce battery and repeat charge of cable.

If too small, use lower shunts or increase battery.

Repeat the latter test several times, allowing cable to charge for one minute, noting readings. Then repeat as many more times, but depress other button of  $R$ , reversing battery and deflection.

The values of these readings may be worked out from the galvanometer constant and an average taken to represent the insulation of the cable.

The foregoing cannot necessarily cover every minor point, but the main operations are given.

To sum up: First, obtain the constant of the galvanometer; this operation was described elsewhere. Second, test insulation of the leads. Third, test for earth currents. Fourth, charge cable. Fifth, cut in galvanometer and shunt. Sixth, reverse battery and repeat fifth. Seventh, strike average of readings.

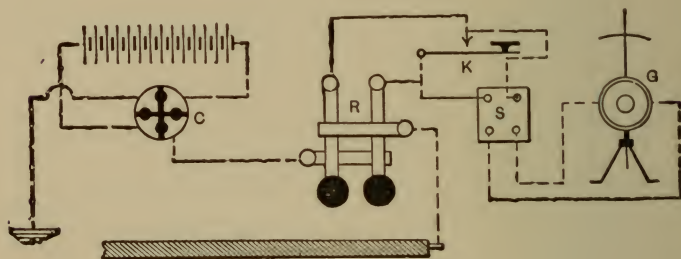


FIG. 85.

Principle allowances to be made are for: shunt, battery, insulation of leads and earth currents.

A slightly different connection for the above test is shown in Fig. 85.

The cable is connected to the reversing key *R*, and a commutator *C* permits of reversing the battery connections, putting either terminal to ground. Or the battery can be cut out entirely and the cable tested for earth currents by directly grounding the connection between *R* and *C*

**Testing Ground Connection.** Connect positive terminal of battery to ground and negative terminal through shunted galvanometer to ground.

Shunt should be so adjusted that deflection is not off the scale. If necessary put resistance in series with galvanometer. Next short circuit ground connection by connecting positive wire to ground wire on galvanometer.

The deflections in each case will show the state of ground connection. The better it is the less difference there will be between the two deflections.

**Cable Insulation with the Willyoung Set K.** The general scheme of this test is in Fig. 87.

The cable is normally grounded by its sheathing or armor and one terminal of the battery is grounded.

The constant of the galvanometer is first calculated by setting the Bridge as in Fig. 86. One cell of battery is used and the shunt arm is on  $\frac{1}{100}$ .

Adjust the rheostat until a deflection of say 10 degrees is obtained.

Multiply the resistance unplugged by the deflections and the multiplying power of the shunt.

In this example let the rheostat be 1800, then  $1800 \times 10 \times 100 = 1,800,000$  ohms. This is the resistance through which the galvanometer is deflected one degree by one cell of battery.

The cable is now connected in as in Fig. 87, to *D*, and a ground connection made from *G r* at the lower left hand side of the case.

Close the battery key for 10 seconds and then close the galvanometer key, the deflections being noted.

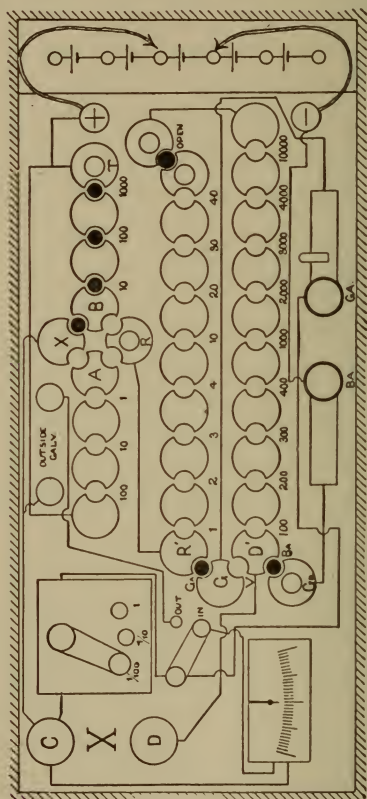


FIG. 86.

The battery has been increased to six cells, therefore the constant is to be multiplied by 6 and divided by the deflection obtained.

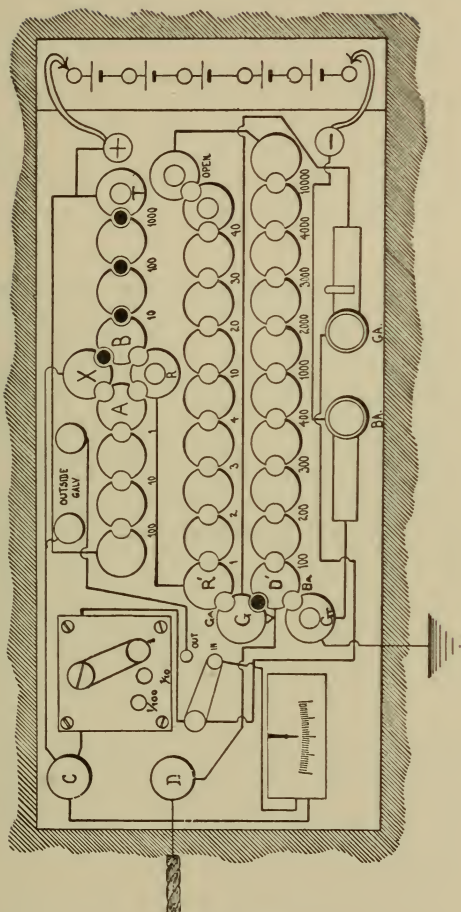


FIG. 87.

Owing to condenser action of the cable there will be a rush of current into the cable at first. It will be well to shunt the galvanometer by the  $\frac{1}{100}$  shunt until the charge of the cable is completed.

By using larger battery increased resistances may be measured.

**Cable Testing by Loss of Charge.** In testing the insulation of cable by the loss of charge method, the cable is charged and discharged, its capacity being compared with that of a standard condenser.

The cable is then charged for one minute and disconnected with its terminal free in the air. This is done by using a key similar to the Kempe discharge key before described.

At the end of one minute, the cable is discharged and the reading noted. Comparison of several such readings show the ability of a cable to retain a charge, *i.e.*, its insulation.

**Formula.** Let  $D$  be the deflection upon instantly discharging the cable,  $d$  that after one minute. Then the percentage of loss of charge will be 
$$\frac{D-d}{D} \times 100$$

In many cases where delicate apparatus is not at hand the loss of charge method can be used for approximate results.

The writer has tested multiple conductor submarine mine cables in New York Harbor with a few cells of dry battery and the galvanometer in a portable testing set.

When the direct deflection method failed owing to want of sensibility in the galvanometer, the difference of deflection made after charge, insulate and discharge gave results.

**Capacity Tests.** The capacity test of a cable is similar to that described in testing condensers.

A standard condenser is charged and discharged and the galvanometer deflections noted. The cable is then substituted for the standard condenser and the deflections noted. Comparison of the two results gives a comparison of the capacity of each.

The calculations are made as in condenser tests.

**Conductivity Tests.** The conductivity of a cable conductor may be measured with a Wheatstone Bridge as in any similar test for conductivity or resistance.

When both ends are available they are connected to the bridge in the usual manner.

If only one end is at hand it is often possible to use a second conductor of the same cable, looping the two together at the distant end. The resistance of one will be then one-half the reading if both are similar in diameter, material and length.

If a ground connection becomes necessary it

must be made with the greatest care that it interposes no undue resistance.

**Locating Faults in Cable.** If the grounded fault were of practically zero resistance and the ground connection between the fault and the battery also of zero resistance, the location of a fault would be easy.

It would then only be necessary to measure the resistance of the cable core up to the fault from both ends of the cable. As the core is of uniform resistance, the two results would be in the same ratio as the lengths of the cable.

For example, let the total length of the cable be 10,000 feet and its total resistance 21 ohms. Measuring from one end *A* the resistance to the fault is 14 ohms. From the other end *B*, the resistance is 7 ohms. Then as 14 is  $\frac{2}{3}$  of 21, the fault would be  $\frac{2}{3}$  of the total length of the cable from *A*. Or 6666 feet from *A* and 3333 feet from *B*, neglecting fractions.

But ground connections or faults rarely fulfil the above condition, in fact they usually vary from time to time. It becomes necessary to use a test such as the Varley or Murray, which disregard the resistance of the fault.

A method of locating a fault as in Fig. 88 may be adopted in certain cases.

A good cable and the faulty one are looped at

the distant end *D*. The resistance of the loop *A B* is then measured by the Bridge method. One  $\times$  terminal of a Bridge being grounded, the other terminal is applied to *A* and the resistance *A F* is measured, and similarly the resistance *B F*. It is evident that both *A F* and *B F* include the resistance of the fault to earth.

The resistances *A F* and *B F* being added together, subtracting the resistance of *A B* will leave twice the resistance of *F* to earth. Twice the resistance because it has been added in both *A F* and *B F*.

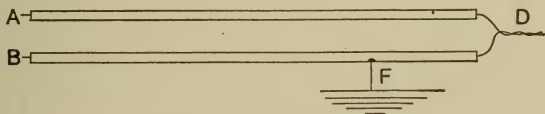


FIG. 88.

If now the resistance of *F* be subtracted from *B F* it will give the resistance of *B* to *F*. Knowing the resistance of the cable per foot the distance can be determined.

EXAMPLE.—Let *A B* measure 22 ohms; *A F* equal 26 ohms, and *B F* 16 ohms. Then  $26 + 16 = 42$ , and less 22 = 20 ohms. One-half this, or 10 ohms, is the resistance of the fault to ground. The resistance of *B F* or 16 ohms less 10 = 6 ohms.

If the cable conductor resistance were 11 ohms per mile, the fault would be  $\frac{6}{11}$  of a mile from *B*, or 2880 feet.

To properly understand the Varley and Murray tests consider a Wheatstone Bridge the arms of which are equal. The rheostat is replaced by a length of cable and the unknown resistance is also replaced by a length of cable, both being similar in resistance per foot.

If both lengths are the same, their resistances are the same, the Bridge balances and no deflection takes place.

Now shorten one length and add resistance  $R$  in series with it until the Bridge again balances,

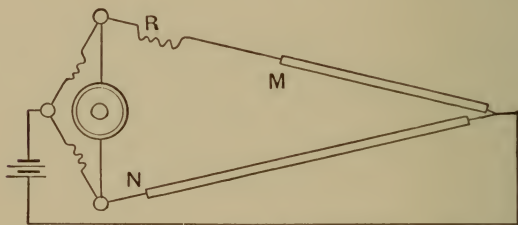


FIG. 89.

Fig. 89. The added resistance equals that of the piece cut off.

If the resistance per foot is known, the length of the shorter piece can be easily calculated.

Instead of connecting in the battery by a wire as shown, use earth connections at each point.

The only result will be to interpose a resistance in the battery circuit. It will not affect the balance but only reduce the effective power of the battery. This may be overcome by enlarging the battery.

Before making the test the copper core resistance of the loop between  $M N$  must be known either by calculation or measurement.

The latter is known as the Varley test, a more complete description is as follows:

**The Varley Test.** In this test for a fault or earth connection the Bridge is connected as in Fig. 90. The battery is grounded and its circuit is completed by the ground at the fault  $F$ . The faulty

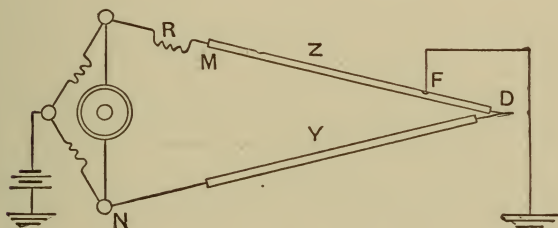


FIG. 90.

cable is looped or connected at its distant end  $D$  with a good cable.

To obtain a balance it is clear that the rheostat  $r$  must be adjusted until its resistance added to that of the cable core between  $M$  and  $F$  together equal the resistance of the core from  $F$  to  $N$ .

It is also clear that the resistance of the ground at  $F$  only reduces the energy of the battery current.

The test is therefore independent of the amount of core exposed to the ground at  $F$ .

**Formula.** Using the letters in Fig. 90, let  $z$  be the resistance of cable from  $F$  to  $M$ ,  $Y$  that of the cable from  $F$  to  $N$ ,  $R$  the resistance of the entire cable loop,  $F$  the resistance of the fault,  $r$  the resistance of the rheostat when galvanometer is balanced.

Then  $Y + z = R$ , and  $Y + F = r + z + F$   
or  $Y = r + z$ .

$Z$  then equals  $\frac{R-r}{2}$ .

The distance  $x$  of the fault from  $M$  is

$$\frac{R}{z} = \frac{L}{x} \text{ or } x = \frac{z L}{R}$$

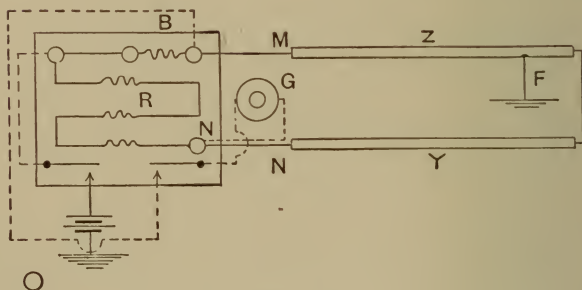


FIG. 91.

**The Murray Test.** This is somewhat similar to the Varley test but one arm of the Bridge is made adjustable. One regular Bridge arm is used, the other being replaced by the rheostat giving an arm of large adjustment.

The circuit is given in Fig. 91.  $B$  is one Bridge arm,  $R$  the rheostat now the second Bridge arm,

$Z$  the faulty cable between  $M$  and the fault  $F$ ,  $Y$  the remainder of the faulty cable and also the good cable in the loop.

The rheostat is adjusted until there is no deflection. From a previous discussion of the Bridge this will be seen to occur when the resistance  $R$  bears the same proportion to  $Y$  as  $B$  does to  $Z$ . Or  $R : Y :: B : Z$ .

Suppose for example only the total length of the loop from  $M$  to  $N$  is 400 feet. Its resistance is 40 ohms. A fault occurs at a distance from  $M$  to be determined.

Arm  $B$  is 100 ohms.  $R$  is adjusted and on balance reads 300 ohms.  $R$  is therefore three times  $B$ .

$Y$  must bear the same proportion to  $R$  that  $B$  does to  $Z$ ; here  $Y$  must be three times  $Z$ .

As  $Y$  and  $Z$  added together equal the whole resistance of the cable,  $Y$  will be  $\frac{3}{4}$  and  $Z$   $\frac{1}{4}$  of this resistance (or length).

$Y$  therefore equals 30 ohms, and  $Z$  10 ohms.

Or if the length is required,  $Y$  is  $\frac{3}{4}$ , that is, 300 feet, and  $Z$   $\frac{1}{4}$  or 100 feet.

**Rule.** To obtain the length of  $Z$  by means of a rule for calculation. The resistance  $B$  is to be divided by  $B$  added to  $R$  and the result multiplied by the length of the cable loop or  $L$ .

Same example,  $\frac{100}{100 + 300} \times 400$  or  $\frac{1}{4} \times 400 = 100$  feet.

**Formula.**  $R : Y :: B : Z$ , or  $\frac{R}{Y} = \frac{B}{Z}$ .

$Z + Y = L$ , then  $Z = L - Y$ .

$x$  or distance of  $F$  from  $M =$

$$\frac{B}{B + R} \times L.$$

**Murray Test with Aone Set.** The layout of the Willyoung testing set for the Murray test is in Fig. 92.

**Formula.** Let  $r$  be resistance of loop,  $Y$  be distance of fault from  $D$ ,  $A$  resistance unplugged in Bridge arm  $A$ ,  $R$  resistance unplugged in rheostat.

$$\text{Then } \frac{R}{A + R} = \frac{Y}{r}, Y = \frac{R r}{A + R}.$$

In fault testing the negative pole of the battery is preferably connected to the cable. If the positive pole be applied and there be a bared spot in the insulation, this bared spot will be acted on by the current, and apparently improved, but the chloride of copper formed is at the expense of the copper core.

**Locating Fault by Unreeling Cable.** In this method two insulated reels are used, or an insulated tank, a galvanometer, battery, etc.

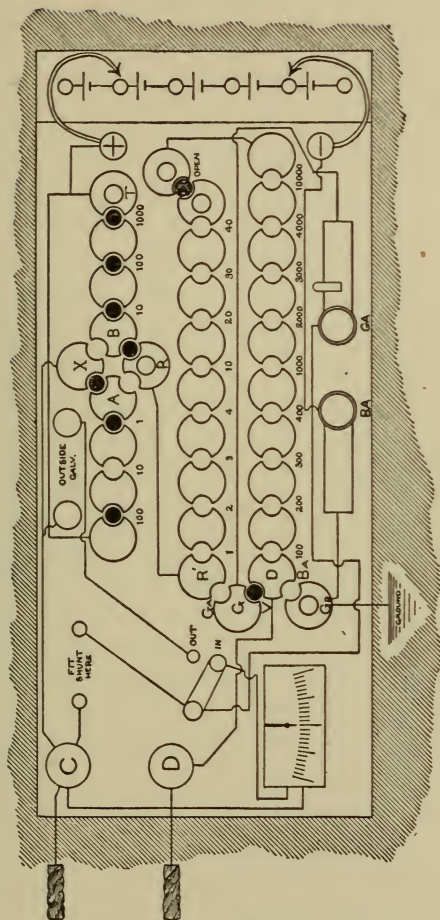


FIG. 92.

One end of the cable conductor is connected to a galvanometer the second terminal of the latter being grounded through a battery.

The cable is wound from one reel to the other, the slack passing through the water in the tank. As soon as a fault reaches the water, the galvanometer will be deflected by the current flowing through the circuit including galvanometer, battery, ground fault and cable.

If an insulated tank is used, the ground connection of battery and galvanometer is made to the water in it.

## CHAPTER XI.

### TESTING WITH VOLTMETER.

**Testing with Voltmeter.** The adaptability of a good portable voltmeter to everyday testing is surprising to those who have not studied it.

There are few tests outside of high resistance tests in cable insulation work that cannot be performed. And even the latter are possible with a sufficiently low reading voltmeter and a large battery.

A voltmeter will do everything that a galvanometer of the same sensibility will, and a great deal more.

The most useful instrument would be a double scale portable having one total scale reading one hundredth that of the other. This together with 50 cells of small but good dry battery and a few standard resistance coils would make a testing set of vast utility.

**Testing Resistance with Voltmeter.** In Fig. 93 is shown the direct deflection method of testing resistance  $R$  with a voltmeter  $V$ .  $S$  is a switch and  $B$  a battery.

The e.m.f. of  $B$  is first noted by moving the switch arm to the left. The arm is then moved to the right, and the e.m.f. through  $R$  noted. The first deflection showed the deflection of  $V$  caused by the battery  $B$  through the resistance of  $V$ . The second deflection was through the resistances of  $R$  and  $V$ . If  $V$  was 10,000 ohms and the first deflection 10 degrees, only one degree of deflection would be obtained through ten times 10,000 or

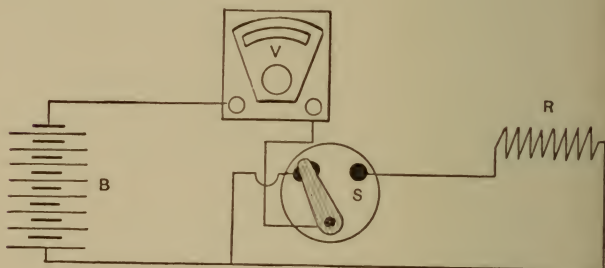


FIG. 93.

100,000 ohms, which latter is the constant for  $V$ . Let the second deflection be 5 degrees. The resistance of  $R$  is therefore  $\frac{100,000}{5}$  or 20,000 ohms, but the resistance of  $V$  must be deducted.  $20,000 - 10,000 = 10,000$  ohms as the resistance of  $R$ .

The constant for the voltmeter may be calculated as above, or a formula may be used for the entire calculation.

**Formula.** In the formula let  $V$  be the first deflection,  $V_1$  the second deflection, and  $r$  be the resistance of the voltmeter,

Then  $\frac{V \times r}{V_1} - r = x$  or the resistance of  $R$ .

For measuring low resistances a low reading voltmeter or a millivoltmeter is preferable if a battery or low e.m.f. be used.

In many cases the current in a power circuit may be used instead of an extra battery.

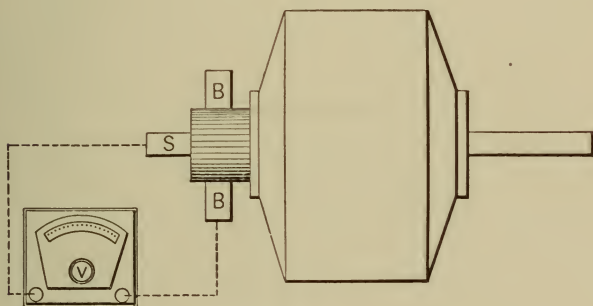


FIG. 94.

**Insulation of Generator with Voltmeter.** In testing the insulation of a generator in operation, connection is made as in Fig. 94 where  $V$  is the voltmeter,  $S$  the shaft or part of the framework, and  $B B$  the brushes.

The generator furnishes its own testing current. The e.m.f. across  $B B$  is first noted, then the e.m.f. from  $B$  to  $S$  and the last formula applied.

Care must be taken that the voltmeter is not affected by the generator and that all connections and contacts are good.

**Insulation Resistance of Armature.** A test of the insulation resistance of the entire armature may be made with the armature removed or disconnected from the fields.

A bare copper wire is wound tightly around the commutator so as to touch all segments. The testing circuit is between the shaft and this copper wire. This will give the combined leakage paths between all coils and segments to the frame.

The copper wire ensures a better contact with all segments. Where the armature coils are in series with each other and tapped to the commutator, no lower insulation will be noted than between one segment and the shaft. That is, providing all armature coil connections are good. The voltmeter should be in circuit with a tap from the mains as in the test for insulation when generator is running.

If the armature is in its place and all field and brush connections complete, the test will show the entire insulation of the machine. Brushes must in the latter case rest on the commutator.

**Testing Electric Light Wiring.** A short circuit on an electric light system generally indicates itself. On the other hand, it may be desired to test the mains for such before cutting in the dynamos.

Testing an extensive system of wiring for short circuits from a main switchboard is a difficult task without having an idea of the lamps, etc., connected to it.

If there were 1000 lamps in multiple between the leads, the resistance might be as low as one-fifth of an ohm.

Such a low resistance between two leads would be a veritable short circuit if it was due to defective insulation. If it is practicable to turn off all lamps first, the matter does not then present much difficulty.

A simple test on a circuit of say 110 volts would be to use an incandescent lamp of the same voltage.

This lamp would be connected between one side of the main being tested and a source of e.m.f., perhaps a dynamo. A wire is run from the other side of the circuit to the other terminal of the dynamo. A short circuit on the main would cause the lamp to light up. Of course the dynamo is to be disconnected from the main by its switch.

If a voltmeter be used instead of the lamp, the actual resistance is determined by simple calculation.

The e.m.f. of the dynamo is to be multiplied by the resistance of the voltmeter and the result divided by the e.m.f. observed when in series with the circuit being tested. Deducting the resistance of the voltmeter the answer is the actual resistance between the two sides of the main.

In either method, the actual location of the trouble is assisted by opening the branch circuit switches on the board one at a time. When the faulty circuit is reached upon opening its switch, the lamp goes out or the voltmeter reading decreases.

The practice of connecting pilot lamps across the circuit at motors and other apparatus is liable to cause perplexity.

A magneto bell would ring easily through one lamp. It would be troublesome to measure low resistances such as one lamp on the voltmeter, as the change of deflection would be slight. The lamp test would therefore be preferable for a short circuit.

A short circuit in a branch leading from a cut out may be hunted for after replacing one of the fuses by a lamp. The lamp will burn until the short circuit is removed. A lamp twisted loose from its base, or a faulty socket is best found by this method.

If the circuit be cut between the fault and the cut-out, the test lamp in the cut-out will cease to burn.

**Measuring Switchboard or Line Insulation.** This method has been before described in the direct deflection tests, except that here one terminal of the voltmeter is grounded.

A brief summary of the test between a switchboard bus and the ground will be given.

Take reading of total e.m.f. of circuit.

Take reading between bus and a ground connection.

Multiply resistance of voltmeter by e.m.f. of circuit, divide result by e.m.f. of bus to ground, and deduct resistance of voltmeter.

Answer will be ohms to ground of opposite bus to one used in calculation.

Should both sides of the circuit be grounded the calculations become vastly more complicated.

When testing one side, the voltmeter will be in multiple with the fault from the side to which it is connected, and vice versa.

And the two ground connections will form a connection between the mains of a resistance equal to the resistance of each ground added together.

If it were possible to disconnect one main from all connection with the other main, the test would be simple. The insulation to ground of each main would be ascertained while the other main was disconnected. But this is not often practicable.

Another method would be to disconnect both main wires from the bus-bars or from the current source, strap them together with a piece of bare copper wire, and measure the insulation to ground as if they were one wire.

This would give the joint insulation-resistance of the main to ground which after all is what is needed most in practice.

**Formula.** Let  $V$  equal e.m.f. of circuit,  $V_1$  e.m.f.

between main to ground,  $R$  resistance of insulation to be ascertained,  $r$  resistance of voltmeter.

$$\text{Then } R = \frac{V \times r}{V_1} - r.$$

In using the voltmeter for measuring resistances there is another method of working which gives the same result.

First deduct the second reading on voltmeter from the first reading. Then divide this result by the second reading and multiply by resistance of the voltmeter.

EXAMPLE. Let e.m.f. of testing circuit or that between mains be 110 volts, resistance of voltmeter 15,000 ohms, reading through resistance ground, etc., be 10 volts. Then  $110 - 10 = 100$ ,  $\frac{100}{10} \times 15,000 = 150,000$  ohms.

Working this by the first method,  $\frac{110 \times 15000}{10} = 165,000$ , deduct 15,000 = 150,000 ohms as before.

The chief advantage of the first method is that a constant can be figured for the particular instrument at a given voltage as described below.

The formula will be for the second method. Let  $V$  be e.m.f. of circuit,  $V_1$  e.m.f. through resistance,  $r$  resistance of voltmeter then

$$\frac{V - V_1}{V_1} \times r = x$$

TABLE V.

Insulation Resistance.

$V_1$ or Voltage through Unknown Resistance.	$V$ or Voltage of Circuit = 110 $r$ or Resistance of Voltmeter = 16,500	$V$ or Voltage of Circuit = 110 $r$ or Resistance of Voltmeter = 17,000.
1	1,798,500	1,853,000
2	891,000	918,000
3	588,500	606,333
4	432,750	450,500
5	346,500	357,000
10	165,000	170,000
20	74,250	76,500
30	44,000	45,333
40	28,875	29,750
50	19,800	20,400
100	1,650	1,700
110	0	0

**Resistance Table for Voltmeter Tests.** Table V. is computed for ready reference in insulation or resistance tests with a Weston voltmeter or other instrument of high resistance.

The first column gives the reading through the resistance, the second and third columns the actual resistance of the insulation.

Both the latter columns are figured for a line e.m.f. of 110 volts and for an instrument resistance of 16,500 and 17,000 ohms respectively.

Where a number of readings have to be made it is handy to figure a constant, that is, multiply the resistance of the voltmeter by the e.m.f. of the circuit.

The result or constant then can be used by simply dividing it by the e.m.f. read with insulation in series and subtracting the resistance of the voltmeter.

**Resistance of Voltmeter.** This may be determined by one of the tests given to find resistance of a galvanometer. The one-half deflection is perhaps the simplest.

Connect voltmeter to a steady e.m.f. and read deflection.

Then add resistance in series with voltmeter until deflection is reduced to one-half. The added resistance will equal resistance of voltmeter.

This is clearly so because the one-half deflection is due to one-half current, and one-half current is due to doubling the resistance of voltmeter. In order to double the voltmeter resistance a resistance has been added which is equal to it.

**Formula.** Let  $V$  represent first deflection,  $V_1$  the one-half deflection,  $R$  resistance of voltmeter,  $r$  resistance added.

$$\text{Then } V_1 = \frac{V}{2} \text{ when } r = R.$$

**Testing e.m.f. around Armature.** There are two methods of testing the distribution of e.m.f. around the armature and determining the equality of the magnetic field.

One is as shown in Fig. 95.  $H$  is an insulating handle carrying two carbon brushes  $A B$  from which run wires  $C D$  for the voltmeter connection.

$A B$  are set just far enough to span the insulation between two commutator segments.

By making contact on the commutator and

gradually moving *H* in the direction of rotation, the e.m.f. is tested at different points in the armature under the influence of various parts of the field.

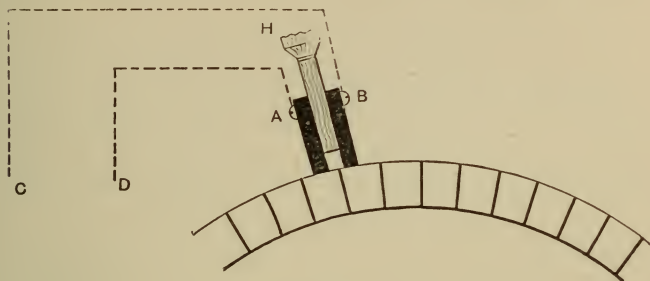


FIG. 95.

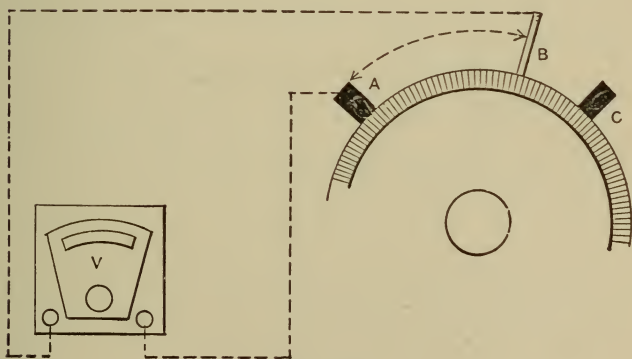


FIG. 96.

These e.m.fs. being plotted on a chart give a graphic record of the distribution of field flux.

Another method is Fig. 96, where one movable brush is used, the other voltmeter connection being on one of the regular working brushes.

This shows a gradual rise or fall of e.m.f. until the total e.m.f. of the generator is reached, but not so readily the actual e.m.f. of any one coil at a time.

**Measuring Drop across a Lamp.** To measure the drop or voltage expended in a lamp while burning the connections should be as in Fig. 97.  $L$  is the lamp,  $V$  the voltmeter and an ammeter  $A$  is shown

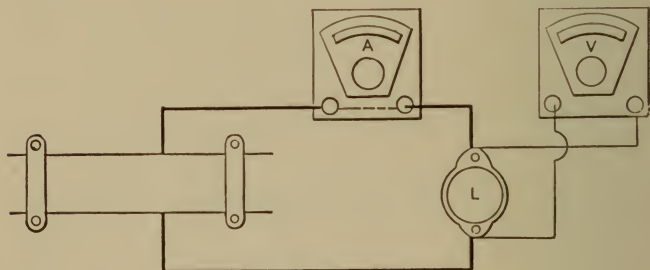


FIG. 97.

so that the current consumption can also be figured. The ammeter also is necessary if the resistance of  $L$  is to be determined.

The drop across  $L$  will be directly indicated by  $V$ . The current shown by  $A$  multiplied by the e.m.f. at  $L$  will give the watts expended in  $L$ .

**Lamp Current Efficiency Test with Voltmeter.** The amount of current taken by an incandescent

lamp on a given voltage depends upon the resistance of its filament.

Comparison of the hot resistance of one lamp with that of a standard lamp will therefore show the current efficiency of the first lamp.

If a low reading ammeter be available the current measurement may be made direct. But such an ammeter is not always at hand.

The drop across each lamp is to be measured with the voltmeter as in Fig. 97.

The e.m.f. indicated in each case will be proportional to the resistance of the lamp. And the current consumption will be in proportion to the resistance of each. The higher the e.m.f. across the lamp terminals, the higher will be its resistance and the lower its current consumption.

The e.m.f. of the testing circuit must be the same in both operations.

This test does not show the true efficiency of the lamp as no data is obtained of the relative candle powers.

And the resistance of  $L$  can be computed by dividing the current reading of  $A$  by the e.m.f. reading of  $V$  or  $R = \left(\frac{E}{I}\right)$ .

Suppose  $V$  reads 100 volts and  $A$  .5 ampere. Then  $100 \times .5 = 50$  watts, and  $100 \div .5 = 200$  ohms.

**Testing a High Voltage with a Low Reading Voltmeter.** This is accomplished by the fall of poten-

tial method. Suppose it is desired to measure the e.m.f. across a circuit of about 550 volts with a voltmeter reading to 150 volts.

Connect five 110 volt lamps  $L$  in series across the circuit, Fig. 98.

Then measure the e.m.f. between  $A B$ ,  $B C$ ,  $C D$ ,  $D E$  and  $E F$  and the sum of these e.m.fs. will equal that between  $A F$ .

Care must be taken that the connections of the voltmeter are made so as to include all parts of the circuit in turn. For instance, when shifting from  $A B$  to  $B C$ , the terminal from  $A$  must be

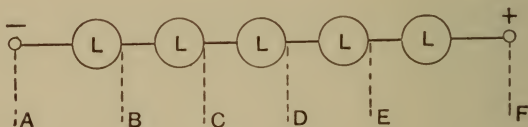


FIG. 98.

placed exactly at  $B$  where the other terminal of the voltmeter was. Or part of the e.m.f. in the wire or connection may be unmeasured, if this be neglected.

*The lamps must all be kept burning during this test, or the voltmeter may be injured.*

**Temperature and Resistance.** In testing coils of wire with their normal current flowing it will be found that the resistance will gradually increase, due to the current flowing in them. This increase is about .004 ohm per degree Centigrade for each

ohm of the coil (see Table VI). This is of very great importance in generator and motor tests. It would reduce the e.m.f. of a shunt generator owing to decreased field current. And it would speed up a shunt motor by reason of decreased field and decreased counter e.m.f.

TABLE VI.

Table Showing Increase in Resistance of Pure Copper Wire for Rise of Temperature above a Given Point.

Centigrade	Increase in ohms per ohm	Centigrade	Increase in ohms per ohm
1	.00389	21	.08169
2	.00778	22	.08558
3	.01167	23	.08947
4	.01556	24	.09338
5	.01945	25	.09725
6	.02334	26	.10102
7	.02723	27	.10503
8	.03112	28	.10894
9	.03501	29	.11281
10	.03890	30	.11680
11	.04279	31	.12059
12	.04669	32	.12450
13	.05051	33	.12837
14	.05447	34	.13226
15	.05835	35	.13615
16	.06225	36	.14061
17	.06613	37	.14593
18	.07030	38	.14782
19	.07391	39	.15171
20	.07780	40	.15575

This table is computed from an average between five authorities. The increase in ohms per ohm shows the fraction of an ohm which a wire one ohm in resistance would increase if its temperature were raised as per column of temperature. The coefficient .00389 is used but for ready calculation; .004 is used in the formulas, there is no absolute standard. To reduce Centigrade to Fahrenheit, multiply by 9, divide by 5, and add 32 to result.

All tests of generator and motor should record the temperature both of the air and machine.

The thermometer used for the air test should lie a few feet from the end of the shaft so as not to be influenced by air currents from a revolving armature.

And of course it should not be near any hot pipes or engine cylinders.

Temperature tests of field coils and armatures may be made with a thermometer laid on the part under test and covered with cotton waste. But such tests do not show heat inside the coils and are unreliable. A more reliable method is by taking advantage of the rise of resistance in the coil due to temperature rise.

The resistance of the coil cold may be measured and recorded. Its resistance is then measured from time to time and the temperature calculated.

For example, let the cold resistance of a shunt field coil be 120 ohms. One-half hour later it is 135 ohms.

This is a rise of 15 ohms, as it is the rise on 120 ohms, the temperature will be  $\frac{15 \text{ ohms}}{120 \text{ ohms}} \div .004$  or 32° C.

A simple way to find the temperature rise is to divide the difference between the cold resistance and the hot resistance by the total resistance cold. Then find the nearest figure in the resistance column of Table VI. Against this will be the temperature. In this example

$135 - 120 = 15$ ,  $\frac{15}{120} = .125$ . In Table nearest is .124 or  $32^{\circ}$  C.

A third method is divide the difference between the two resistances by the cold resistance and multiply by a constant 252 for the Centigrade rise.

Same example.  $.125 \times 252 = 32$ .

The temperature test by resistance shows the average temperature of the coils.

For test of the temperature at specific points, a special device may be prepared.

A strip of mica about two inches square is wound with 200 turns of No. 36 silk covered copper wire.

The strip is then fixed to a convenient handle if desired. This coil may be inserted in crevices between the coils of the armature, etc., its resistance being measured from time to time will give the temperature by computation as before.

**Formula.** Let  $R$  be the cold resistance,  $H$  be the hot resistance,  $t C$  the temperature in Centigrade degrees,  $t F$  the temperature in Fahrenheit degrees.

$$\text{Then } t C = \frac{H - R}{R} \times 252.$$

$$\text{And } t F = \frac{H - R}{R} \times 423.$$

**Testing for a Break in a Coil.** Testing for a break in a field coil of a dynamo or motor may be done by simply connecting a bell and battery in

series with the coil, Fig. 99, and trying if the bell rings. If it rings the circuit of course is complete.

But some field coils are of high resistance in which case a voltmeter, Fig. 100, is substituted for

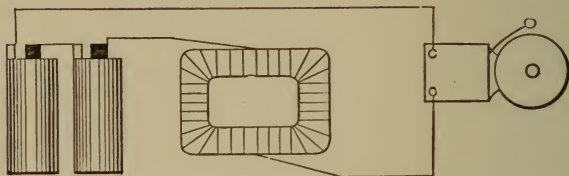


FIG. 99.

the bell. A lead may be taken from an electric light circuit to replace the battery. And if no definite readings are desired an incandescent lamp may replace the voltmeter.

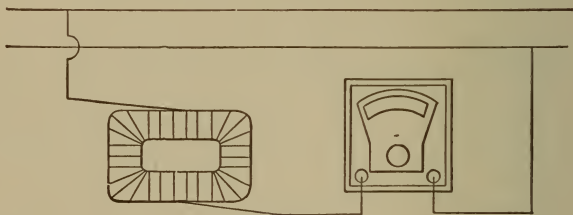


FIG 100.

But the voltmeter method will show the extent of any fault in the circuit or the resistance of the latter. The resistance is calculated from the deflections by the method given elsewhere.

**Testing the Resistance of Coils.** If a number of coils are to be compared, as in a motor or dynamo, they may be tested without disconnecting them other than from the brushes, Fig. 101.

Pass current through the coils as they are in series, using a rheostat  $R$  if necessary, a bank of lamps will answer.

Measure the e.m.f. across the terminals of each coil,  $AB$ ,  $CD$ ,  $EF$  and  $GH$ , and compare the readings; they should all be equal. If not, the

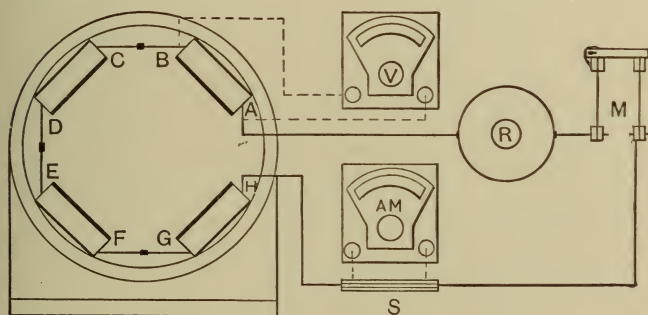


FIG. 101.

low reading coils are short circuited unless the high reading coils are faulty or open.

The actual resistance of each coil can be computed if an ammeter  $AM$  be put in series to give the current value.

By ohms law the resistance will equal the e.m.f. divided by the current or  $R = \frac{E}{I}$ . For example,

if the readings show one ampere and 15 volts, the resistance will be  $\frac{15}{1}$  or 15 ohms.

**Testing Armature Coils.** Armature coils being of low resistance can best be tested by the fall of potential method.

Current from an electric light circuit is passed through a number of coils by connecting the leads to segments situated some distance apart. The exact distance will depend upon the instruments available whether low or high reading. The e.m.f. is then read between segments or from one segment to the others in succession.

A rheostat or lamp bank should be inserted in series with the current leads.

If the e.m.f. between segments is uniform the coils and connections are good.

If a jump occurs at a segment, the voltmeter needle moving a greater distance than usual, a poor connection is probably the cause.

**Testing Armature Resistance.** The connections for this test are in Fig. 102. *S* is a switch connected to a source of current. *A* an ammeter, *V* a millivoltmeter, *L* one or more incandescent lamps for resistance purposes to control testing current. Field wires of a shunt machine are disconnected. Current from *S* passes through the armature coils, ammeter, and resistance lamps.

The connections may be made with copper wire making good contact on commutator segments by inserting them under brushes *B B* of opposite polarity.

The armature is stationary during this test.

The contact must be good, a strip of copper sheet laid flat on the segments is better than a mere wire. The copper strips should be held firmly down on the segments.

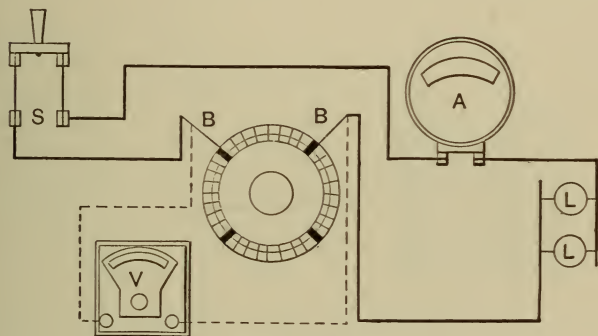


FIG. 102.

Readings are taken of the e.m.f. between the segments to which the connections of the current circuit are made.

Readings are also taken of the current indicated by the ammeter.

Then by ohms law, the resistance equals the e.m.f. divided by the current.

For example, let the current  $I$  be one ampere, the e.m.f. one-tenth of one volt, then one-tenth

divided by one equals one-tenth, or one-tenth of an ohm.

If the armature resistance is so low that a very small reading is given on the millivoltmeter, increase the current flow by adding more lamps in multiple.

The importance of good voltmeter contact at the commutator segments will be seen if a number of tests are made. Improve the contact in each case until no increase of deflection is noted on

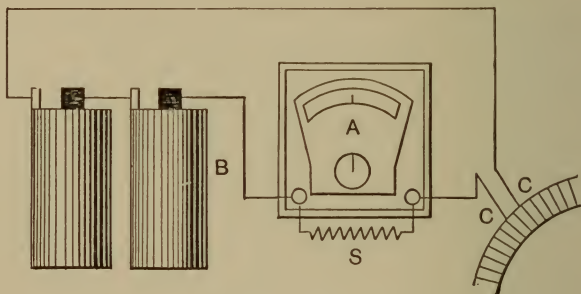


FIG. 103.

voltmeter. The larger the current through the coils the easier the test.

A form of test where an ammeter and battery are used is given in Fig. 103.

The milliammeter *A* is adjusted by means of a shunt *S* to give a large deflection when the terminal leads are short circuited. Its leads are then touched on adjacent segments of the commutator.

The deflections as compared with one another give the comparisons of coil resistance.

If a coil is open or a connection broken, the ammeter will indicate low reading when spanning its segments.

If one coil is partly open, the high resistance at the fault will give a low reading on the ammeter.

If a coil is short circuited, the deflection will be greater than that across a good coil. It will be equal of course to the deflection obtained by touching the ammeter leads together.

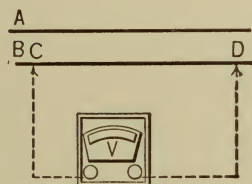


FIG. 104.

**Voltmeter Test of Current in Circuit.** It is often desired to know the current flowing in a lead when it is impracticable to cut the lead and insert an ammeter.

A very close approximation may be made with a low reading voltmeter by measuring the drop along a part of the wire.

The voltmeter is connected between two bared points on the cable as in Fig. 104. The resistance of the cable between these points is read from a table of copper wire resistance. The connections must be made with care and the leads to the in-

strument be large enough to interpose no appreciable resistance.

Take the case of a cable No. 0 B. & S. The resistance per thousand feet is .096 ohm.

The low reading or millivoltmeter is connected across ten feet and a reading observed of 14.4 hundredths of a volt.

As the resistance of ten feet is .00096 ohm, by ohms law  $= \frac{.144}{.00096} = 150$  amperes.

This low reading is perfectly possible on the double scale instruments mentioned at the beginning of this chapter.

Another method would be to measure the e.m.f. across the line at two points. The first would be nearest to the generator or switchboard, the second at the point where the cable branched off to smaller wires.

The difference between the two readings would be due to the loss in the line and the loss beyond the point of second reading.

The loss in the line divided by the computed resistance of the line would give the current flowing.

The line resistance is of course its length multiplied by its resistance per thousand feet. The actual length of wire is to be used, that is twice the distance between the two points.

EXAMPLE. Cable 250 feet between points, in all 500 feet No. 0 B. & S. Resistance .048 ohm. E.m.f. at first point 115 volts at second point 110 volts; loss in line thus 5 volts.

$\frac{E}{R} = \frac{5}{.048}$  or neglecting fraction  $\frac{5}{.05} = 100$  amperes.

The readings must be made as near simultaneously as possible, two adjusted voltmeters will be preferable although not absolutely necessary.

### Corrections in Resistance by "Drop" Methods.

If great accuracy is desired the drop through the voltmeter may be allowed for. The current in the voltmeter will be found by dividing the e.m.f. indicated by the voltmeter resistance. This current is to be deducted from the ammeter readings.

In armatures where the coils are in series but tapped off at commutator segments, the path through the armature coils will be double between brushes. One path is through coils on top section and another path through bottom section coils.

If a coil were open in its windings, current would still flow to the testing instruments by the second path. But a jump of the needle would be shown on the voltmeter when spanning the break.

If a connection between coil and segment were broken, the ammeter would not show any less current except at the instant when the faulty segment was under the brush or connection.

**Plotting Curves.** A graphical method of recording tests is by plotting curves on sectional paper.

In Fig. 105 are shown the readings of e.m.f.

taken half way around the commutator of a bipolar generator.

The figures at the left hand side of the chart are the voltage readings. The figures along the bottom of the chart represent the segment number.

The readings along the horizontal lines are the abscissæ, those up the perpendicular lines, the ordinates.

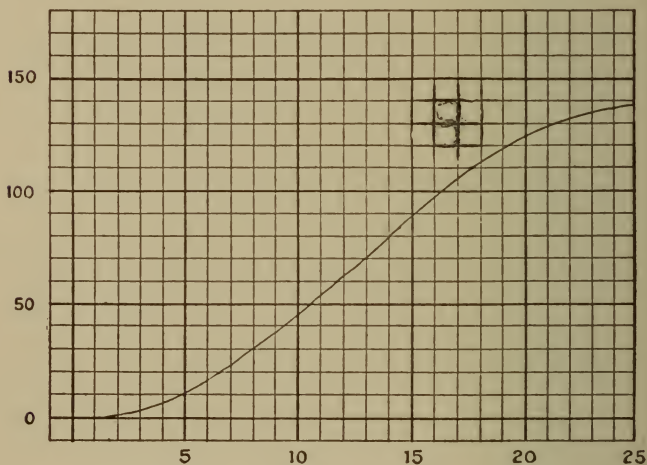


FIG. 105.

In making such a chart, the figures representing the voltage and segment numbers are first marked.

Then as a reading is taken a dot is made at the intersection of the lines representing the e.m.f. and the segment. When the total number of readings is made, the dots are connected by a line running through them.

For example, the first reading between brush and segment 4 is 5 volts, a dot is made on the vertical line corresponding to No. 4 segment, and at the point where a horizontal line from 5 volts would cut it.

A second reading of 10 volts on segment 5 is similarly marked, and another 15 volts at segment 6, and so on.

If the divisions represented by the abscissæ and ordinates are not close enough, computation may be made with a pair of dividers. But cross section paper for such charts is made with 8 and 10 divisions per inch.



## APPENDIX.

---

# Testing Telegraph Wires and Cables and Locating Faults in Telegraph and Telephone Wires and Cables.

BY

JESSE HARGRAVE

*Asst. Electrical Engineer Postal-Telegraph-Cable Company.*

With 28 new Diagrams.



## CHAPTER XII.

### TESTING TELEGRAPH WIRES AND CABLES.

**Early Morning Tests.** All wires leading from each terminal station are tested out regularly every morning not later than seven o'clock for continuity, earth contacts, or "grounds," and crosses. The wire chief simply calls up the distant chief on some wire known to be intact and tries out first one wire and then another until all have been tested. Failing to get the distant station on any particular wire, if it is found that the testing relay fails to open while the distant end stands open, then the wire is in contact with the earth or else mixed with some other wire. If the testing relay remains open while the distant end is to opposite battery pole or to the ground, then the wire is open. If the wire be mixed with some other wire it is usually quickly found out by noticing a disturbance between the two or the development of some other symptom with which the testing chief very soon becomes familiar. Fig. 106 shows the testing relay standing closed to an intermediate ground while the distant end is open.

Fig. 107 shows the testing relay standing open to a break while the distant end is grounded.

When a wire has been found to be grounded or open, each intermediate testing station, beginning at the distant end and proceeding in regular order,

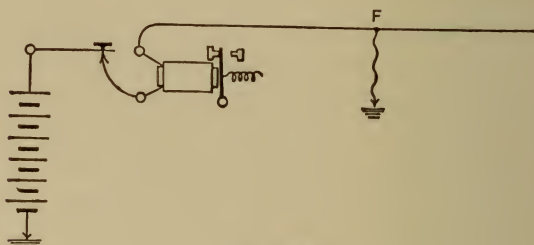


FIG. 106.

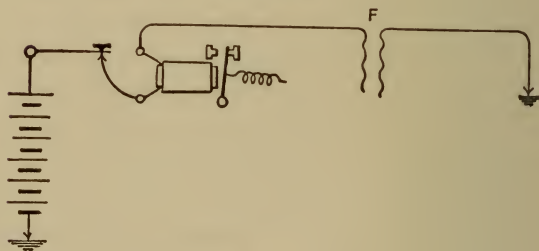


FIG. 107.

is told to open or ground the wire until the location of the fault is definitely determined between stations.

In the case of crossed wires, the distant station is told to open both wires, and a battery is then applied to one, and the other is grounded through the testing relay. If the battery on one wire closes

the relay on the other wire, it is quite obvious that it does so through a cross between the testing station and the distant station's opening. Successive stations are then called up in regular order and told to open the wires until the fault is localized. Fig. 108 shows the testing relay closed through the cross.

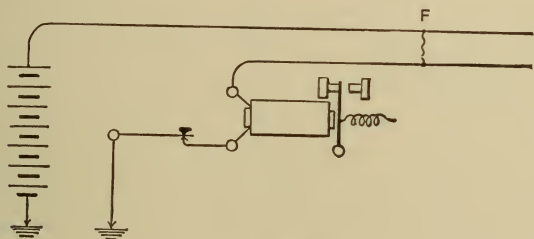


FIG. 108.

**Wrecks.** It frequently happens that all wires become mixed by reason of a tree falling across the line or other cause. Such conditions are known as "wrecks." It usually takes some little time for the wire chief to test the wires out and determine definitely just what conditions exist at the wreck—that is, what wires are crossed with each other, which are open or grounded, etc. The writer has found that the test outlined in Fig. 109 to be the quickest and surest way of testing out such trouble. Each wire in turn is connected to the test relay whose other terminal is connected to ground. All other wires are then opened and a moderately strong battery is placed to one at a time. Those that are

crossed with the wire under test will close the relay the moment the battery is applied to them, provided the wires are not "dead grounded." The spring of

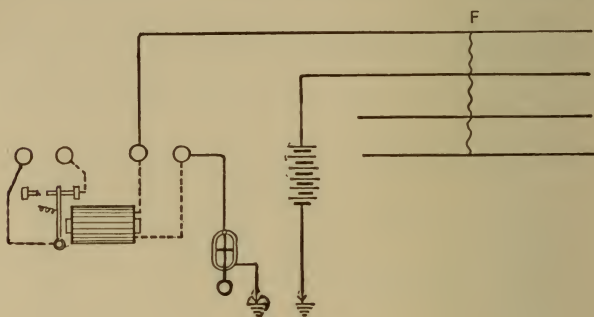


FIG. 109.

#### AUTOMATIC SIGNAL WHEN WIRES COME O. K.

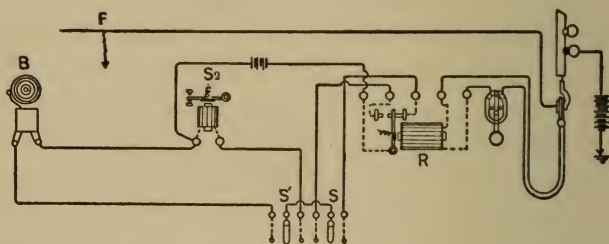


FIG. 110.

relay should be left reasonably slack while this test is being made.

When an "opening" or "ground" is located on a wire by any of the methods described above, it is

customary for the wire chief to order the lineman upon whose section the fault is located to hunt for it, giving all the information possible which will assist him in finding and removing it with the least possible delay. It is then very important that the wire chief know the instant that the wire is cleared of the trouble, and in order to accomplish this result the arrangement outlined in Fig. 110 is much used by one of the large telegraph companies. If the wire be "grounded" the first station beyond  $F$  is instructed to leave it open. Relay  $R$  is then cut into the wire as shown and switches  $S$  and  $S^1$  thrown to the left, which throws bell  $B$  into circuit on back contact of relay  $R$ . So long as the wire remains grounded at  $F$  relay  $R$  remains closed and its armature rests on its front contact, thus leaving the bell circuit open. The moment the lineman removes the ground, however, relay  $R$  opens and rings bell through its back armature contact. The wire chief then reverses both switches, throwing sounder  $S_2$  into circuit on front contact of  $R$ , and proceeds to test out the wire in the usual manner and assign it to a circuit.

Should the wire be open instead of grounded, the distant station is instructed to keep it to his ground, switch  $S$  is thrown to the right and switch  $S^1$  to the left. It will then be seen that the moment the lineman closes the break  $R$  will close to the distant station's ground, thus ringing bell  $B$  through its front contact. Both switches are then placed

to the right, and the chief proceeds to test out the wire in the usual manner.

**Locating Grounds by Wheatstone Bridge Measurements.** When a ground has been located on a wire by the method described above it is often desirable to make a closer and more exact location of it by electrical measurement in order that every facility may be afforded the lineman in finding and clearing the trouble in the shortest possible time. In making this test the Varley loop measurement described in Chapter X is usually employed. A good wire is looped with the faulty one at the next station beyond the fault, as shown in Fig. 90. The mode of procedure is then the same as described under head of "The Varley Test" on pages 157-8. The values of the ratio arms  $A$  and  $B$  are usually made equal and should be that value which more nearly approaches the resistance of the loop under measurement.

For example, if the looped wires measure 400 ohms, then 100 ohms should go in arms  $A$  and  $B$ , whereas if loop measures 600 ohms, then 1000 ohms should be used in the arms of bridge. Great care should be taken in this, as in all other bridge tests, to insure a proper battery strength. If dynamo current be used, a reducing rheostat should invariably be placed in circuit and sufficient resistance should be cut in as to obviate any danger of overheating the coils of the bridge. It is sometimes

advisable to cut a milli-ammeter in circuit with the battery so that a check can be kept on the current entering bridge.

**Measurement for Crosses using Varley Test.** If a good, clear wire is available it should be looped

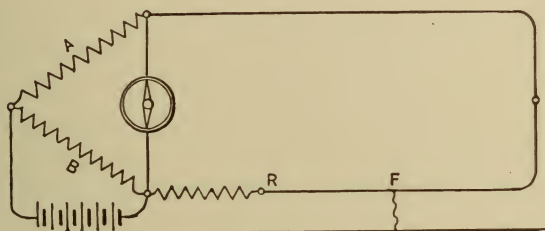


FIG. 111.

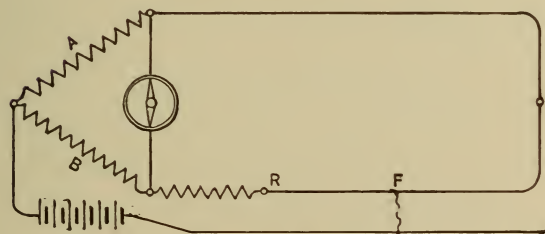


FIG. 112.

with one of the crossed wires at the first convenient station beyond the fault and a measurement made of the loop, as in Fig. 111.

Another measurement is then made as in Fig. 112.

It will be seen that the battery instead of being led to the loop through the distant fault via ground, as is shown in Fig. 90, is carried via the crossed wire to point *F*. It sometimes happens that the end of the second crossed wire is not available for joining on to battery, and in this case the distant station at which the wires have been looped is told to ground the second crossed wire, and the battery is then grounded as in Fig. 113. It should be borne in mind that in this case the earth serves the same purpose of conducting the battery to the loop via the fault as did the second crossed wire in Fig. 112, the path of current being shown by the small arrows.

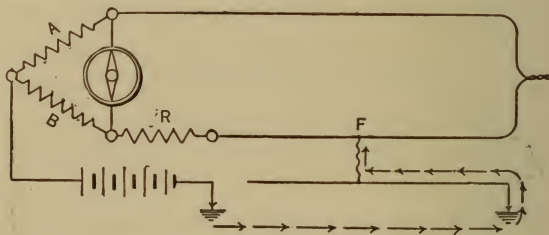


FIG. 113.

The formula for this test is the same as given on page 158, or, boiled down, it is simply  $F = \frac{L - R}{2}$  where  $F$  is resistance to the fault,  $L$  is resistance of loop as per Fig. 111, and  $R$  is result of measurement as per Fig. 112 or Fig. 113. The above is, of course, assuming that equal values are used in

arms  $A$  and  $B$  of bridge, which is almost always the case in measurements of overhead wires. The reason for this is that, as one ohm represents the fractional part of a mile of overhead wire, it is not necessary, except in unusual cases, to obtain closer locations by means of multiplied ratios in arms  $A$  and  $B$ . In No. 9 B. & S. gauge copper wire one ohm represents a little less than a quarter of a mile, whereas in No. 8 gauge iron wire it represents a little less than one-twelfth of a mile.

When the value of  $F$  has been obtained by the above formula it is easy to arrive at the distance by dividing this result by what the wire measures in ohms per mile.

Although the Varley loop test only is spoken of in connection with the foregoing tests for crosses and grounds, yet it will readily be seen that the Murray test described in Chapter X is applicable. The Murray test is preferred by some by reason of its simplicity, especially where the two looped wires are of the same kind and gauge, in which case the initial, or loop, resistance measurement is dispensed with and the result is figured out directly in miles. It should be borne in mind in connection with this test, however, that any chance inequality in resistance of the two wires or imperfect connection or contact at distant stations or elsewhere would disturb its correctness. For this reason it is perhaps safer to figure the result in ohms and then divide by the ohms per mile to get at the distance.

**Measurement for Crosses Using the Two Crossed Wires Only.** A study of Figs. 112 and 113 will soon convince the reader that the resistance of the cross between the two wires can be neglected. So long as it furnishes a path for sufficient current to enter the loop in order to give a readable galvanometer deflection on an unbalanced condition of one or two ohms, then it does not matter whether its resistance be 1 or 1000 ohms so far as affecting the result is concerned. It is this fact which makes this particular measurement so reliable and to be preferred to a simple resistance measurement through the cross.

#### FIRST MEASUREMENT.

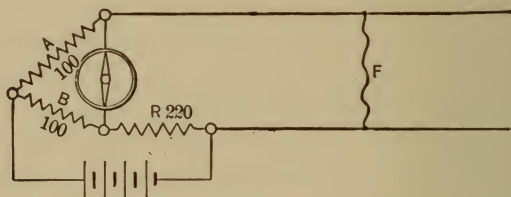


FIG. 114.

When a third good wire is not available for this measurement, however, a reasonably reliable location of the trouble can be made by tests outlined in Figs. 114 and 115. In these tests the resistance of the fault is taken into account, and so long as it does not change between the two tests it does not alter the result.

## SECOND MEASUREMENT.

The simple formula for this test is  $F = \frac{L - r}{2}$ ,

where  $F$  is resistance to fault,  $L$  is result of measurement as per Fig. 114, and  $r$  is result of measurement as per Fig. 115. The explanation of this test is that the resistance necessary in rheostat in Fig. 115 to make a balance simply places point  $X$  at the theoretical center of the loop formed by this resistance and the two wires through  $F$ . It is obvious, then, that to deduct this resistance from the loop measurement of Fig. 114 and then halve the result gives the resistance to point  $X$ .

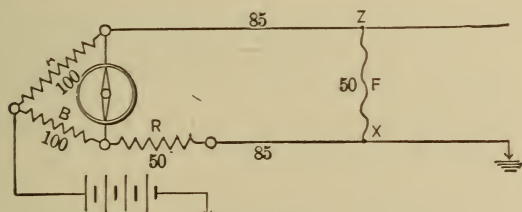


FIG. 115.

If in Fig. 114 we obtain a balance with 220 in  $R$  and in Fig. 115 a balance is obtained with 50, then  $220 - 50$  gives us 170, and this divided by 2 gives us 85 as resistance to  $X$ . Let us further assume that the wires are of the same kind and gauge; then it follows that 85 ohms is also the resistance between  $A$  and  $Z$ , which leaves us 50 ohms for the fault. Then  $50 + 85$  on one side of  $X$  equals  $50 + 85$

on the other side, which balances the system and proves the result to be correct.

Fig. 116 outlines another method of locating a cross by employing the two crossed wires only. In this test it will be seen that the resistance of  $F$  is neglected, but the resistance between wire  $a$  and ground at distant station figures in the result and cannot be accounted for. "Earth currents," or difference in potentials between the earth at points  $Gr$  and  $G$ , would cause considerable error in this measurement, and for this reason it is not recommended, although the writer has at times made use of it with more or less success.

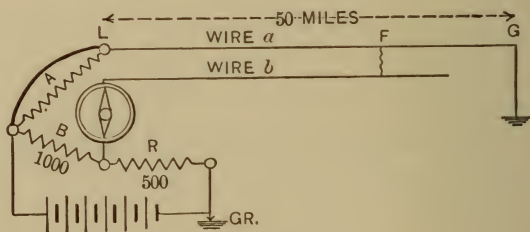


FIG. 116.

In arranging for this test the next distant station beyond fault  $F$  is asked to ground one of the wires, and this wire is connected to point  $L$  of bridge. Arm  $A$  of bridge is then shunted out with a piece of copper wire or else plugged up, and that terminal of galvanometer which normally connects to point  $L$  is detached and connected to the

second crossed wire *b*. It will then readily be seen that that section of wire *a* between *L* and *F* bears the same ratio to the section between *F* and *G* as arm *B* bears to the resistance unplugged in *R* to obtain a balance. It will also be seen that *a* can either be reckoned as having so much ohmic resistance or as being so many miles in length. For example, assuming that the distance to point *G* is 50 miles, then the distance to *F* is  $\frac{50 \times 1000}{1500}$  or  $33 \frac{1}{3}$  miles.

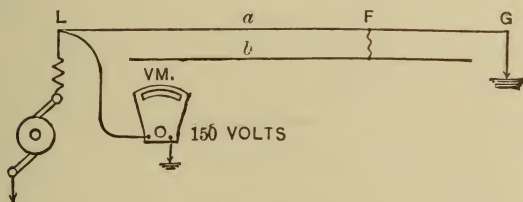


FIG. 117.

**Locating a Cross by Voltmeter Test.** A simple volt-meter measurement for a cross on two wires, but one which is not recommended for its reliability, is outlined in Figs. 117 and 118. Were it not for errors which are likely to arise by reason of earth currents this test would be convenient and useful. The same objections hold against it, however, as are cited against the test described in the foregoing paragraph. A voltmeter of very high resistance is necessary in this test.

If the potential at point  $L$  in Fig. 117 is found to be 150 volts, then it is obvious that there is a gradual drop of 150 volts along wire  $a$  until point  $G$  is reached, where it falls to zero provided  $G$  is a neutral ground and there is no difference of potential between it and the ground at the testing station. It then follows that if the potential has fallen from 150 at  $L$  to 100 volts at fault  $F$ , as indicated in Fig. 118, it has dropped through one-third of its value

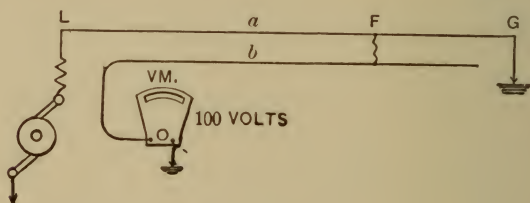


FIG. 118.

between  $L$  and  $G$ , and if the distance between those points be 100 miles it is further obvious that the distance between  $L$  and  $F$  is  $33 \frac{1}{3}$  miles, or

$$\frac{150 \text{ volts} - 100 \text{ volts} \times 100 \text{ miles}}{150 \text{ volts}} = 33 \frac{1}{3} \text{ miles.}$$

It will be noted that the accuracy of this test is affected by the ratio that the resistance of the wire  $b$  between  $F$  and  $VM$  bears to the resistance of  $VM$ . If, however, the resistance of  $VM$  be very high, say sixty thousand or more ohms, then the error due to this cause would be slight. The test, however, is a rough one at best and is not recom-

mended except where the instruments for the other more reliable tests are lacking.

**Insulation Tests—Milliammeter Method.** It is customary to make periodical tests of the insulation resistance of telegraph and telephone wires. Up to a few years ago these tests were made with the tangent galvanometer almost exclusively, but with the advent of direct-reading voltmeters and milliammeters, quicker and in every way more satisfactory methods for making them were found.

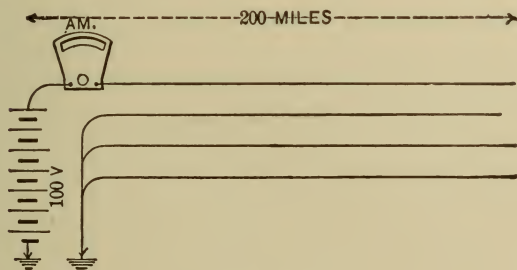


FIG. 119.

The milliammeter furnishes an accurate and ready means of making these measurements, the results of which are directly figured out by Ohm's law. The simple method of making the tests is illustrated in Fig. 119, where the wires are all shown open at the distant station. The wire chief then quickly inserts his meter in first one and then the other, applying an appropriate battery as shown,

until he has run through the entire number on that particular pole line. It will be noted that all wires are grounded except the one under test. This is to not only measure the amount of leakage between the wire under test and earth, but also any leakage which may exist between it and any of the other wires.

The test is ordinarily made with a double-scale milliammeter, employing the most sensitive coil, which usually records on the lower scale. This lower scale is usually calibrated in divisions of .2 milliampere (or .0002 ampere). Referring to Fig. 119, suppose that with a pressure of 100 volts a deflection of 2 divisions on "lower" scale is noted. This would denote that a current of four-tenths of a milliampere (.0004 ampere) was passing out to the "open" wire from 100 volts' pressure. Then,

by Ohm's law,  $R = \frac{E}{I}$ ; hence 100 volts  $\div$  .0004

ampere = 250,000 ohms, which would represent the total insulation resistance of the wire. In considering this test the mileage insulation resistance is always reckoned, and this is arrived at by multiplying the length of the wire in miles by the total or absolute insulation resistance. Assuming that our wire in this instance is 200 miles in length, then the insulation per mile would be 50,000,000 ohms, or 50 megohms.

**Insulation Test by Voltmeter Method.** This test is made in the same manner as described in Fig. 119,

substituting the voltmeter for the milliammeter. The total insulation resistance is arrived at by methods described in Chapter XI, and the mileage insulation resistance is then computed as shown in last paragraph.

When the presence of an abnormal leakage is disclosed by these tests it is customary for the testing chief to localize the same by means of sectional tests; that is, by having successive intermediate stations open the wire for test until the leakage is located between two of them. The lineman who has charge of that section is then ordered to clear it.

**Conductivity Tests.** Conductive resistance tests are for the purpose of checking up joints and connections and, in the case of iron wire, the rate of deterioration from year to year. Some of the big wire companies have these tests made semi-annually, usually in the extremes of temperature, such as in July and January. The wires are looped at the distant station and simple resistance measurements made, such as shown in Fig. 111, for example.

In order to arrive at the exact resistance of each particular wire it is customary to measure three wires in loop combinations three times. For example, suppose we want to arrive at the exact resistance of each of three wires numbered 1, 2, and 3. We loop them in the following order:

$$1 \text{ and } 2 = 400 \text{ ohms.}$$

$$1 \text{ and } 3 = 450 \quad "$$

$$2 \text{ and } 3 = 500 \quad "$$

As each wire has been measured twice, we add the three results and halve their sum. Then if we deduct the result of any one of the three loop measurements from half of the sum of all three results it gives us the resistance of the wire which is not involved in the loop deducted. For example, the sum of the above three measurements is 1350, the half of which is 675. Now, if from this we deduct the loop measurement of 2 and 3, which was 500 ohms, it gives us the resistance of No. 1 = 175; and so, if we deduct the loop measurement of 1 and 3, which was 450, it gives us 225 ohms as the resistance of No. 2, etc.

Any one of the wires whose resistance is thus arrived at may then be used in a loop measurement with any other wire, whose resistance can then be definitely determined.

When the resistance of each wire has been definitely arrived at by the above method, the results are then divided by their length in miles and their resistance per mile recorded, due allowance having been made for all cable in circuit, etc.

Whenever the resistance of any particular wire is found to be abnormally high, sectional measurements are made to determine the location of the added resistance, which usually consists of a bad joint or loose contact. This sectional measurement is accomplished by having successive intermediate stations loop the wires for measurement.

## CHAPTER XIII.

### LOCATING FAULTS IN TELEGRAPH AND TELEPHONE CABLES.

This subject has been pretty thoroughly covered in the chapter on "Cable Testing" and there is little left to be said. There are a few useful points, however, which have not been covered and which it is thought best to call attention to.

**Location of Grounds and Crosses by Varley Method Using Multiplied Arm Ratios.** Telegraph and telephone cables are usually of such short lengths that it is necessary to make very close locations of faults in them in order that the measurements may be of much real value. This is especially true of aerial cables, and more especially true of aerial cables carrying important trunk-line telegraph wires. If trouble on a few of the conductors in such cables can be successfully located and cleared without interrupting the working circuits on the other conductors, then the test becomes of great value.

In order to do this, a multiplied ratio must be used in arms *A* and *B* of bridge in the Varley test. The arm values are usually made 10 in *A* and 1000 in *B*, which gives a ratio of 1 to 100.

In making this test the operator should be very careful that he is getting perfect contacts in all of his bridge connections. If his bridge is of the plug type he should see to it that all plugs and holes are perfectly clean and bright. If there is any sign of oxidization in either, then the plugs should be cleaned with very fine sandpaper, such as 00, and a wooden peg, such as the end of a wooden pen staff, should be forced into each plug receptacle and turned around several times. If a radial-type bridge is used, the stubs should be bright and clean, as should also the under side of the radial arm which makes contact with them. The operator should be

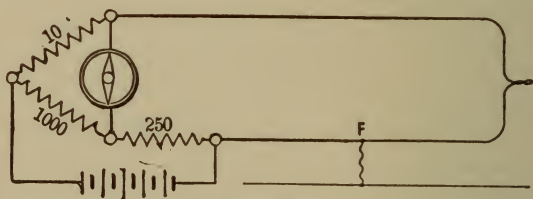


FIG. 120.

absolutely sure that everything is all right before proceeding, and if he does this he will frequently save much extra trouble and annoyance.

Suppose that we have two crossed conductors in a cable 1000 feet long. One of the conductors involved is looped to a good conductor at one end of cable, and a measurement is made from the other

end. A simple loop resistance measurement is first made, as in Fig. 120. Say that our result is 250.

According to the formula for this test,  $r = \frac{A \times R}{B}$ , where  $r$  is the loop resistance,  $A = 10$ ,  $R = 250$ , and  $B = 1000$ . We get 2.5 ohms for our loop.

The connections are then made as in Fig. 121.

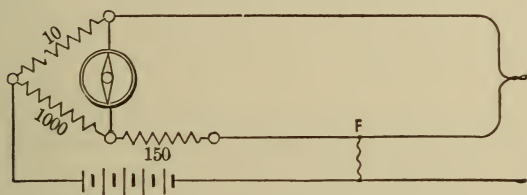


FIG. 121.

If it now takes 150 ohms in  $R$  to effect a balance, then  $F = 2.5 - \frac{(2.5 + 150) \times 10}{1000 + 10} = .99$ , where  $F$  is resistance to the fault. This divided by what the conductor measures per foot would give the distance to the fault.

Let us assume in this instance that our conductor is a No. 14 B. & S. gauge copper wire which measures approximately .0025 ohm per foot at normal temperature. Then our distance to fault would be  $.99 \div .0025 = 396$  feet.

In making this test the operator should invariably verify his measurement by reversing the wires

leading to his bridge and make a third test, seeing whether or not this test checks correctly with the previous one. Fig. 122 shows the connections for this "check" measurement, the formula for which is

$$F = \frac{(L + R) \times A}{A + B}, \text{ or } \frac{(2.5 + 97) \times 10}{1000} = .99, \text{ where}$$

$F$  represents the distance to the fault,  $L$  the loop measurement as in Fig. 120,  $R$  the resistance it takes to balance in this measurement, and  $A$  and  $B$  the arms of the bridge.

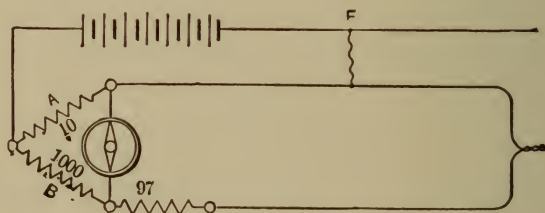


FIG. 122.

It will readily be seen that instead of connecting the battery to the second crossed conductor as shown in Figs. 121 and 122, it could just as well be grounded and then the second crossed conductor grounded, as is shown in the case of overhead-wire measurement, Fig. 113. In cases where the conductors are grounded instead of crossed the measurements are made in the same manner as described above, except that in Figs. 121 and 122 the battery

terminal is grounded instead of being connected to the second crossed wire.

**How to Find Trouble after Located.** It does not, perhaps, belong within the scope of this work to deal with cable faults beyond describing electrical methods necessary in their localization. It might, however, prove helpful to a great many to briefly describe one or two very useful and simple methods of finding the trouble after it has been measured for. This is not so important in the case of underground cables, where it is usually only necessary to know between which manholes the trouble lies. In aerial lead cable, however, it is a matter of considerable importance.

It rarely happens that a cross between two conductors of a lead cable is a solid or metallic one. There is usually a medium of charred paper or carbonized compound which forms the cross. This is equally true of conductors crossed with the lead sheath of the cable. If, now, a current of some considerable volume, say anywhere from 100 to 250 milliamperes, can be made to traverse the cross for any length of time it will be found that the lead sheath will quickly rise in temperature at the point where the trouble exists. It is, therefore, only necessary, after a measurement has been made, to ground one conductor of a crossed pair and apply a grounded source of e.m.f. of 100 or more volts to the other crossed wire, and then have the sheath

examined for a distance of ten or fifteen feet on either side of the point where the measurement placed the fault, until the warm spot is found.

This method has frequently been made use of to great advantage where the sheath of cable bore no sign to indicate the location of the fault. There are comparatively few cases of trouble in aerial lead cable where the method will not work out, and it makes the repairs possible without severing a conductor, the faulty conductors being simply separated, their insulation repaired, and a split sleeve wiped on over the bared section.

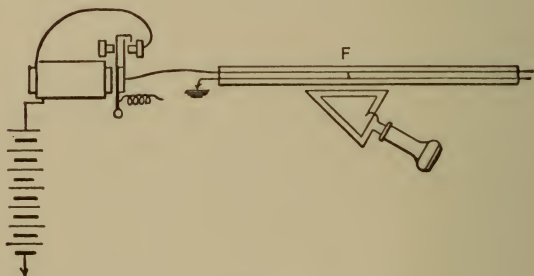


FIG. 123.

Another method which is referred to in some of the text-books (see Young's *Work on Electrical Testing*) is to send a moderately heavy intermittent current into the faulty conductor and then search for the fault by passing a coil of insulated wire in series with a telephone receiver along in close prox-

imity to the sheath. If the current be sufficiently strong, and if the interruptions are of sufficient frequency, then a coil of wire of a conveniently large number of convolutions should pick up enough of the current by induction to produce a noise in the telephone receiver, and this noise should begin to diminish when the point of trouble is passed. Fig. 123 outlines a convenient plan for applying this method.

This method also presents a convenient means of identifying a faulty cable among a number of others in a common subway, or in the case of submarine cables in midstream when they have been brought up by grappling irons.

**Varley Test by Leeds & Northrup's Dial Testing Set.** In this bridge the arms *A* and *B*, instead of consisting of the conventional 10, 100, and 1000 ohm units, are composed of a fixed set of coils so arranged that a radial arm, representing the point of divide and carrying one pole of the battery, in moving about among them creates the usual proportions. The bridge is also arranged so that a throw of certain switches places the organization in position for the Varley, Murray, or simple loop resistance measurement.

It will be noticed in Fig. 124, which shows the theoretical arrangement of the bridge, that there is no chance for imperfect contacts in arms to give rise to multiplied error. The only possible imper-



right let us call the Varley measurement  $R$ , then  $F = \frac{L - DR}{D + 1}$ , where  $F$  is resistance to fault and  $D$  is the ratio dial reading. It will be noticed that this formula is very simple and quickly handled. For example, take the measurement described in Figs. 120, 121, and 122, where for  $L$  we got 2.5 ohms, and for  $R$  we got 150 ohms, then with our ratio arm on the .01 point we would read

$$F = \frac{2.5 - (.01 \times 150)}{.01 + 1}, \text{ or } \frac{1}{1.01} = .99 \text{ ohm.}$$

Fig. 125 shows the actual arrangement of this bridge.

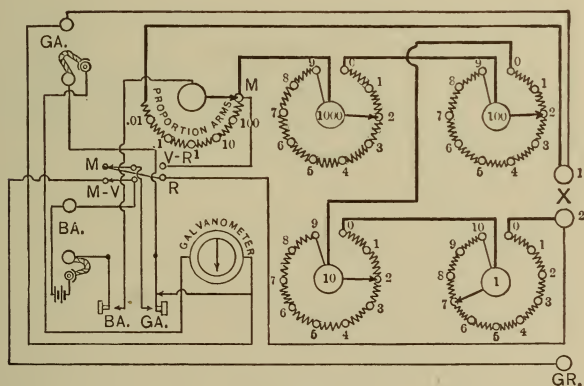


FIG. 125.

### Murray Test with Leeds & Northrup Dial Bridge.

Now let us throw both switches to the right and place arm  $A$  on point  $M$ . If the student will trace

out the connections he will see that the arrangement is identical with that outlined in Fig. 91. It will also be found that we have 1000 ohms, or the entire ratio arms resistance as our fixed ratio factor. If now we obtain a balance on 656 ohms and call this Result  $R$ , then

$$F = \frac{R \times L}{1000 + R}, \text{ or } \frac{656 \times 2.5}{1000 + 656} = .99 \text{ ohm.}$$

**Locating Openings in Cable Conductors by Bridge Method.** Several methods for locating cable conductor openings have been described in different text-books, but the following will perhaps be found to be about the simplest and most reliable:

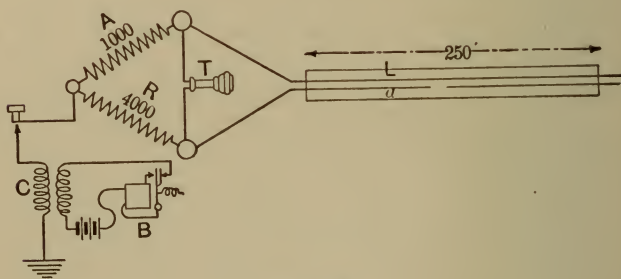


FIG. 126.

In Fig. 126  $A$  and  $R$  are the arms of the bridge,  $R$  being made the rheostat resistance so as to get a wider range of adjustment than would be afforded by the  $B$  arm.  $C$  is a small induction coil, such as is used in telephones.  $B$  is an ordinary buzzer con-

nected in series with the primary of  $C$  and a few cells of dry battery. When a balance is obtained there will be no noise in telephone receiver  $T$ , and  $A$  will then bear the same inverse ratio to  $R$  as  $L$  does to  $a$ , hence the formula

$$F = \frac{A \times L}{R}, \text{ or } \frac{1000 \times 250}{4000} = 62.5 \text{ feet,}$$

where  $F$  equals the distance to opening on conductor  $a$ ,  $L$  the length of conductor and  $R$  the balancing resistance.

Another arrangement for localization of this class of trouble is outlined in Fig. 127.

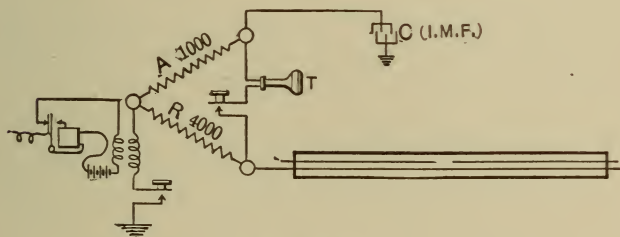


FIG. 127.

In this case  $C$  is a standard condenser, against whose capacity we are measuring the capacity of the good conductor in cable. Let us call the capacity of  $C$  1 M.F. Then say it takes 4000 ohms in  $R$  to balance the system so that there will be minimum noise in  $T$ . Then

$$C' = 1 \times \frac{A}{R}, \text{ or } \frac{1 \times 1000}{4000} = .25 \text{ M.F.}$$

This gives the capacity of the good conductor, and it is then only necessary to find the capacity of the broken conductor up to the break to ascertain how far out the fault lies.

Let us say that a like measurement of the open conductor gives us .125 M.F. and that the cable is 7500 feet long, then it is obvious that our fault is  $\frac{.125}{.250}$  of 7500 feet, or 3750 feet distant.

In order to obviate any error which might arise by reason of a difference in the static capacity of the broken and good conductor it would be well to make a third test involving the good conductor looped to the open one at the distant end. This would give us the capacity of the one that is open beyond the fault. Let us call the result of this measurement .380 M.F.; then it is obvious that the open conductor has a slightly greater capacity per foot than the good one and our formula would be

$$F = \frac{A L}{A + (C - B)} \text{ or } \frac{125 \times 7500}{125 + (380 - 250)} = 3676 \text{ ft.},$$

where  $F$  equals distance to fault,  $A$  equals capacity of open conductor,  $B$  equals capacity of good conductor,  $C$  equals capacity of good conductor looped to open conductor at distant end, and  $L$  equals length of cable.

It will doubtless occur to the reader that tests  $B$  and  $C$  can be dispensed with if the open conductor is measured from both ends.

In order that these tests for open conductors may be accurate it is necessary that the opening be a clean break and clear of escape.

**The Leeds & Northrup Fault Finder.** This instrument has been designed with a view of reducing calculations connected with fault location to a minimum, also so as to simplify the manipulation as much as possible.

It may be used to measure conductor resistance to locate faults by four distinct tests and to locate opens using a buzzer and telephone. (With it a rough measurement can also be made of the resistance of faults so that the operator can decide how closely he should be able to make the location.)

### **Resistance Measurement with the Leeds and Northrup Fault Finder.**

The essential feature of the apparatus is the uniform resistance  $AB$ , which is wound in a circle and is about 100 ohms. By a special construction it is arranged so that contact can be made at any point along it, and it is, therefore, equivalent to a high resistance wire. It has a moving contact  $C$  and a scale of 1000 divisions. In series with this there are the two resistances  $E$  and  $R$ .  $E$  has exactly the same resistance as the wire  $AB$ .  $R$  has a resistance of 100 ohms. Either resistance may be short-circuited by a small switch. The resistances shown

between the ground post and the battery and between post *BA* and the battery key are simply to protect the battery and the apparatus from excessive current. Fig. 128 shows the proper connections for measuring conductor resistance. As in the ordinary slide wire bridge, the resistance *X* between the

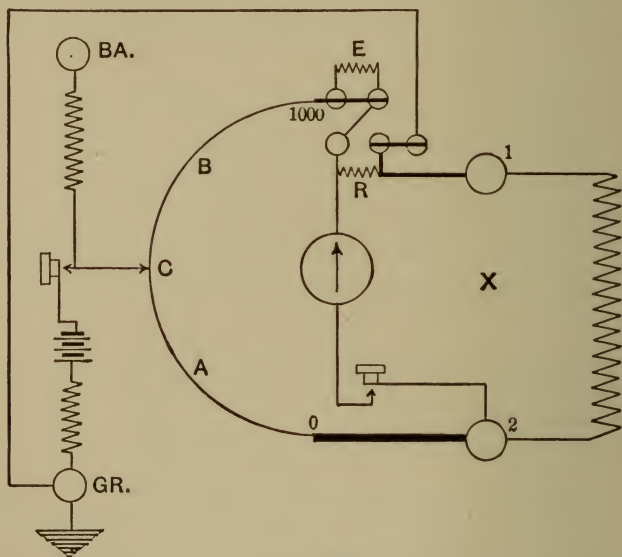


FIG. 128.

two posts 1 and 2 is gotten from the formula  $X = \frac{A}{1000 - A} R$ . To avoid the necessity of solving in each case the fraction  $\frac{A}{1000 - A}$ , a table is furnished with the set, giving the value of this fraction

for each value of  $A$ . The resistance is accordingly determined in each case by simply setting the contact  $C$  for a balance and reading from the table the value opposite the number on the scale and multiplying by 100.

### Fault Location with the Leeds & Northrup Fault Finder.

#### FIRST METHOD.

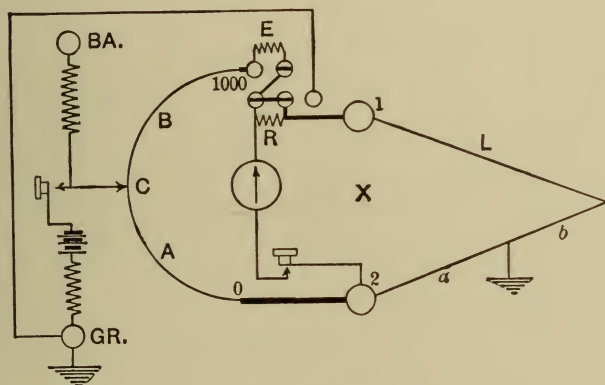


FIG. 129.

This method is to be used in locating faults where there are two wires having equal resistance, in one of which there is a fault. Connect and set switches as shown in Fig. 129. It will be remembered that  $E$  is equal to the resistance of the wire  $AB$ . From the symmetry of the arrangement it will be obvious that the contact point  $C$  would rest for a balance at 1000 on the scale if the fault were exactly at the junc-

tion between the good and the bad wires ; it would rest at 500 if the fault were half way along the bad wire ; and at whatever point it comes to rest, the reading, divided by 1000 and multiplied by the length of the bad wire, is the distance from the instrument to the fault.

## SECOND METHOD.

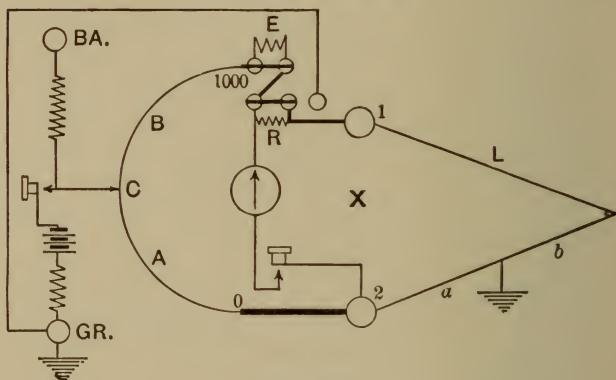


FIG. 130.

This method is to be used for locating faults where the good and the bad wires are not equal to each other. The connections are shown in Fig. 130. It is the ordinary Murray loop, and it will readily be seen that the resistance  $a$  to the fault will be gotten from the formula  $a = \frac{A}{1000} L$ , where  $L$  is the resistance of the loop and  $A$  is the reading of the contact  $C$  on its scale.





value  $\frac{A}{1000 - A}$  can be read from the table. The connections are shown in Fig. 132.

Fig. 133 shows the actual arrangement of the Leeds & Northrup Fault Finder.



## INDEX.

---

<b>Abscissae</b> .....	188
Allowances in cable tests.....	148
Ammeter.....	39
"    checking.....	126
"    connections to equalizer.....	74
"    series .....	39
"    shunt .....	40, 58
"    Thomson.....	64
"    voltmeter used as.....	185
Ampere turns.....	3
Armature coils, resistance of.....	182
"    insulation of.....	166
Arms of bridge.....	81
"    setting of.....	81, 91
Armor connection to ground.....	143
Astatic ammeter.....	67
"    galvanometer.....	9
Automatic signaling device.....	196
Averaging cable tests.....	144, 147
<b>Ballistic</b> galvanometer.....	17
Battery, negative to cable.....	144
"    reversed in cable test.....	147
"    standard.....	38
"    tests of.....	116
Bridge, Wheatstone.....	75
"        "        Leeds & Northrup.....	217
"        "        Post Office.....	78

Bridge, Wheatstone, Queen.....	88
“ “ slide wire.....	95
“ “ Stearns .....	96
“ “ Whitney .....	91
“ “ Willyoung .....	85
<b>Cable,</b> capacity tests.....	153
“ battery in testing.....	144
“ electrification of.....	144
“ faults, the locating of.....	154, 211, 228
“ multiple, testing of.....	144
“ testing.....	142
“ “ allowances in.....	148
“ “ operations.....	148
Capacity, measurement of.....	138
Cardew voltmeter.....	53
Care of instruments.....	73
Calculating shunts.....	28
Cell, Clark.....	38
“ checking e.m.f. of.....	125
“ measuring resistance, etc., of.....	117
“ standard .....	38
“ Weston .....	38
Charge, loss of.....	140
Chart, plotting.....	187
Charging condenser.....	135
Checking ammeter .....	126
“ e.m.f.....	125
“ voltmeter .....	126, 129
Clark cell.....	38
Coil, suspension of.....	12, 20
“ armature, testing.....	166, 182
“ field, testing.....	179
Coils, resistance.....	24
Commutator .....	35
Compensating magnet.....	10

Condenser.....	29, 136
“    adjustable .....	31
“    charge and discharge.....	135
“    comparison of.....	139
Conductivity test .....	209
Constant.....	12, 106
“    deflection .....	109
Copper wire resistance.....	5
Cords for shunt.....	59
Corrections for drop method.....	187
Current, measurement by voltmeter.....	185
Curves, plotting of.....	187
<b>D'Arsonval</b> galvanometer .....	16
Deflection.....	2
“    constant .....	109
“    direct .....	105
Deflections not uniform.....	2, 6
Differential voltmeter.....	50
Dielectrics .....	29, 141
Direct deflection constant.....	12, 106
“    “    method .....	105
Discharge key.....	36, 136
“    of condenser.....	136
Drop across lamp .....	174
“    along line .....	185
Duplex instruments.....	48
<b>Earth</b> or ground connections.....	149
“    currents .....	147
“    influence of.....	9
“    magnetic constant of.....	121
Edgewise voltmeter.....	72
Electrification of cable.....	144
Electro-dynamometer system.....	68
Electro-magnetic system.....	70

Electrostatic system.....	70
E.m.f. around armature.....	173
“ in circuit.....	102
“ testing high with low reading voltmeter.....	175
Equalizer, ammeter connections.....	74
Evershed ohmmeter.....	99
<b>Faults</b> , location of.....	154, 193, 228
Figure of merit.....	12, 106
Field coils, testing.....	179
Fault finder, Leeds & Northrup.....	223
<b>Galvanometer</b> , astatic.....	9
“ ballistic .....	17
“ constant .....	12
“ D’Arsonval .....	16
“ moving coil.....	13
“ resistance of.....	3, 13, 114
“ scale .....	22
“ sensibility .....	12
“ shunts.....	27, 107
“ tangent .....	6, 121
“ Thomson reflecting.....	12
“ wall pattern.....	19
“ windings for.....	4
Generator, e.m.f. around armature.....	173
“ insulation of.....	165
German silver wire.....	25
Ground connection.....	149
<b>Hot wire voltmeter</b> .....	53
<b>Incandescent</b> lamp test.....	174
Inclined coil ammeter.....	64
“ “ voltmeter .....	65
Inductive capacity.....	141

Insulation and length of cable.....	144
“ and temperature.....	144
“ by loss of charge.....	140, 152
“ of cable averaged.....	147
“ of armature.....	166
“ of generator.....	165
“ of line.....	166
“ resistance of cable.....	142
“ test with telephone.....	145
“ “ with milliammeter.....	207
“ “ “ voltmeter .....	208
<b>Kelvin galvanometer</b>	
(See Thomson galvanometer.)	
Key, discharge .....	36
“ Kempe .....	36, 136
“ reversing .....	32
“ rubbing contact.....	35
“ Rymer-Jones .....	34
“ short circuit.....	32
Keystone voltmeter.....	69
<b>Lamp, drop across.....</b>	174
“ efficiency of incandescent.....	174
Line insulation, testing of.....	166
Loss of charge, insulation by.....	140, 152
Location of faults.....	154
Loop tests.....	154
Loss or drop of e.m.f.....	174, 185
<b>Magnet, compensating.....</b>	10
Magnetic vane instrument.....	61
Magnetic influence of earth.....	9, 121
Manganin .....	25
Measuring high e.m.f.....	175
Megohms, calculating in.....	109

Merit, figure of.....	12
Miles, reducing results to.....	144, 201, 205
Milliampere, and meters.....	52
Millivolt, and meters.....	52
Multiple cable testing.....	144
Multiplier for voltmeter.....	51
Multiplying power of shunt.....	29
Murray fault test.....	158, 219
<b>Negative</b> pole of battery to cable.....	144
<b>Ohm's Law</b> , applications of.....	3, 103
Ohmmeter, Evershed.....	99
"    Sage .....	97
Ordinate .....	188
Oscillatory discharge of condenser.....	136
<b>Parallax</b> .....	71
Platinoid .....	25
Platinum silver.....	25
Plotting curves.....	187
Plugs for resistance coils.....	24
Polarized instruments.....	74
Portable sets—see Wheatstone Bridge.	
Positive pole of battery to ground.....	144
Potentiometer .....	123
Potential indicator.....	49, 63
Power of shunt, multiplying.....	29
Proportional arms of bridge.....	81
<b>Queen</b> voltmeter .....	70
"    portable testing set.....	88
<b>Reading</b> instruments.....	71
Reducing result to mile lengths.....	144, 201, 205

Resistance and temperature.....	176
“ of battery.....	117
“ of galvanometer.....	3, 13, 114
“ of copper wire.....	5
“ of voltmeter.....	45
“ slab .....	26
“ testing of.....	104, 113
“ wires .....	24
Reversing battery in cable test.....	144
“ key .....	34
Rheostat .....	3, 23
Rymer-Jones key.....	34
<b>Sage</b> ohmmeter.....	97
Scale, galvanometer.....	22
Sensibility of galvanometer.....	12
Series ammeter.....	39
Shunts, ammeter.....	58
“ “ care of.....	59
“ calculating .....	28
“ galvanometer .....	27
“ multiplying power.....	29
“ use of.....	27, 107
Solenoidal voltmeter.....	61
Standard cell.....	38
Stearns bridge.....	96
Storage battery, instruments for.....	74
Suspension of coil.....	12, 20
<b>Tangents</b> .....	6
Tangent galvanometer.....	6, 121
Telephone, testing with.....	145, 215
Temperature and resistance.....	176
“ “ insulation .....	144
Testing Armature.....	166-172, 182
“ by direct deflection.....	105

Testing by loss of charge.....	140, 152
" cable .....	142, 148, 153, 211, 229
" sunimary of.....	148
" capacity .....	138
" current in lamp.....	174
" drop across lamp.....	174
" earth currents.....	149
" field coils.....	179
" for crosses.....	195, 199, 202, 204
" grounds .....	194, 198, 225
" opens .....	194, 220, 227
" lengths of wire.....	96
" wiring .....	166
" with bridge .....	79, 85, 88, 91
" galvanometer .....	102
" milliammeter .....	207
" ohmmeter .....	97-99
" potentiometer .....	129
" voltmeter .....	163, 205, 208
Thermometer test.....	178
" electric .....	179
Thomson reflecting galvanometer.....	12
" inclined coil ammeter.....	64
Turn, ampere .....	3
 Unreeling, test of cable by.....	 160
 Varley fault test.....	 157, 211, 217
Voltmeter, Cardew .....	53
" checking .....	126, 129
" differential .....	50
" hot wire.....	53
" Keystone .....	69
" mutiplier for .....	51
" principle of.....	39
" Queen .....	70

Voltmeter, low reading and high e. m. f.....	175
“ resistance of.....	39-45-172
“ sensibility of.....	45
“ Thomson .....	64
“ used as ammeter.....	185
“ Westinghouse .....	62
“ Weston .....	41
“ Whitney .....	54
<b>Wattmeter</b> .....	68
Westinghouse voltmeter.....	62
Weston standard cell.....	38
Wheatstone Bridge .....	75
“ “ Leeds & Northrup.....	217, 220
“ “ P. O. form.....	78
“ “ Queen .....	88
“ “ slide wire.....	95
“ “ Stearns .....	96
“ “ Whitney .....	91
“ “ Willyoung .....	85
Wire, resistance of copper.....	5
Wires, resistance.....	24
Wire, testing in lengths.....	96
Wiring, testing of.....	166
<b>Zero, central</b> .....	49, 74
“ method .....	125
“ resistance of fault.....	154



# WESTON

## Electrical Measuring Instruments

The continued development and improvement in the well-known Weston Instruments has resulted in the present practically perfect models.



WESTON STANDARD PORTABLE VOLTMETERS AND AMMETERS are the best instruments available for use in testing circuits.



WESTON LABORATORY STANDARD INSTRUMENTS are the most sensitive and accurate obtainable. They are recognized and used as Standards throughout the world.

LOW PRICED PORTABLE INSTRUMENTS are sold by the Weston Company for use where extreme accuracy is not required. Even in these low priced instruments the usual per-

fection of workmanship peculiar to Weston products is exhibited.

WESTON SWITCHBOARD INSTRUMENTS of the following types: ILLUMINATED DIAL, ROUND PATTERN, EDGEWISE, DUPLEX, in large variety of sizes and ranges are the best made mechanically, as well as electrically. They are unsurpassed in points of low consumption of energy and indicate instantaneously any variation in the circuits.

**Catalogues giving full description of all types of Instruments  
will be mailed promptly upon application to**

## Weston Electrical Instrument Company

MAIN OFFICE AND WORKS,

**Waverly Park, NEWARK, N. J., U. S. A.**

NEW YORK OFFICE, 74 CORTLANDT ST.

# THE LEEDS & NORTHRUP CO.

---

## *Electrical Measuring Instruments*

INCLUDING

## Portable Testing Sets and Cable Testing Apparatus



L. & N. DECADE PORTABLE TESTING SET

Potentiometers  
Standard Condensers  
Standard Resistances  
Conductivity Bridges

Galvanometers  
Self-Induction Apparatus  
Resistance Thermometers  
Dynamometers  
Photometric Apparatus

---

4901 STENTON AVE., PHILADELPHIA

# ELECTRICAL BOOKS.

---

**THE DISEASES OF ELECTRICAL MACHINERY.** By ERNST SCHULZ. Edited with a preface by Sylvanus P. Thompson. Contents of Chapters: 1, *Continuous Current Machines*; breakdowns in the armature; brushes and brush holders; faults in the field winding; faults in the regulator or starter. 2, *Singlephase and Polyphase Generators*; faults in armature; grounds in generators; connections of different phases; field windings. 3, *Singlephase and Polyphase Induction Motors*; stator faults; rotor faults. 4, *Transformers*; faults in winding; effects of lightning. 5, *Efficiency*; examples of efficiency calculations.

94 pages, 42 illustrations, 12mo., cloth, \$1.00.

**ELECTRICAL TABLES AND MEMORANDA.** A valuable little reference book for engineers, electricians, motor inspectors and others interested in the electrical science, containing many tables and much valuable information in a very small space, with a number of illustrations, by PROF. SILVANUS THOMPSON. 64mo., roan, gilt edges, 40c.

**THE VOLTAIC ACCUMULATOR.** By EMILE REYNIER. Contents: Part 1, Principles, definitions, voltmeters. Part 2, Voltaic accumulators of various types. Part 3, Technology. Part 4, Application of accumulators. 202 pages, 62 illustrations, cloth, \$3.00.

**THE MERCURIAL AIR PUMP.** By PROF. SILVANUS P. THOMPSON, D. Sc. 37 pages, 43 illustrations, large 8vo., paper, 60c.‡

**THERMO-ELECTRIC REACTIONS AND CURRENTS, BETWEEN METALS IN FUSED SALTS.** By THOMAS ANDREWS, F.R.S. 18 pages, with illustrations and tables, 8vo., paper, 40c.‡

**THE APPLICATION OF ELECTRICITY TO RAILWAY WORKING.** By WILLIAM EDWARD LANGDON. Contents of Chapters: 1, On the construction of a telegraph line. 2, Surveying. 3, Construction. 4, Telegraph instruments and batteries. 5, Block signalling. 6, Single line working. 7, Automatic block signalling. 8, Interlocking. 9, Miscellaneous appliances in connection with block signalling. 10, Train lighting. 11, Electric light and power. 12, Intercommunication in trains. 13, Administration. Appendix. Index. 301 pages, 5 full page plates and 143 engravings and diagrams, 8vo., cloth, \$5.00.

**ELECTRICAL TESTING OF TELEGRAPH CABLES.** By COL. V. HOSKIAER. Third edition. 12mo., cloth, \$1.50.

**HARD SOLDERING, A MANUAL OF INSTRUCTION IN.** By H. ROWELL, with a chapter on soft soldering and brazing. 12mo., cloth, 75c.

**JUST OUT.**

293 pages, 298 illustrations, 8vo.

Cloth, \$1.00 net.

---

== THE ==  
**MODEL LIBRARY**

---

VOL. I.

Consisting of the following four American books,  
with very complete general index.

**The Study of Electricity and Its Laws**  
for Beginners.

**How to Install Electric Bells, Annun-**  
ciators and Alarms.

**Dry Batteries, How to Make and Use**  
Them.

**Electrical Circuits and Diagrams.** Illus-  
trated and explained.

## 25c. BOOKS.

---

**ELECTRICITY.** The study of, and its laws for beginners, comprising the laws of electric current generation and flow, Ohm's law, galvanism, magnetism, induction, principles of dynamos and motors, wiring, with explanations of simple mathematics as applied to electrical calculations. By N. H. SCHNEIDER. With 55 original illustrations and 6 tables.

**DRY BATTERIES.** A practical handbook on the designing, filling and finishing of dry batteries, with tables, for automobiles, gas engine, medical and coil work, electric bells, alarms, telephones, experiments and all purposes requiring a first-rate battery. Fully illustrated with 30 original drawings.

**ELECTRICAL CIRCUITS AND DIAGRAMS.** Being a selection of original up-to-date and practical diagrams for installing annunciators, alarms, bells, electric gas lighting, telephones, electric power light and wiring circuits, induction coils, gas engine igniters, dynamos and motors, armature windings. By N. H. SCHNEIDER.

**ELECTRIC BELLS AND ALARMS.** How to install them. By N. H. SCHNEIDER. Including batteries, wire and wiring, circuits, pushes, bells, burglar alarms, high and low water alarms, fire alarms, thermostats, annnunciators, and the locating and remedying of faults. With 56 original diagrams.

**MODERN PRIMARY BATTERIES.** Their construction, use and maintenance, including batteries for telephones, telegraphs, motors, electric lights, induction coils, and for all experimental work. By N. H. SCHNEIDER. 94 pages, 55 illustrations. The best and latest American book on the subject.

**EXPERIMENTING WITH INDUCTION COILS.** H. S. NORRIE, author of "Induction Coils and Coil Making." A most instructive little book, full of practical and interesting experiments, fully explained in plain language with numerous hints and suggestions for evening entertainments. Arranged under the following headings: Introduction; The Handling of Ruhmkorff Coil; Experiments with Sparks; Effects in the Vacuum; Induction and Wireless Telegraphy. With 36 original illustrations. [In the press]

**SMALL ACCUMULATORS.** How made and used, by P. MARSHALL. Giving full descriptions how to make all the parts, assemble them, charge the cells and run them, with examples of their practical application. Useful receipts and memoranda and a glossary of technical terms. 80 pages, 40 illustrations, paper.

**ELECTRIC GAS LIGHTING.** How to install Electric gas igniting apparatus including the jump spark and multiple systems for all purposes. Also the care and selection of suitable batteries, wiring and repairs, by H. S. NORRIE. 101 pages, 57 illustrations, paper,

## 25c. BOOKS.

---

**SIMPLE ELECTRICAL WORKING MODELS.** How to make them and how to use them. With 43 illustrations.

**TELEPHONES AND MICROPHONES.** Making and using simple forms of telephones and microphones, with 29 illustrations.

**SMALL ELECTRIC MOTORS.** How to make and use them, including design, examples of small motors, and their applications, speed controllers, starters, fuses, etc. 48 illustrations.

**ELECTRIC LIGHTING** for amateurs. The installation of electric light on a small scale, construction of lamps and lamp holders, switches, batteries and their connections. With 45 illustrations.

**INDUCTION COILS.** A practical handbook on the construction and use of shock and spark coils. With 35 illustrations.

**X-RAYS SIMPLY EXPLAINED.** The theory and practical application of Radiography. 10 illustrations and 6 plates.

**STATIC ELECTRICITY.** Simple experiments in. A series of instructive and entertaining electrical experiments with simple and inexpensive apparatus. With 51 illustrations.

**SIMPLE SCIENTIFIC EXPERIMENTS.** How to perform entertaining and instructive experiments with simple home-made apparatus. With 59 illustrations.

**SMALL ELECTRICAL MEASURING INSTRUMENTS,** describing the making and using of the different instruments fully illustrated.

**SMALL DYNAMOS AND MOTORS.** How to make and use them. A practical handbook, by F. E. POWELL. Contents of Chapters: 1. General Considerations. 2. Field Magnets. 3. Armatures. 4. Commutators and Other Details. 5. Tables of Windings. 6. How to Build a Small Machine. 7. Useful Data. 8. Testing and Repairing. 76 pages, fully illustrated with detail drawings.

**UNIVERSAL TIME CARD MODEL.** By setting to the desired hour at any one place the movable model will show at a glance the actual time of all the other places in the world. Printed in two colors.

## CROSS SECTION BOOKS 25c. each.

**THE HANDY SKETCHING BOOK.** Size 5x8, scale 8 to 1 in.

**THE HANDY SKETCHING PAD.** Size 8x10, scale 8 to 1 in.

**ELECTRICIANS' SKETCHING BOOK.** Size 5x8, scale 10 to 1 in.

**ELECTRICIANS' SKETCHING PAD.** Size 8x10, scale 10 to 1 in.

**PLOTTING PAD.** Size 9x11, scale 16 to 1 in.

# ELECTRICAL INSTRUMENTS— and TESTING.

How to Use the Voltmeter, Ammeter, Galvanometer, Potentiometer, Ohmmeter, the Wheatstone Bridge, and the Standard Portable Testing Sets.

BY

NORMAN H. SCHNEIDER.

Author of "Care and Handling of Electric Plants," "Induction Coils and Coil Making," "Circuits and Diagrams," etc., etc.

---

The aim of the author has been to produce a complete and practical work on this important subject.

First describing the various forms of Electrical Testing and Measuring Instruments and their construction.

Secondly, their practical application to everyday work with numerous examples worked out.

Thirdly, detailing the many tests of insulation resistance, current and e.m.f. that can be made with a voltmeter.

Using only formulas in simple algebra and then explaining them in plain language for the benefit of practical men lacking a knowledge of mathematics.

During the past ten years the author has made hundreds of tests, which has made him familiar with the subject from the practical standpoint. He has also obtained valuable information and diagrams from the principal manufacturers of Testing Instruments. The apparatus described is modern and in universal use.

Most of the diagrams have been specially drawn for this book.

The work is divided into XI. chapters as follows:

Introduction; Chapters I. and II, The Galvanometer; III, Rheostats; IV, The Voltmeter; V, The Wheatstone Bridge; VI, Forms of Portable Sets; VII, Current Flow and e.m.f.; VIII, The Potentiometer; IX, Condensers; X, Cable Testing; XI, Testing with Voltmeter.

230 pages, 105 illustrations and diagrams, 12mo., cloth, \$1.00.

EVERYBODY'S BOOK ON ELECTRICITY.

# PRACTICAL ELECTRICS.

A UNIVERSAL HANDY-BOOK

ON

EVERYDAY ELECTRICAL MATTERS.

---

FIFTH EDITION.

---

## CONTENTS.

*Alarms.*—Doors and Windows ; Cisterns ; Low Water in Boilers ; Time Signals ; Clocks. *Batteries.*—Making ; Cells ; Bichromate ; Bunsen ; Callan's ; Copper-oxide ; Cruikshank's ; Daniel's ; Granule carbon ; Groves ; Insulite ; Leclanché ; Lime Chromate ; Silver Chloride ; Smee ; Thermo-electric. *Bells*—Annunciator System ; Double System ; and Telephone ; Making ; Magnet for ; Bobbins or Coils ; Trembling ; Single Stroke ; Continuous Ringing. *Connections.* *Carbons.* *Coils.*—Induction ; Primary ; Secondary ; Contact-breakers ; Resistance. *Intensity Coils.*—Reel ; Primary ; Secondary ; Core ; Contact-breaker ; Condenser ; Pedestal ; Commutator ; Connections. *Dynamo-Electric Machines.*—Relation of Speed to Power ; Field-Magnets ; Pole-pieces ; Field-magnet Coils ; Armature Cores and Coils ; Commutator Collectors and Brushes ; Relation of size to efficiency ; Methods of exciting Field-Magnets ; Magneto-Dynamos ; Separately excited Dynamos ; Shunt Dynamos ; Organs of Dynamos as constructed in practice ; Field-Magnets ; Armatures ; Collectors ; Brush Dynamo ; Second Class ; Alternate Currents ; Third Class. *Fire Risks.*—The Dynamo ; Wires ; Lamps ; Danger to persons. *Measuring.*—Non-Registering Instruments ; Registering Instruments. *Microphones.*—Construction, &c. *Motors.*—Application ; for Railways. *Phonographs Photophones.* *Storage.*—Plates. *Terminals.*—Charging. *Telephones.*—Forms ; Circuits and Calls ; Transmitter and Switch ; Switch for Simplex.

135 PAGES.

126 ILLUSTRATIONS.

8 VO.

**Cloth, 75 Cents.**

**AN AMERICAN BOOK.**

# **INDUCTION COILS and MAKING.**

Second edition thoroughly revised, greatly enlarged and brought up to latest American Practice,

**BY H. S. NORRIE,**  
(NORMAN H. SCHNEIDER)

---

Considerable space in the new matter is given to the following : Medical and bath coils, gas engine and spark coils, contact breakers, primary and secondary batteries; electric gas lighting; new method of X-ray work, etc. A complete chapter on up-to-date wireless telegraphy; a number of new tables and 25 original illustrations. Great care has been given to the revision to make this book the best American work on the subject. A very complete index, contents, list of illustrations and contents of tables have been added.

## **Contents of Chapters.**

1. Construction of coils; sizes of wire; winding; testing; insulation; general remarks; medical and spark coils. 2. Contact breakers. 3. Insulation and cements. 4. Construction of condensers. 5. Experiments. 6. Spectrum analysis. 7. Currents in vacuo; air pumps. 8. Rotating effects. 9. Electric gas lighting; in multiple; in series. 10. Primary batteries for coils; varieties; open circuit cells; closed circuit cells; solutions. 11. Storage or secondary batteries; construction; setting up; charging. 12. Tesla and Hertz effects. 13. Roentgen Radiography. 14. Wireless telegraphy; arrangement of circuits of coil and coherer for sending and receiving messages; coherers; translating devices; air conductors; tables; contents; index.

**XII + 270 Pages, 79 Illustrations, 5 x 6½ Inches.**  
**Cloth, \$1.00.**

# PRINCIPLES OF ELECTRICAL POWER.

(CONTINUOUS CURRENT.)

FOR MECHANICAL ENGINEERS.

BY

A. H. BATE, A.M.I.E.E.

---

The rapid progress that has been made of late years in the application of electricity to industrial purposes, and particularly in the transmission of power by means of the electric motor, has made it imperative for every engineer who wishes to keep up to date to have some knowledge of the way electrical currents are controlled and used for practical purposes. This work is especially written for the practical engineer, mathematics being avoided.

## Contents of Chapters.

1. The Electric Motor.
2. Magnetic Principles.
3. Electrical Measurements.
4. The Dynamo.
5. Construction of Motor.
6. Governing of Motors.
7. Open and Closed Motors; rating.
8. Motor Starting Switches.
9. Speed Control of Shunt-wound Motors.
10. Series Motor Control.
11. Distribution System.
12. Installing and Connections.
13. Care of Dynamos and Motors.
14. Cost of Plant.
15. Examples of Electric Driving.

Horse-power absorbed by various machines, including general engineering and shipyard machines; wood working and printing machinery (arranged in 14 pages of tables).

**XII + 204 pages, 63 illustrations, 12 mo. cloth. \$2.00.\***

THE PRACTICAL ENGINEER'S HANDBOOK.

TO THE CARE AND MANAGEMENT OF

# ELECTRIC POWER PLANTS

By NORMAN H. SCHNEIDER,

*Chief Engineer, "White City," Colingwood, Ohio.*

## EXTRACTS FROM PREFACE.

In revising the first edition of Power Plants the author decided to greatly enlarge it in the hope that it will have a still greater success than the first one. The section on theory is thoroughly revised. A complete chapter on Standard Wiring including new tables and original diagrams added. The National Fire Underwriters' rules condensed and simple explanations given.

Direct and alternating current motors have been given a special chapter and modern forms of starting rheostats described at length. The principles of alternators have been considered also transformers and their applications. Modern testing instruments and their use are given a separate chapter. New matter has been added to storage batteries including charging of automobile batteries, 10 new tables, and 137 new illustrations.

## SYNOPSIS OF CONTENTS OF CHAPTERS.

1. THE ELECTRIC CURRENT; series and multiple connections; resistance of circuits; general explanation of formulas.
2. STANDARD WIRING; wiring formulas and tables; wiring systems; cut-outs; conduits; panel boxes; correct methods of wiring.
3. DIRECT AND ALTERNATING CURRENT GENERATORS; management in the power house; windings; selection of generators.
4. MOTORS AND MOTOR STARTERS; various forms of motors; controllers; care of motors and their diseases; rules for installing.
5. TESTING AND MEASURING INSTRUMENTS; voltmeter testing and connections; instruments used; switchboard instruments.
6. THE STORAGE BATTERY; different kinds; switchboards for charging fixed and movable batteries; management of battery.
7. THE INCANDESCENT LAMP; various methods of testing; life of lamps.
8. ENGINEERING NOTES; belts and pulleys h.p. of belts. Tables. Contents. Index.

290 pages, 203 illustrations. 12mo., cloth, \$1.50.

Full limp leather, \$2.50.

# Design of Dynamos

BY

SILVANUS P. THOMPSON, D. Sc., B. A., F. R. S.

## EXTRACTS FROM PREFACE.

"The present work is purposely confined to continuous current generators. The calculations and data being expressed in inch measures; but the author has adopted throughout the decimal subdivision of the inch; small lengths being in mils, and small areas of cross-section in sq. mils, or, sometimes, also, in circular mils."

## CONTENTS OF CHAPTERS.

1. DYNAMO DESIGN AS AN ART.
2. MAGNETIC DATA AND CALCULATIONS. Causes of waste of Power. Coefficients of Dispersion. Calculation of Dispersion. Determination of exciting ampere-turns. Example of Calculation.
3. COPPER CALCULATIONS. Weight of Copper Wire. Electrical resistance of Copper, in cube, strip, rods, etc. Space-factors. Coil Windings; Ends; Insulation; Ventilating; Heating.
4. INSULATING MATERIALS AND THEIR PROPERTIES. A list of materials, including "Armialac," "Vitrite," "Petrifite," "Micanite," "Vulcabeston," "Stabilite," "Megohmite," etc. With tables.
5. ARMATURE WINDING SCHEMES. Lap Windings, Ring Windings, Wave Windings, Series Ring-Windings, Winding Formulae. Number of circuits. Equalizing connections. COLORED PLATES.
6. ESTIMATION OF LOSSES, HEATING AND PRESSURE-DROP. Copper Losses, Iron Losses, Excitation Losses, Commutator Losses, Losses through sparking. Friction and Windage Losses. Secondary Copper Losses.
7. THE DESIGN OF CONTINUOUS CURRENT DYNAMOS. Working Constants and Trial Values; Flux-densities; Length of Air-gap; Number of Poles; Current Densities; Number of Armature Conductors; Number of Commutator Segments; Size of Armature (Steinmetz coefficient); Assignment of Losses of Energy; Centrifugal Forces; Calculation of Binding Wires; Other procedure in design. Criteria of a good design. Specific utilization of material.
8. EXAMPLES OF DYNAMO DESIGN.
  1. Shunt-wound multipolar machine, with slotted drum armature.
  2. Over-compounded Multipolar traction generator, with slotted drum armature, with general specifications, tables, dimensions and drawings, fully described.

A number of examples of generators are given in each chapter, fully worked out with rules, tables and data.

VIII.  $\times$  253 pages, 92 illustrations, 10 large folding plates and 4 THREE-COLOR PLATES, 8vo., cloth, \$3.50.

# Dynamo-Electric Machinery

VOL. I.—CONTINUOUS CURRENT.

BY

SILVANUS P. THOMPSON, D.Sc., B.A., F.R.S.

---

7th Edition Revised and Greatly Enlarged.

---

## CONTENTS OF CHAPTERS.

1. Introductory. 2. Historical Notes.
  3. Physical Theory of Dynamo-Electric Machines.
  4. Magnetic Principles; and the Magnetic Properties of Iron.
  5. Forms of Field-Magnets.
  6. Magnetic Calculations as Applied to Dynamo Machines.
  7. Copper Calculations; Coil Windings.
  8. Insulating Materials and their Properties.
  9. Actions and Reactions in the Armature.
  10. Commutation; Conditions of Suppression of Sparking.
  11. Elementary Theory of the Dynamo, Magneto and Separately  
Excited Machines, Self-exciting Machines.
  12. Characteristic Curves.
  13. The Theory of Armature Winding.
  14. Armature Construction.
  15. Mechanical Points in Design and Construction.
  16. Commutators, Brushes and Brush-Holders.
  17. Losses, Heating and Pressure-Drop.
  18. The Design of Continuous Current Dynamos.
  19. Analysis of Dynamo Design.
  20. Examples of Modern Dynamos (Lighting and Traction).
  21. Dynamos for Electro-Metallurgy and Electro-Plating.
  22. Arc-Lighting Dynamos and Rectifiers.
  23. Special Types of Dynamos; Extra High Voltage Machines,  
Steam-Turbine Machines, Extra Low Speed Machines, Exciters,  
Double-Current Machines, Three-Wire Machines, Homopolar (Uni-  
polar) Machines, Disk Dynamos.
  24. Motor-Generators and Boosters.
  25. Continuous-Current Motors.
  26. Regulators, Rheostats, Controllers and Starter.
  27. Management and Testing of Dynamos.
- Appendix, Wire Gauge Tables. Index.

996 pages, 573 illustrations, 4 colored plates, 32 large folding  
plates. 8vo., cloth. \$7.50.†

# Alternating - Current Machinery

BEING VOL. II OF

## DYNAMO-ELECTRIC MACHINERY.

BY

SILVANUS P. THOMPSON, D.Sc., B.A., F.R.S.

---

Owing to the enormous increase in the use of electrical machinery since the publication of the sixth edition of DYNAMO-ELECTRIC MACHINERY the author has deemed it advisable to divide the work. Vol. I. is devoted to DIRECT CURRENT MACHINERY and this the second part. Vol. II. ALTERNATING CURRENT MACHINERY. Amongst the many new features treated special mention must be made of the number of fine colored plates of windings and the many large folding scale drawings. These two volumes make the most comprehensive and authoritative work on dynamo machinery. The work has been so universally adopted that it has been found necessary to translate it into French and German.

### CONTENTS OF CHAPTERS.

1. Principles of Alternating Currents.
  2. Periodic Functions.
  3. Alternators.
  4. Induced E.M.F. and Wave-Forms of Alternators.
  5. Magnetic Leakage and Armature Reaction.
  6. Winding Schemes for Alternators.
  7. Design of Alternators. Compounding of Alternators.
  8. Examples of Modern Alternators.
  9. Steam Turbine Alternators.
  10. Synchronous Motors, Motor Generators, Converters.
  11. Parallel Running of Alternators.
  12. Transformers.
  13. Design of Transformers.
  14. Induction Motors.
  15. Design of Induction Motors.
  16. Examples of Induction Motors.
  17. Single-Phase Induction Motors.
  18. Alternating-Current Commutator Motors.
- Appendix. The Standardization of Voltages and Frequencies.  
Complete Index.

XX+848 pages, 546 illustrations, 15 colored plates and 24 large folding plates. 8vo., cloth. \$7.50 $\frac{1}{2}$ .

# Books for Steam Engineers.

---

**DIGRAM OF CORLISS ENGINE.** A large engraving giving a longitudinal section of the Corliss engine cylinder, showing relative positions of the piston, steam valves, exhaust valves, and wrist plates when cut-off takes place at  $\frac{1}{4}$  stroke for each 15 degrees of the circle. With full particulars. Reach-rods and rock shafts. The circle explained. Wrist-plates and eccentrics. Explanation of figures, etc. Printed on heavy paper, size 13 in. x 19 in., **25c.**

**THE CORLISS ENGINE** and its Management. A Practical Handbook for young engineers and firemen, (3rd edition) by J. T. HENTHORN. A good little book, containing much useful and practical information. **Illustrated, cloth, \$1.00.**

**THE FIREMAN'S GUIDE** to the Care and Management of Boilers, by KARL P. DAHLSTROM, M.E., covering the following subjects: Firing and Economy of Fuel; Feed and Water Line: Low Water and Priming: Steam Pressure: Cleaning and Blowing Out; General Directions. A thoroughly practical book. **Cloth, 50c.**

**A B C OF THE STEAM ENGINE.** With a description of the automatic shaft governor, with six large scale drawings. A practical handbook for firemen helpers and young engineers, giving a set of detail drawings all numbered and lettered and with names and particulars of all parts of an up-to-date American high speed stationary steam engine. Also a large drawing and full description of the automatic shaft governor. With notes and practical hints. This work will prove of great help to all young men who wish to obtain their engineer's license. **Cloth, price 50c.**

**HOW TO RUN ENGINES AND BOILERS.** By E. P. WATSON, (for many years a practical engineer, and a well-known writer in *The Engineer*.) A first-rate book for beginners, firemen and helpers. Commencing from the beginning, showing how to thoroughly overhaul a plant, foundations, lining up machinery, setting valves, vacuum, eccentrics, connection, bearings, fittings, cleaning boilers, watertube boilers, running a plant, and many useful rules, hints and other practical information; many thousands already sold. **160 pages, fully illustrated, cloth, \$1.00.**

**AMMONIA REFRIGERATION.** By I. I. REDWOOD. A practical work of reference for engineers and others employed in the management of ice and refrigerating machinery. A first-rate book, beginning from the bottom and going carefully through the various processes, stage by stage, with many tables and original illustrations. **Cloth, \$1.00.**

**MEYER SLIDE VALVE.** Position diagram of cylinder with cutoff at  $\frac{1}{8}$ ,  $\frac{1}{4}$ ,  $\frac{3}{8}$  and  $\frac{1}{2}$  stroke of piston with movable valves, on card  $7\frac{1}{2}$  in. x  $5\frac{1}{2}$  in. **Price, 25c.**

AN ELEMENTARY TEXT-BOOK  
ON  
STEAM ENGINES AND BOILERS,  
FOR THE  
USE OF STUDENTS IN SCHOOLS AND COLLEGES.  
BY  
J. H. KINEALY.

*Professor of Mechanical Engineering, Washington University.*

---

Illustrated with Diagrams and Numerous Cuts, Showing American Types  
and Details of Engines and Boilers.

---

This book is written solely as an elementary text-book for the use of beginners and students in engineering, but more specially for the students in the various universities and colleges in this country.

No attempt has been made to tell everything about any one particular subject, but the author has endeavored to give the student an idea of elementary thermodynamics, of the action of the steam in the cylinder of the engine, of the motion of the steam valve, of the differences between the various types of engines and boilers, of the generation of heat by combustion, and the conversion of water into steam.

Care has been taken not to touch upon the design and proportion of the various parts of engines and boilers for strength; as, in the opinion of the writer, that should come after a general knowledge of the engine and boiler has been obtained.

In the derivation of some of the formulæ in thermodynamics, it has been necessary to use the calculus, but the use of all mathematics higher than algebra and geometry has been avoided as much as possible.

An earnest endeavor has been made to present the subject in a clear and concise manner, using as few words as possible and avoiding all padding.

CONTENTS OF CHAPTERS.

Chapter I.—Thermodynamics; First Law of Thermodynamics; Work, Power; Unit of Heat; Mechanical Equivalent; Application of Heat to Bodies; Second Law of Thermodynamics; Specific Heat; Absolute Temperature; Application of Heat to a Perfect Gas; Isothermal Expansion; Adiabatic Expansion; Fusion; Vaporisation; Application of Heat to Water; Superheated Steam. Chapter II.—Theoretical Heat Engine; Cycle; Thermodynamic Efficiency; Perfect Gas Engine; Perfect Steam Engine; Theoretical Diagram of the Real Engine; Clearance; Efficiency

# THE SLIDE VALVE

SIMPLY EXPLAINED.

By W. J. TENNANT, Asso. M. Inst. Mech. E.

The work has been thoroughly revised and enlarged  
in accordance with the present American Practice.

By J. H. KINEALY, D. E., M. Am. Soc. Mech. E.

---

The work is based upon notes and diagrams which were prepared by Mr. Tennant in his lectures to his classes of working engineers and students towards the obtainment of clear *general* notions upon the Slide Valve, its design, varieties, adjustments and management. They have been revised and considerably added to and in this form the authors believe they will be of considerable value to all engineers and others interested in steam engines.

---

## CONTENTS OF CHAPTERS.

- I. The Simple Slide.
- II. The Eccentric a Crank. Special Model to give Quantitative Results.
- III. Advance of the Eccentric.
- IV. Dead Centre. Order of Cranks. Cushioning and Lead.
- V. Expansion—Inside and Outside Lap and Lead; Advance affected thereby. Compression.
- VI. Double-ported and Piston Valves.
- VII. The Effect of Alterations to Valve and Eccentric.
- VIII. Note on Link Motions.
- IX. Note on very early cut-off, and on Reversing Gears in general.

The illustrations aim to cover the different kinds of Slide Valves, and the circular diagrams will prove a novel feature.

**88 Pages.    41 Illustrations.    12mo.    Cloth, \$1.00**

# LUBRICANTS, OILS AND GREASES.

TREATED THEORETICALLY AND GIVING PRACTICAL  
INFORMATION REGARDING THEIR

## COMPOSITION, USES AND MANUFACTURE.

*A PRACTICAL GUIDE FOR MANUFACTURERS, ENGINEERS,  
AND USERS IN GENERAL OF LUBRICANTS.*

By ILTYD I. REDWOOD,

Associate Member American Society of Mechanical Engineers; Member Society Chemical Industries (England); Author of 'Theoretical and Practical Ammonia Refrigeration,' and a 'Practical Treatise on Mineral Oils and Their By-Products.'

---

### CONTENTS.

INTRODUCTION.—Lubricants.

#### THEORETICAL.

CHAPTER I.—Mineral Oils: American and Russian; Hydrocarbons.

CHAPTER II.—Fatty Oils: Glycerides; Vegetable Oils; Fish Oils.

CHAPTER III.—Mineral Lubricants: Graphite; Plumbago.

CHAPTER IV.—Greases: Compounded; "Set" or Axle; "Boiled" or Cup.

CHAPTER V.—Tests of Oils: Mineral Oils. Tests of Oils: Fatty Oils

#### MANUFACTURE.

CHAPTER VI.—Mineral Oil Lubricants: Compounded Oils; De-bloomed Oils.

CHAPTER VII.—Greases: Compounded Greases; "Set" or Axle Greases; Boiled Greases; Engine Greases.

APPENDIX.—The Action of Oils on Various Metals. Index.

TABLES: I.—Viscosity and Specific Gravity. II.—Atomic Weights. III.—Origin, Tests, Etc of Oils. IV.—Action of Oils on Metals.

LIST OF PLATES: I.—I. I. Redwood's Improved Set Measuring Apparatus. II.—Section Grease Kettle. III.—Diagram of Action of Oils on Metals.

8vo. Cloth, \$1.50.

# Mechanical Draft.

BY

J. H. KINEALY, M. Am. Soc. M.E.

*Past President American Society Heating and Ventilating Engineers.*

---

## PREFACE.

In writing this book the author has assumed that those who will use it are familiar with boilers and engine plants, and he has had in mind the practicing engineer who is called upon to design power plants, and who must therefore decide when it is best to use some form of mechanical draft. The arrangement of the book is what the experience of the author in making calculations for mechanical draft installations has shown him is probably the best. And he has tried to arrange the tables in such a way and in such a sequence that they may prove as useful to others as they have to him.

## CONTENTS OF CHAPTERS.

1. GENERAL DISCUSSION. Introduction; systems of mechanical draft; chimneys v. mechanical draft; mechanical draft and economizers.

2. FORCED DRAFT. Systems; closed fire-room system; closed ashpit system; small fan required; usual pressure; forced draft and economizers; advantages; disadvantages.

3. INDUCED DRAFT. Introduction; temperature of gases; advantages; disadvantages.

4. FUEL AND AIR. Weight of coal to be burned; evaporation per lb. of coal; effect of rate of evaporation; weight of air required; volume of air and gases; volume of gases to handle; leakage; factor of safety.

5. DRAFT. Relation to rate of combustion; resistance of grate; resistance due to economizer; draft required under different conditions.

6. ECONOMIZERS. Effect of adding; ordinary proportion and cost; increase of temperature of feed water.

7. FANS. Type and proportions of fan used; relation between revolution of fan and draft; capacity of fan.

8. PROPORTIONING THE PARTS. Diameter of fan wheel required; speed at which the fan must run; power required to run the fan; size of engine required; steam used by fan engine; choosing the fan for forced draft, for induced draft without economizer, for induced draft with economizer; location of the fan; breeching and up-take; inlet chamber; discharge chimney; by-pass; water for bearings.

Appendix. Tables. Index. 156 pages. 13 plates. 16mo.

Cloth, \$2.00.

THE AUTHORITY ON THIS SUBJECT.

# CENTRIFUGAL FANS.

A THEORETICAL AND PRACTICAL TREATISE ON  
Fans for Moving Air In Large Quantities  
At Comparatively Low Pressures.

BY

J. H. KINEALY, M. Am. Soc. M.E.

Past-President American Society Heating and Ventilating Engineers.

The matter in this book was a series of articles written for the *Engineering Review*. The favorable attention which they attracted lead the author to believe that there was a real demand for a book treating in a theoretical as well as a practical way on centrifugal fans. The articles have been thoroughly revised, added to, and made as complete as possible.

## Contents of Chapters.

1. Flow of Air; Volume of Air Flowing; Pressure Necessary for required velocity.
2. Vortex; Vortex with Radial Flow.
3. Fans; First Type of Fans; Second or Guibal Type of Fans; Third Type of Fans; Modern Type.
4. Fan Wheel; Vanes or Floats; Inlet; Width.
5. Capacity; Blast Area; Effect of Outlet on Capacity; Air per Revolution.
6. Pressure; Work.
7. Horse Power Required to Run a Fan; Engine Required to Run a Fan; Motor Required to Run a Fan; Width of Belt.
8. Efficiency; Air per Horse Power.
9. Exhausters.
10. Housing; Dimensions of Housings; Shaft.
11. Cone Wheels.
12. Disk Fans; Number of Revolutions per Minute; Capacity of a Disk Fan; Horse Power Required.
13. Choosing a Fan. Index.

Twenty-two tables have been prepared and they have been arranged in the way, which the experience of the author in designing heating and ventilating plants has shown to be the most convenient. The tables are full and complete, all calculations having been very carefully checked, read and revised. XIV.+206 pages, 39 diagrams. Full limp leather pocketbook.

Round Corners, gilt edges. \$5.00.†

# CHARTS FOR LOW PRESSURE STEAM HEATING

FOR THE USE OF

ENGINEERS, ARCHITECTS, CONTRACTORS AND  
STEAM FITTERS.

**By J. H. KINEALY, M.E.**

*M. Am. Soc. M. E., M. Am. Soc. of H. and V. Eng'rs, &c., &c.*

---

The author has long been in the habit of using charts to aid him in his work. Knowing the value of them in saving time, simplifying work and ensuring correct calculations he feels confident that they will be appreciated by engineers, architects and contractors, for whose benefit they have been compiled. Care has been taken to make the charts as clear and as easily understood and, above all, as accurate as possible. They have been based upon theoretical considerations, modified by what is considered to be good practice in this country.

---

CHART 1.—This chart is for determining the number of square feet of heating surface of a low pressure steam heating system, pressure not to exceed 5 lbs. per square inch by the gauge, necessary to supply the heat lost through the various kinds of wall surfaces of rooms. The chart is divided into four parts. CHART 2.—For determining the diameters of the supply and return pipes for a heating system. CHART 3.—For finding the number of square feet of boiler heating surface and the number of square feet of grate surface for a boiler that is to supply steam to a steam heating system. CHART 4.—For determining the area of the cross section of a square flue, or the diameter of a round flue, leading from an indirect radiation heater to the register in a room to be heated.

Full details are given for the use of these cards

These four charts are printed on heavy white card-board and bound together with cloth, size 13 in. by 9¼ in., \$1.00†.

*These cards are securely packed for mail and sent to any part of the World on receipt of price.*

# Gas Analyst's Manual.

By JAQUES ABADY, M. Inst. Mech. E.

(Incorporating F. W. Hartley's "Gas Analyst's Manual" and  
"Gas Measurement.")

---

## EXTRACT FROM PREFACE.

The numerous requests received by the Publishers for the late Mr. F. W. Hartley's "Gas Analyst's Manual and "Gas Measurement" form the justification of the present work, which embodies practically the entire contents of those two volumes. It has been found, however, that their scope was too narrow to comply with modern requirements in various directions, although ample at the time they were written, and so I have ventured to add such extensions as appeared to be necessary in order to meet the demand which exists for a comprehensive work on Gas Apparatus and its use.

This large work has been in course of preparation for the past three years by Mr. Jaques Abady, and has been very carefully revised by other experts.

Many valuable tables of data have been included, a number of which come from the private note books of the Author, being practically results obtained by him during many years of work as Expert, Gas Engineer and Gas-Works Materials Manufacturer.

## CONTENTS OF CHAPTERS.

- 1.—Photometry (58 pages.)
- 2.—The table photometer and Photometer Room (38 pages.)
- 3.—Standard of Light (32 pages.)
- 4.—Calorimetry and Specific Gravity, with a note on Mond Gas (48 pages.)
- 5.—The Referees' Test for Sulphur and Ammonia in Gas (28 pages.)
- 6.—Coal Testing (22 pages.)
- 7.—Testing Enrichment and Purification Materials (33 pages.)
- 8.—Purity Tests for Gas in the Various Stages of its Manufacture (43 pages.)
- 9.—Testing Bye-products (35 pages.)
- 10.—Technical Gas Analysis (63 pages.)
- 11.—Meter-Testing Apparatus (48 pages.)
- 12.—Meter and Governor Testing (34 pages.)
- Appendix, Data, Tables, Formulae, etc., (38 pages.)

And very complete Contents, Index and List of Illustrations, and Tables, &c. &c.

XV+560 pages,  $5\frac{1}{2} \times 8\frac{1}{2}$  in., 93 illustrations and 9 folding plates.

**Bound in Handsome Half Leather - \$6.50 †**

*The Design and Construction*

OF

# OIL ENGINES.

WITH FULL DIRECTIONS FOR

**Erecting, Testing, Installing, Running and Repairing.**

Including descriptions of American and English

**KEROSENE OIL ENGINES.**

---

**By A. H. GOLDINGHAM, M.E.**

---

**SYNOPSIS OF CONTENTS OF CHAPTERS:**

1. Introductory ; classification of oil engines ; vaporizers ; ignition and spraying devices ; different cycles of valve movements. 2. On design and construction of oil engines ; cylinders ; crankshafts ; connecting rods ; piston and piston rings ; fly-wheels ; air and exhaust rams, valves and valve boxes ; bearings ; valve mechanism, gearing and levers ; proportions of engine frames ; oil-tank and filter ; oil supply pipes ; different types of oil engines ; cylinders made in more than one piece ; single cylinder and double cylinder engines ; crank-pin dimensions ; fitting parts ; assembling of oil engine ; testing water jackets, joints, etc. 3. Testing for leaks, faults, power, efficiency, combustion, compression ; defects as shown by indicator ; diagrams for setting valves ; how to correct faults ; indicator fully described ; fuel consumption test, etc. 4. Cooling water tanks ; capacity of tanks ; source of water supply ; system of circulation ; water pump ; exhaust silencers ; self starters ; utilization of waste heat of exhaust. 5. Oil engines driving dynamo ; installation of plant ; direct and belt connected ; belts ; power for electric lighting ; loss of power. 6. Oil engines driving air compressors ; direct connected and geared ; table of pressures ; pumping outfits ; oil engines driving ice and refrigeration outfits. 7. Full instructions for running different kinds of oil engines. 8. Hints on repairs ; adjustment of crank-shaft and connecting rod bearing ; testing oil inlet valves and pump ; fitting new spur gears, etc. 9. General descriptions with illustrations of American and English oil engines ; methods of working ; portable oil engines, etc., etc. Index and tables.

**XIII. + 196 pages, 7½ x 5½, 79 illustrations, cloth, \$2.00**

PRACTICAL HANDBOOK  
ON  
**GAS ENGINES.**

*With Instructions for Care and Working of the Same.*

By G. LIECKFELD, C.E.

TRANSLATED WITH PERMISSION OF THE AUTHOR BY

Geo. Richmond, M.E.

TO WHICH HAS BEEN ADDED FULL DIRECTIONS FOR THE RUNNING OF

**OIL ENGINES.**

---

CONTENTS.

Choosing and installing a gas engine. The construction of good gas engines. Examination as to workmanship. As to running. As to economy. Reliability and durability of gas engines. Cost of installing a gas engine. Proper erection of a gas engine. Construction of the foundation. Arrangement for gas pipes. Rubber bag packing devices. Exhaust pipes. Air pipes. Setting up gas engines. Brakes and their use in ascertaining the power of gas engines. Theory of the brake. The Brauer band brake. Arrangement of a brake test. Explanation of the expressions "Brake Power" and "Indicated Power." Comparisons of the results of the brake test and the indicated test. Quantity of work consumed by external friction of the engine. Distribution of heat in a gas engine. Attendance on gas engines. General remarks. Gas engine oil. Cylinder lubricators. Rules as to starting and stopping a gas engine. The cleaning of a gas engine. General observations and specific examination for defects. Different kinds of defectives. The engine refuses to work. Non-starting of the engine. Too much pressure on the gas. Water in the exhaust pot. Difficulty in starting the engine. Clogged slide valve. Leaks in gas pipes. Unexpected stopping of engine. Irregular running. Loss of power. Weak gas mixtures. Late ignition. Cracks in air inlet. Back firing. Knocking and pounding inside of engine. Dangers and precautionary measure in handling gas engines. Examination of gas pipes. Precautions when:—Opening gas valves. Removing piston from cylinder. Examining with light openings of gas engines. Dangers in starting. Dangers in cleaning. Safeguards for fly-wheels. Danger of putting on belts. **Oil Engines.** Gas engines with producer gas. Gasoline and oil engines. The "Hornsby-Akroyd" oil engine. Failure to start. Examination of engine in detail. Vaporizer valve box. Full detailed directions for the management of Oil Engines. Concluding remarks. 120 pages, illustrated, 12mo, cloth, \$1.00

# THE CHEMISTRY OF FIRE

—AND—

## FIRE PREVENTION.

---

**A HANDBOOK FOR INSURANCE SURVEYORS,  
WORKS MANAGERS, AND ALL INTERES-  
TED IN FIRE RISKS AND  
THEIR DIMINUTION**

BY

**HERBERT INGLE, F.I.C., F.C.S.**

—AND—

**HARRY INGLE, PH.D., B.Sc.**

TECHNOLOGICAL CHEMIST.

---

### **Contents of Chapters.**

**I.** Definition of Fire. Old Theories as to its Nature, Modern Views of Combustion—The Physical and Chemical Properties of the Atmosphere, the Chief Properties of its Constituents—Some Conditions Affecting the Combustion of Substances in Air, the Principle of the Miner's Safety Lamp.

**II.** Explanation of Chemical Terms, Outline of the Atomic Theory. Brief Explanations of the Use of Chemical Formulæ and Equations.

**III.** Methods of Preparations of Oxygen, Brin's Oxygen Manufacture—Heat Measurements, the Calorimeter, Calorific Power of Substances Burning in Air.

**IV.** Coal Gas: Its Preparation, Purification and Composition—Properties of Its Chief Constituents—Reciprocity of Combustion—Gaseous Diffusion—Explosion of Gases—Dust Explosions.

**V.** Fuel: Chemical Composition of Wood, Charcoal, Peat, Lignite, Coal, Coke, Petroleum, Coal Gas—Use of "Atmospheric Burners"—Producer Gas—Water Gas—Dawson Gas.

# CROSS SECTION PAPER.

---

**Scale EIGHT to ONE Inch.**

## THE HANDY SKETCHING PAD.

Printed on one side, in blue ink, all the lines being of equal thickness with useful tables. Size 8 x 10 inches. Price, 25c. each. Per dozen pads, \$2.50.

## THE HANDY SKETCHING BOOK.

Made from this paper but printed on both sides. Size of book 5 x 8 inches, stiff board covers. Price, 25c. each; per dozen books, \$2.50.

---

**Scale EIGHT to ONE Inch.**

A large sheet with heavy inch lines and half inch lines, printed in blue ink. Size of sheet, 17 x 22 inches. Per quire (24 sheets),

---

**Scale TEN to ONE Inch.**

Size 17 x 22 inches, printed in blue ink, with heavy inch lines and half inch lines. Per quire (24 sheets),

---

## The Electrician's Sketching Book.

Made from this paper. Scale 10 to 1 inch. Size of book 5 x 8 inches, with stiff card board covers. Price, 25c. each; per dozen, \$2.50.

## The Electrician's Plotting Pad.

Same paper, only printed on one side, size of pad, 8 x 10 inches, 25c.; per dozen, \$2 50.

Any Books and Pads Assorted, per dozen, \$2 50.

**ANY QUANTITY MAILED TO ANY PART OF THE WORLD  
POST-PAID ON RECEIPT OF PRICE.**

This paper is *Printed from plates*. Try it and you will find it

**GOOD, ACCURATE AND CHEAP.**

---

**SPON & CHAMBERLAIN,**

**NEW YORK, U. S. A.**

## 25c. BOOKS.

---

**MODEL BOILER MAKING.** Contains full instructions for designing and making model stationary, marine and locomotive boilers. Fully illustrated with original working drawings.

**METAL WORKING TOOLS AND THEIR USES.** A Handbook for Young Engineers and Apprentices. Shows how to use simple tools required in metal working and model making. Illustrated.

**SIMPLE MECHANICAL WORKING MODELS.** How to make and use them, including stationary engine locomotive, steamboat, waterwheel, etc. With 34 illustrations.

**MODEL STEAMER BUILDING.** A practical handbook on the design and construction of model steamer hulls, and fittings, with 39 scale drawings.

**MACHINERY FOR MODEL STEAMERS.** On the design, construction, fitting and erecting of engines and boilers for model steamers, with 44 scale drawings.

**THE SLIDE VALVE.** Simply explained for working engineers. Fully illustrated.

**THE LOCOMOTIVE,** simply explained. A first introduction to the study of the locomotive engine, their designs, construction and erection, with a short catechism, and 26 illustrations.

**THE BEGINNER'S GUIDE TO THE LATHE.** An elementary instruction book on turning in wood and metal. By P. MARSHALL. 76 pages, 75 illustrations.

**GAS AND OIL ENGINES.** A practical handbook on, with instructions for care and running. Illustrated.

**STANDARD SCREW THREADS.** A Guide to Standard Screw Threads and Twist Drills. (Small sizes.) Illustrated.

**STEAM TURBINES.** How to design and build them. A practical handbook for model makers. Contents of Chapters. 1. General Consideration. 2. Pressure Developed by an Impinging Jet; Velocity and Flow of Steam Through Orifices. 3. Method of Designing a Steam Turbine. 4. Complete Designs for DeLaval Steam Turbines; Method of Making Vanes; Shrouding. 5. The Theory of Multiple Stage Turbines. Fully illustrated with detail drawings and tables.

**MECHANICAL DRAWING,** simply explained. Use of instruments, reading and setting out drawings, inking in and finishing, drawings for reproduction, lettering, with 44 illustrations.

**ACETYLENE GAS.** How to make and use it. A practical handbook on the uses of Acetylene Gas, suitable apparatus for its generation, hints and fitting up, etc. 34 illustrations.

**LETTERING FOR DRAWINGS.** A System of Easy Lettering, by J. H. CROMWELL, with an appendix of eight new alphabets by G. Martin. Giving a variety of very attractive alphabets suitable for engineering and architectural drawings. **8th thousand. 50c.**

**PROJECTION DRAWING.** Twelve plates on, by OSWALD GUETH, M.E., Inst. Mech. Drawing, Cooper Inst., N. Y. Arranged in three sections: *Projections*, plate 1, Prisms; 2, Pyramids; 3, Inclined Prisms; 4, Inclined Pyramids. *Sections*, plate 5, Prisms and Pyramids; 6, Cones; 7, Spheres; 8, Various Solids. *Intersections*, plate 9, Prisms; 10, Cylinders; 11, Spheres; 12, Prisms and Pyramids. **Size, 8½ x 11 in., sewn, 75c.**

**ENGINEERING MATHEMATICS.** Simply explained. A textbook for students, apprentices and engineers. By H. H. HARRISON. **165 pages, 59 diagrams, cloth, 75c.**

**ALGEBRA SELF-TAUGHT.** By W. P. HIGGS. 7th edition. The simplest and best book for beginners, mechanics, young engineers and electricians. Commencing from the very beginning, and advancing step by step, with many practical examples worked out. The signs given are fully explained. The language used is so simple that a student can readily master algebra by a little home study. This is the book to help the young man get into a better position. **Bound in cloth, 60c.**

**EDUCATIONAL WOODWORK.** By A. C. HORTH. A complete manual for teachers and organizers of woodworking classes. Contents of Chapters: 1. First Year Course. 2. Second Year Course. 3. Third Year Course. 4. Fittings and Furniture. 5. Discipline. 6. Organization and Method. 7. The Instruction of the Physically and Mentally Deficient and Blind. 8. Object Lessons. Fully illustrated with reproductions from photographs, drawings, and facsimile black-board lessons. **158 pages, 12mo., cloth, \$1.00 net.**

**WOODWORK JOINTS.** How to make and where to use them; including mortise and tenon joints, lap joints, dovetail joints, glue joints and scarfing joints. With a chapter on circular woodwork, revised and enlarged edition, 101 pages, 178 illustrations. **25c.**

**THE BEGINNER'S GUIDE TO FRETWORK.** Containing full instructions on the Use of Tools and Materials; and six full size Fretwork designs. With 39 pages and 26 illustrations. **25c.**

**VENEERING, MARQUETRY AND INLAY.** A practical instruction book in the art of Decorating Woodwork by these methods. By P. A. WELLS. 79 pages, 37 illustrations. **25c.**

**SOFT WOODS AND COLONIAL TIMBERS.** The selection and Uses of Soft Woods and Colonial Timbers. The cultivation, cutting and seasoning. 57 pages, 15 illustrations. **25c.**

**HARD WOODS, ENGLISH AND FOREIGN.** A practical description of Hard and Fancy Woods used by the carpenter and cabinet maker. By P. A. WELLS, 79 pages, 19 illustrations, **25c.**

# SPONS' Mechanics Own Book

**A WORK THAT SHOULD BE IN YOUR BOOKCASE.**

---

The general method of treatment of each subject, is first the raw materials worked upon, its characteristics, variations and suitability; secondly, the tools used, the sharpening and use; thirdly, devoted to typical examples of work to be done, materials, and how to do similar work, etc.

THE FOLLOWING ARE THE PRINCIPAL CONTENTS.

Mechanical Drawing, (13 pages.)  
Mechanical Movements, (55 pages.)  
Casting and Founding in Brass and Bronze, (30 pages.)  
Forging and Finishing, (46 pages.)  
Soldering in all its branches, (26 pages.)  
Sheet Metal Working, (10 pages.)  
Turning and Turning Lathes, (31 pages.)  
Carpentry, (224 pages.)  
Log Huts, Building, Etc., (8 pages.)  
Cabinet-Making, (36 pages.) Upholstery, (6 pages.)  
Carving and Fretwork, (13 pages.)  
Picture Frame Making, (4 pages.)  
Painting, Graining and Marbling, (28 pages.)  
Staining, (13 pages.) Gilding, (3 pages.)  
Polishing, (23 pages.) Varnishing, (4 pages.)  
Paper Hanging, (4 pages.) Glazing, (7 pages.)  
Plastering and White Washing, (9 pages.)  
Lighting, (8 pages.)  
Foundations and Masonry, (46 pages.)  
Roofing, (14 pages.)  
Ventilating and Warming, (13 pages.)  
Electric Bell and Bell Hanging, Gas Fitting, (8 pages.)  
Roads and Bridges, Banks, Hedges, Ditches and Drains, Asphalt Cement Floors, Water Supply and Sanitation.

Total number of pages 702. Total number illustrations 1,420  
Bound in substantial half-extra, - PRICE BY MAIL ONLY \$2.50

We have an 8 page circular giving full contents which will be sent free on application.

# WORKSHOP

# RECEIPTS.

THE MOST COMPLETE

Technical Cyclopedia in 5 Vols.

## First Series.

**Principal Contents.**—Bronzes, Cements, Dyeing, Electrometallurgy, Enamels, Etchings, Fireworks, Fluxes, Fulminates, Gilding, Gums, Japanning, Lacquers, Marble Working, Nitro-Glycerine, Photography, Pottery, Varnishes, etc., etc. 420 pages, 103 illustrations, 12mo, cloth, \$2.00.

## Second Series.

**Principal Contents.**—Acidimetry, Albumen, Alcohol, Alkaloids, Bitters, Bleaching, Boiler Incrustations, Cleansing, Confectionery, Copying, Disinfectants, Essences, Extracts, Fire-proofing, Glycerine, Gut, Iodine, Ivory Substitutes, Leather, Matches, Pigments, Paint, Paper, Parchment, etc., etc. 485 pages, 16 illustrations, 12mo, cloth, \$2.00.

## Third Series.

**Principal Contents.**—Alloys, Aluminium, Antimony, Copper, Electrics, Enamels, Glass, Gold, Iron and Steel, Liquors, Lead, Lubricants, Magnesium, Manganese, Mercury, Mica, Nickel, Platinum, Silver, Slag, Tin, Uranium, Zinc, etc., etc. 480 pages, 133 illustrations, 12mo, cloth, \$2.00.

## Fourth Series.

**Principal Contents.**—Water-proofing, Packing and Stowing, Embalming and Preserving, Leather Polishes, Cooling Air and Water, Pumps and Siphons, Dessicating, Distilling, Emulsifying, Evaporating, Filtering, Percolating and Macerating, Electrotyping, Stereotyping, Book-binding, Straw-plaiting, Musical Instruments, Clock and Watch Mending, Photography, etc., etc. 443 pages, 243 illustrations, 12mo, cloth, \$2.00.

## Fifth Series.

**Principal Contents.**—Diamond Cutting, Laboratory Apparatus, Copying, Filtering, Fire-proofing, Magic Lanterns, Metal Work, Percolation, Illuminating Agents, Tobacco Pipes, Taps, Tying and Splicing, Tackle Repairing Books, Netting, Walking Sticks, Boat-Building, etc., etc. 440 pages, 373 illustrations, 12mo, cloth, \$2.00.

**EACH SERIES has its own Contents and Index and is complete in itself.**

SPONS' ENCYCLOPÆDIA  
OF THE  
**Industrial Arts, Manufactures**  
AND  
**Commercial Products.**

---

EDITED BY

**G. G. ANDRE, F.G.S., Asso.=M. Inst. C.E.**

AND

**C. G. WARNFORD LOCK, F.L.S., F.G.S., M.I.M.M.**

Assisted by many prominent Manufacturers, Chemists and Scientists.

---

This encyclopedia is written by practical men for practical men.

*Raw Materials* form perhaps its most important feature and are dealt with in a way never before attempted.

*Manufacturers* are discussed in detail from the manufacturing standpoint by manufacturers of acknowledged reputation.

Special consideration is given to the utilization of waste, the prevention of nuisance, and the question of adulterations.

Technicalities are explained, and bibliographies (English, American, French, German, etc.), are appended to the principal articles.

Over 2,000 pages and nearly 2,000 illustrations.

We are offering a *Limited* number of sets of a

**SPECIAL THREE VOLUME EDITION HANDSOMELY  
BOUND IN HALF-MOROCCO, CLOTH-GILT,  
MARBLED EDGES, \$15.00 NET.**

---

A full descriptive circular can be had on application.

# Dubelle's Famous Formulas.

KNOWN AS

Non Plus Ultra Soda Fountain Requisites of Modern Times.

By G. H. DUBELLE.

*A practical Receipt Book for Druggists, Chemists, Confectioners and Venders of Soda Water.*

## SYNOPSIS OF CONTENTS.

INTRODUCTION.—Notes on natural fruit juices and improved methods for their preparation. Selecting the fruit. Washing and pressing the fruit. Treating the juice. Natural fruit syrups and mode of preparation. Simple or stock syrups.

## FORMULAS.

FRUIT SYRUPS.—Blackberry, black current, black raspberry, catwaba, cherry, concord grape, cranberry, lime, peach, pineapple, plum, quince, raspberry, red current, red orange, scuppernong grape, strawberry, wild grape. NEW IMPROVED ARTIFICIAL FRUIT SYRUPS.—Apple, apricot, banana, bitter orange, blackberry, black current, cherry, citron, curacao, grape, groseille, lemon, lime, mandarin, mulberry, nectarine, peach, pear, pineapple, plum, quince, raspberry, red current, strawberry, sweet orange, tangerine, vanilla. FANCY SODA FOUNTAIN SYRUPS.—Ambrosia, capillaire, coca-kina, coca-vanilla, coca-vino, excelsior, imperial, kola-coca, kola-kina, kola-vanilla, kola-vino, nectar, noyeau, orgeat, sherbet, syrup of roses, syrup of violets. ARTIFICIAL FRUIT ESSENCES.—Apple, apricot, banana, bergamot, blackberry, black cherry, black currant, blueberry, citron, cranberry, gooseberry, grape, lemon, lime fruit, melon, nectarine, orange, peach, pear, pineapple, plum, quince, raspberry, red currant, strawberry. CONCENTRATED FRUIT PHOSPHATES.—Acid solution of phosphate, strawberry, tangerine, wild cherry.—29 different formulas. NEW MALT PHOSPHATES—36. FOREIGN AND DOMESTIC WINE PHOSPHATES—9. CREAM-FRUIT LACTARTS.—28. SOLUBLE FLAVORING EXTRACTS AND ESSENCES—14. NEW MODERN PUNCHES—18. MILK PUNCHES—17. FRUIT PUNCHES—32. FRUIT MEADS—18. NEW FRUIT CHAMPAGNES—17. NEW EGG PHOSPHATES—14. FRUIT JUICE SHAKES—24. EGG PHOSPHATE SHAKES. HOT EGG PHOSPHATE SHAKES. WINE BITTER SHAKES—12. SOLUBLE WINE BITTERS EXTRACTS—12. NEW ITALIAN LEMONADES—18. ICE CREAM SODAS—39. NON-POISONOUS COLORS. FOAM PREPARATIONS. MISCELLANEOUS FORMULAS—26. LATEST NOVELTIES IN SODA FOUNTAIN MIXTURES—7. TONICS.—Beef, iron and cinchona; hypophosphite; beef and coca; beef, wine and iron; beef, wine, iron and cinchona; coca and calisaya. LACTARTS.—Imperial tea; mocha coffee; nectar; Persian sherbert. PUNCHES. EXTRACTS.—Columbia root beer; ginger tonic; soluble hop ale. LEMONADES.—French; Vienna. Egg nogg. Hop ale. Hot tom. Malt wine. Sherry cobbler. Saratoga milk shake. Pancreatin and wine. Kola-coco cordial. Iron malt phosphate. Pepsin, wine and iron, etc

157 Pages, Nearly 500 Formulas. 12mo, Cloth, \$1

Latest practice, New and original cuts.

---

# KATHARINE MELLISH'S COOKERY

AND

## DOMESTIC MANAGEMENT.

---

### SYNOPSIS OF CONTENTS.

Complete Breakfast Menus, with receipts, pages 1—27.

Complete Luncheon Menus, with receipts, pages 28—74.

Tea Menus, High Tea Menus, with receipts, pages 75—124.

Complete Dinner Menus, with receipts, pages 125—220.

**Processes:**—This chapter is illustrated with exact position of the **cook's hands** during the various operations of preparing, boning birds and joints, trussing fish, joints, poultry, game, hares, rabbits, etc. Larding and icing, etc.

Receipts of separate dishes.

Stocks and soups of all kinds, broth, gravy, etc.

**Fish.**—To clean, general rules for cooking. Numerous receipts for boiling, baking, stewing, frying fish of all kinds.

The preparation and making of gravies, stuffing, forcemeats, purees, garnishes and sauces for all purposes, with many receipts.

**Entrees.**—Their preparation and serving, with receipts.

**Joints.**—Preparation, cooking and serving of, with many receipts.

**Vegetables.**—Preparation and cooking of plain and dressed vegetables of all kinds and how to serve them.

**Poultry and game.**—Preparation, cooking and serving, with receipts.

Pastries, pudding and sweet dishes. Cakes, biscuits, bread.

**Omelets.**—With receipts for preparing, cooking and serving.

Ices, confectionery, syrups, jams, preserves and preserving, cordials, liqueurs, and aerated drinks. Cookery for invalids, carving, serving, etc., etc., and very complete index and contents.

987 pages, 56 full page colored plates, 439 illus. Size, 7½ in. x

10½ in. x 2½ in. Full waterproof texederm in 1, 3 or 5 vols.

Published Weekly,      Annual subscription,      Subscription 6 months, \$1.50  
 Single numbers, 8c.      \$3.00 postpaid.      "      4      "      \$1.00

# THE MODEL ENGINEER AND ELECTRICIAN.

The BEST Paper for Young Engineers, Students, Model Makers, Apprentices,  
and all interested in Mechanical and Electrical Work.

## SPECIAL FEATURES.

**Practical Articles** by experienced writers on the construction and working of model steam, gas and oil engines; model locomotives and railways; model boilers; model steam and electric launches, and sailing yachts; lathes and metal and wood-working tools; pattern-making; brass and iron founding; forging; model dynamos and motors; electric bells, telephones and batteries; accumulators; electric lighting; influence machines; electrical experiments; motor cycles, &c., &c.

**Model Engineers and their Work.**—Illustrated interviews with prominent model engineers, describing their workshops, their methods of working; and some of their models.

**Our Beginners' Column.**—A section devoted to elementary instruction on the use of tools; the making of simple apparatus and models, and the carrying out of easy experiments.

**Practical Letters from our Readers.**—A correspondence column, wherein readers can describe workshop appliances or methods of their own invention and discuss practical matters of mutual interest.

**Amateurs' Supplies.**—Under this heading short descriptions of new tools, apparatus and materials are inserted, thus keeping the reader posted up in the latest improvements.

**A System of Queries and Replies,** by which all readers of the journal can obtain information and advice on mechanical or electrical subjects.

**Original Working Drawings** and high-class illustrations are a regular feature of the journal.

**Prize Competitions** open to all readers, are announced from time to time, on all subjects.

**Model Yachting Notes, New Books, &c., &c.**

All subscriptions should be sent to

**SPON & CHAMBERLAIN,** Sole American Agents.

123-125 Liberty Street, New York, U. S. A.

X 914












LIBRARY OF CONGRESS

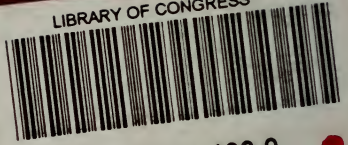

0 003 716 133 0

